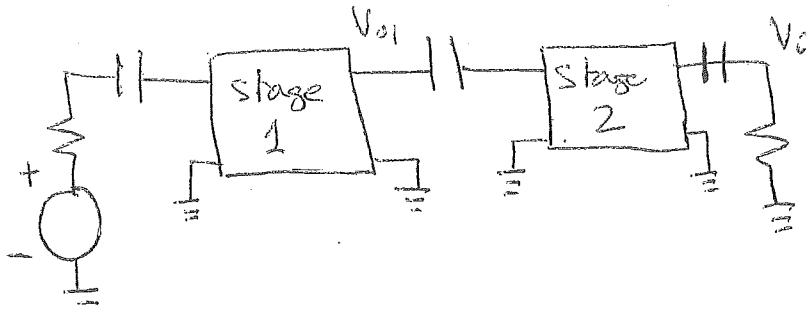


New topics/new lecture.


RC coupled multistage amplifiers:




→ 1st identify each stage: CS, CD, CG

→ Decide how to analyze depending on stages.

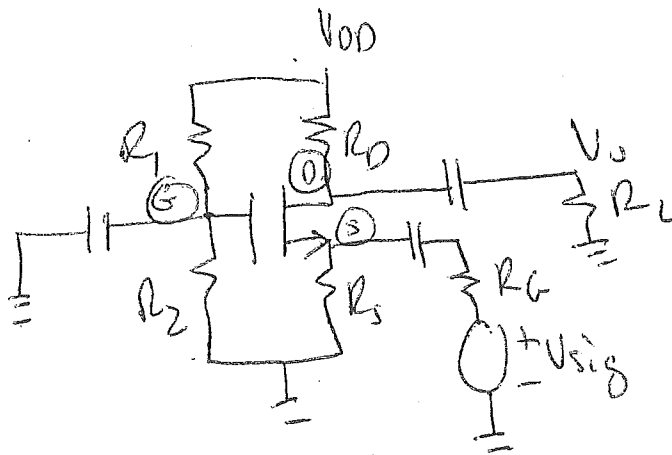→ Common-source amplifier (not discussed before).



DC Analysis (similar to CS amplifier).

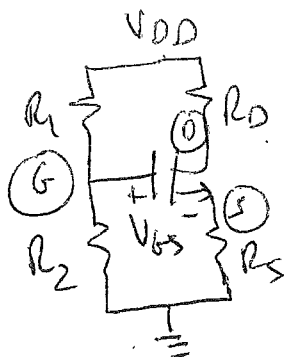

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$V_{GS} = V_G - R_S \left[ \frac{R_D}{2} (V_{GS} - V_T)^2 \right]$$

→ Find  $V_{GS}$

→ Find  $I_D$


→ Determine saturation

$$V_{GS} < V_T$$

→ Find  $I_{D,sat} = k(V_{GS} - V_T)$

12/2/2016

Madhus

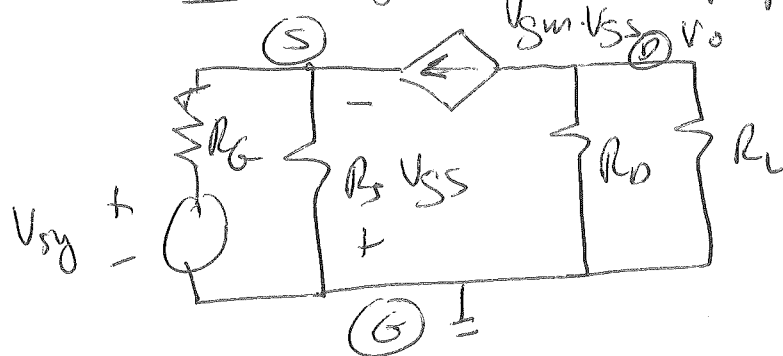Small signal of  $C_b$  amplifier $C_{gs} \rightarrow \text{short}$  $V_{DD} \rightarrow \text{ground}$ 

$$\frac{V_o}{V_{gs}} = -g_m R_{eq}$$

Node at (S) to find  $\frac{V_{gs}}{V_{sig}}$ 

$$\frac{V_s - V_{sig}}{R_G} + \frac{V_s}{R_s} = g_m V_{gs} \quad \text{and } V_{gs} = -V_s$$

$$\frac{V_s - V_{sig}}{R_G} + \frac{V_s}{R_s} = -g_m V_s$$

$$\frac{V_s}{R_G} + \frac{V_s}{R_s} + g_m V_s = \frac{V_{sig}}{R_G}$$

$$V_s \left( \frac{1}{R_G} + \frac{1}{R_s} + g_m \right) = \frac{V_{sig}}{R_G}$$

$$V_s \left( \frac{g_m R_s R_G + R_s + R_G}{R_s R_G} \right) = \frac{V_{sig}}{R_G}$$

$$\therefore \frac{V_s}{V_{sig}} = \frac{R_s}{g_m R_s R_G + R_s + R_G}$$

$$\text{and } \frac{V_{gs}}{V_{sig}} = - \frac{R_s}{g_m R_s R_G + R_s + R_G} \quad \left( \frac{1/R_s}{1/R_s} \right)$$

$$\text{or } \frac{V_{gs}}{V_{sig}} = - \frac{1}{g_m R_G + 1 + \frac{R_G}{R_s}}$$

$$\text{and } g_m R_G + 1 = R_G \left( g_m + \frac{1}{R_G} \right)$$

$$\frac{1}{\frac{1}{g_m} \parallel R_G}$$

→ cont'd

↳ Cont's


Finally:

$$\frac{V_{gs}}{V_{sig}} = - \frac{1}{\frac{R_G}{R_S} + \frac{R_G}{g_m \parallel R_G}}$$

$$\text{And } \frac{V_o}{V_{sig}} = (-g_m R_{eq}) \left( \frac{-1}{\frac{R_G}{R_S} + \frac{R_G}{g_m \parallel R_G}} \right)$$

Or using Input resistance:

$$R_{in} = \frac{V_S}{I_S}$$

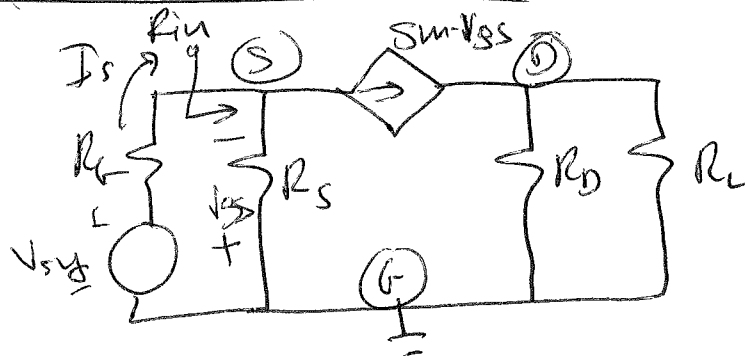

Node (S):

$$\frac{V_S}{R_S} + \frac{V_S - V_{sig}}{R_G} = g_m V_{gs}$$

$\underbrace{\hspace{1.5cm}}_{-I_S}$

$$\text{and } V_{gs} = -V_S$$

$$\frac{V_S}{R_S} + I_S = -g_m V_S$$

$$V_S \left( \frac{1}{R_S} + g_m \right) = I_S$$


$$R_{in} = \frac{V_S}{I_S} = \frac{1}{\underbrace{\frac{1}{R_S} + g_m}_{\text{sum of 2 conductances}}} = \frac{1}{g_m \parallel R_S}$$

And

$$\frac{V_{gs}}{V_{sig}} = - \frac{R_{in}}{R_{in} + R_G}$$

② 12/2/2016  
Madhus


CG - amplifier example:

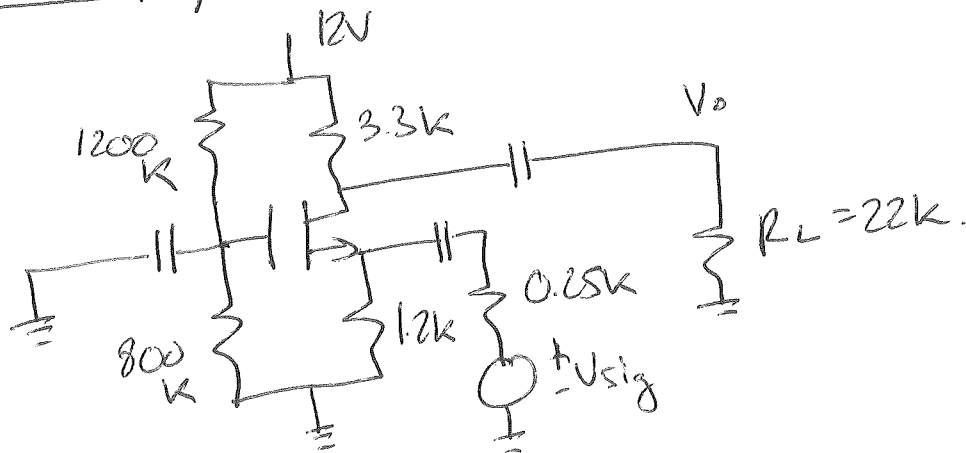

$$K = 1.5 \text{ mA/V}^2$$

$$V_T = 0.9 \text{ V}$$

DC analysis

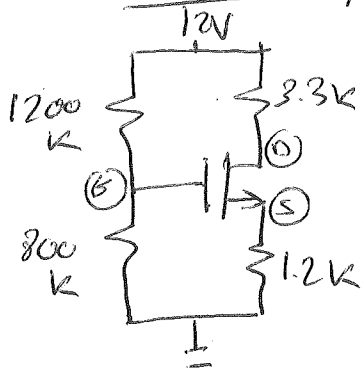

$C_{gs} \rightarrow \text{open}$

$$V_G = 12 \cdot \frac{800}{800 + 1200} = 4.8 \text{ Volts}$$

$$4.8 - 1.2k \left( \frac{1}{2} (1.5 \text{ mA/V}^2) (V_{GS} - 0.9)^2 \right) = V_{GS}$$

$$4.8 - 0.9 V_{GS}^2 + 1.62 V_{GS} - 0.729 = V_{GS}$$

$$4.071 + 0.62 V_{GS} - 0.9 V_{GS}^2 = 0$$

$$V_{GS} = 2.499 \text{ V}$$

$$V_{GS} = 2.499 \text{ V}$$

$$= -1.81 \text{ V}$$

$$I_D = (1.918 \text{ uA}) (1.2k) = 2.3 \text{ V}$$

$$V_D = 12 \text{ V} - (1.918 \text{ uA}) (3.3k) = 5.672 \text{ V}$$


$$\rightarrow V_{DS} = 3.37 \text{ V} > 2.499 - 0.9$$

$$V_{DS} = 5.672 - 2.3 \text{ V} \quad \checkmark$$

Check sat:  $V_{DS} > V_{GS} - V_T$

$$g_m = 1.5 (2.499 - 0.9) = 2.398 \text{ mS}$$

# Small-signal eq. circuit

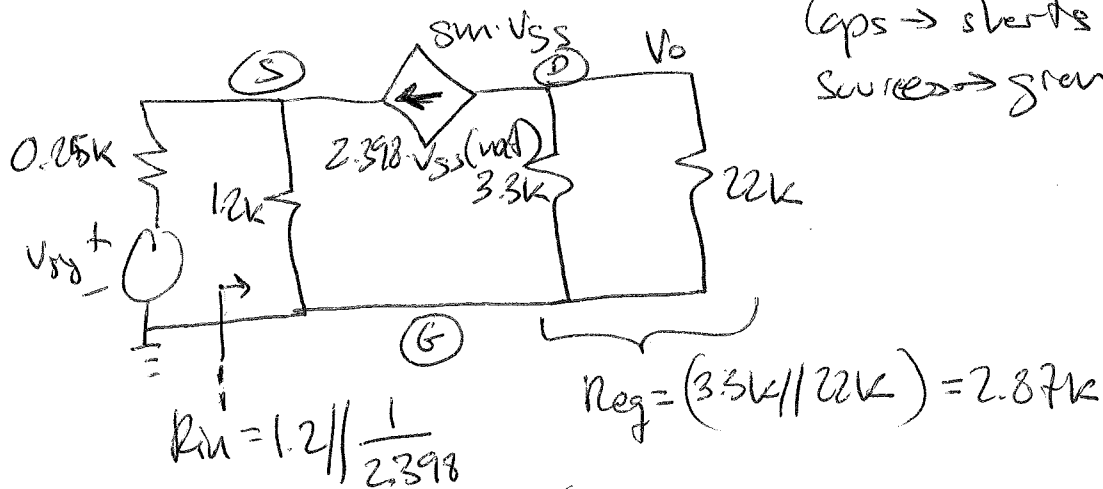


Caps  $\rightarrow$  shorts  
 Sources  $\rightarrow$  ground.

$$R_{in} = 0.3095k = \frac{(1.2k)(0.417k)}{1.817k}$$

$$\frac{V_{gs}}{v_{sig}} = -\frac{R_{in}}{R_{in} + R_{sig}}$$
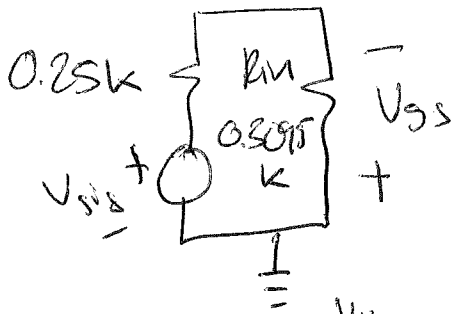
$$\frac{V_{gs}}{v_{sig}} = -\frac{0.3095}{0.25 + 0.3095} = -0.5531$$



$$\frac{V_o}{V_{gs}} = -g_m \cdot R_{eq}$$

$$\frac{V_o}{V_{gs}} = -2.398 \times 2.87 = -6.882$$


$$\therefore \frac{V_o}{v_{sig}} = 3.806 \left( \frac{V}{V} \right) = (-0.5531)(-6.882)$$

**EE 381 ELECTRONICS I (Madhu)**  
**REVIEW PROBLEMS FOR THE FINAL EXAM**

**Problem 1:**  $k = 0.2 \text{ mA/V}^2$  and  $V_T = 1.5 \text{ V}$ .

(a) Find  $V_o$ .


(b) Find the maximum value that  $R_D$  can have before the transistor goes out of saturation. Find  $V_o$  for this condition.

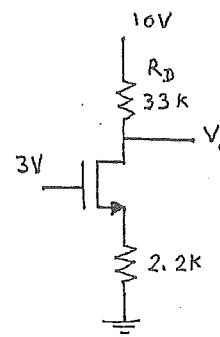

**Problem 2:**  $k_1 = 1.25 \text{ mA/V}^2$ ,  $k_2 = 2.5 \text{ mA/V}^2$ .  $|V_T| = 0.8 \text{ V}$  for both.

(a) Find  $V_o$ .


(b) Replace the current source by a resistor  $R_I$ . What is the value of  $R_I$ ?

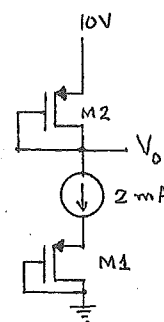

**Problem 3:**  $\mu_n C_{ox} = 0.050 \text{ mA/V}^2$  and  $\mu_p C_{ox} = 0.025 \text{ mA/V}^2$ .  $|V_T| = 0.9 \text{ V}$  for both.


(a) If  $(W/L) = 10$  for both transistors, find  $I_D$  and  $V_o$ .

(b) Repeat the calculations of Part (a) if  $(W/L)$  of the NMOS is changed to 4, keeping  $(W/L)$  of the PMOS at 10.

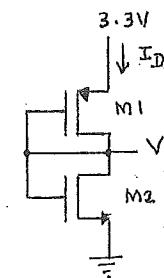

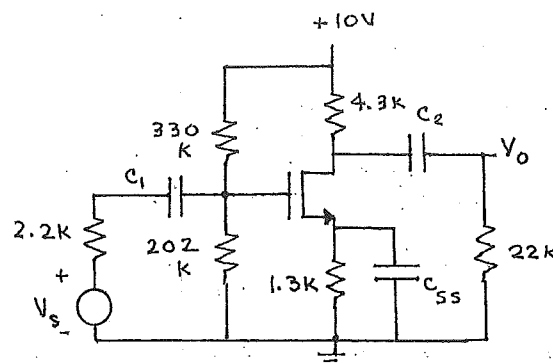**Problem 4:**  $k = 0.9 \text{ mA/V}^2$  and  $V_T = 0.5 \text{ V}$ .  $C_{gs} = 12 \text{ pF}$ .  $C_{gd} = 4 \text{ pF}$ .  $C_{ds} = 6 \text{ pF}$ .


Determine the midband gain and the upper cutoff frequency.



**Problem 5:** The amplifier of the previous problem is required to have a lower cutoff frequency of 30 Hz. (Note the units!) Select the value of  $C_{SS}$  so that it results in a pole at the specified lower cutoff frequency. Select the value of  $C_I$  so that the pole due to it cancels the zero caused by  $C_{SS}$  and select the value of  $C_2$  so that the pole due to it is at 3 Hz.


**Problem 6:**  $\mu_n C_{ox} = 0.092 \text{ mA/V}^2$ .  $|V_T| = 0.9 \text{ V}$ .  
 $(W/L) = 62.5$ .  $\lambda = 0.025 \text{ V}^{-1}$  for both.

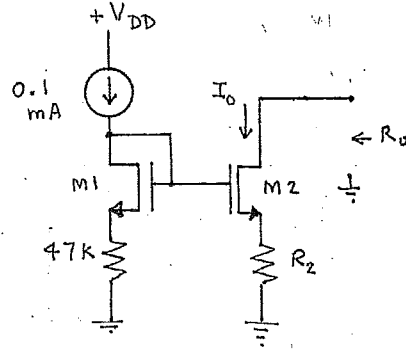- (a) Find the value of  $R_2$  so as to make  $I_o = 0.05 \text{ mA}$ .  
 (b) Find the output resistance  $R_o$ .



**Problem 7:** In the 2-stage CMOS op amp shown below, the sizing ratios of the different transistors are shown in parenthesis.  $\mu_n C_{ox} = 0.160 \text{ mA/V}^2$  and  $\mu_p C_{ox} = 0.064 \text{ mA/V}^2$ .

$|V_T| = 0.7 \text{ V}$  for all transistors.  $\lambda = 0.025 \text{ V}^{-1}$  for NMOS and  $0.05 \text{ V}^{-1}$  for the PMOS devices.

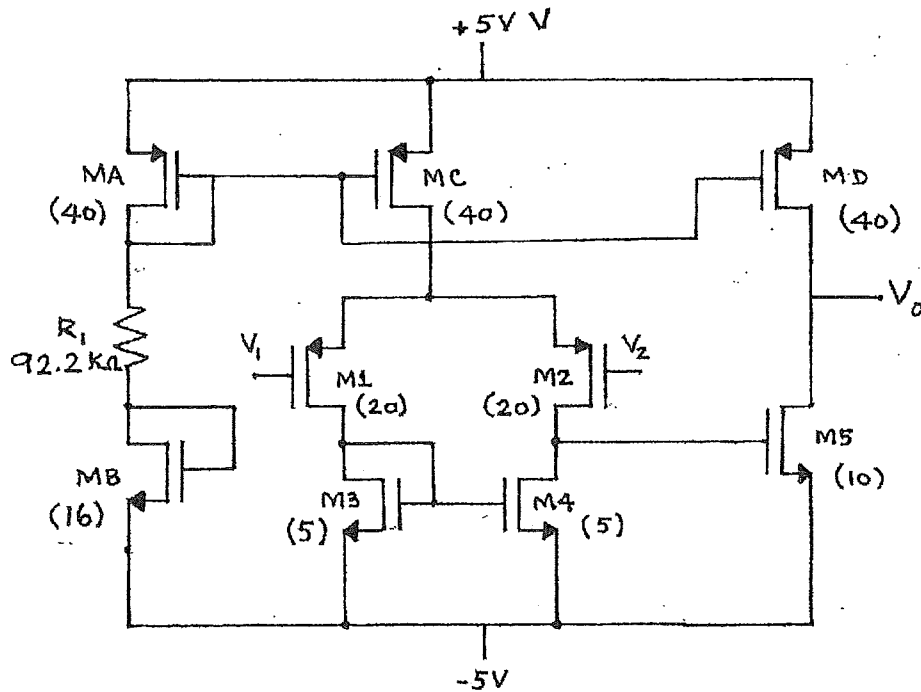


- (a) Determine the Q point values of the drain and gate voltages. Assume that  $V_o = 0$  at the Q point.

(b) Determine the diff mode gain.

**Problem 8:** The asymptotic value of the gain at  $\omega_x$  is given as 97 dB. onstz

(a) Write the expression of the gain function. Be sure to evaluate the constant  $K$ .

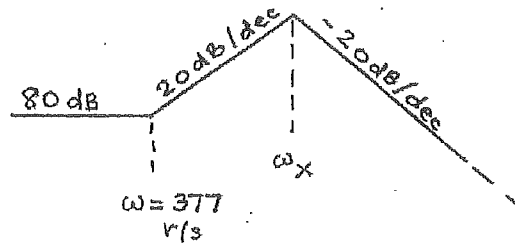(b) Draw the phase plot. Be sure to include all relevant numerical information in the diagram.



**Problem 9:** A two stage op amp has an equivalent circuit with parameters and element values as follows:  $g_{m2} = 1.5 \text{ mS}$ ;  $R_{o1} = 40 \text{ k}\Omega$ ;  $C_1 = 13.5 \text{ pF}$ ;  $g_{m5} = 0.8 \text{ mS}$ ;  $R_{o2} = 62.5 \text{ k}\Omega$ ;  $C_2 = 1.2 \text{ pF}$ .


(a) Sketch the Bode magnitude and phase plots.

(b) Determine the value of the Miller compensation capacitor  $C_C$  needed to introduce a phase margin of  $60^\circ$ .

**PROBLEM 10:** Assume ideal diodes. Find the range of values of  $V_{in}$  for each of the following two states:

(a) both diodes are ON.

(b) D1 ON and D2 OFF.

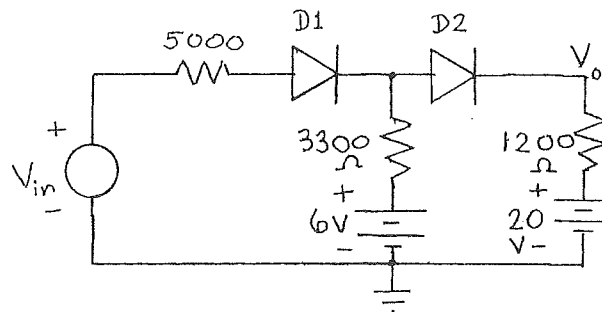




# REVIEW PROBLEMS FOR FINAL EXAM

12/5/2018

Madhu

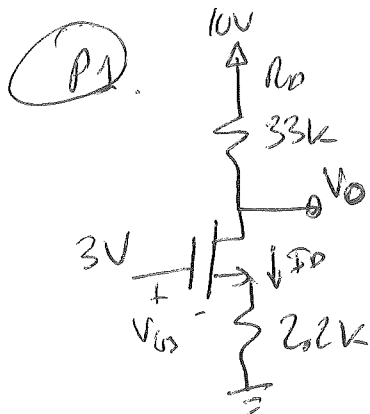

$$k = 0.2 \text{ mA/V}^2$$

$$V_T = 1.5 \text{ V}$$

a) Find  $V_O$ .

b) Find max value of  $R_D$  for saturation and  $V_O$  for this condition.

$$(a) \quad 3 - 2.2 \left( \frac{1}{2} 0.2 (V_{GS} - V_T)^2 \right) = V_{GS}$$

$$3 - 0.22 V_{GS}^2 + 0.66 V_{GS} - 0.495 = V_{GS}$$

$$2.505 - 0.34 V_{GS} - 0.22 V_{GS}^2 = 0$$

$$V_{GS} = -4.23 \text{ V}$$

$$= 2.689 \text{ V}$$

$$V_{GS} = 2.689 \text{ V}$$

$$I_D = 0.1414 \text{ mA}$$

$$\text{And } V_O = 5.335 \text{ V} = 10 - I_D R_D$$

$$(b) \quad V_{GD} = V_T \leq 1.5 \text{ V}$$

$$V_{GD} = 1.5 \text{ V}$$

$$V_D = 1.5 \text{ V (min)}$$

$$R_D = 60.11 \text{ k}\Omega$$

$$V_{DS} = V_{GS} - V_T = 3 - 1.5 = 1.5 \text{ V}$$

$$V_{DS} = \underbrace{10 - I_D R_D}_{V_D} - \underbrace{I_D R_S}_{V_S}$$

$$V_{DS} = 1.189 = (10 - 0.1414 \cdot R_D) - 0.311$$

$$R_D = \frac{1.189 + 0.311}{0.1414} = 3.32 \text{ k}\Omega$$

$$V_{DS} = 1.189 = \underbrace{(10 - I_D R_D)}_{V_D} - \underbrace{I_D R_S}_{V_S}$$


$$1.189 = 10 - 0.1414 \cdot R_D - 0.311$$

$$1.189 - 10 + 0.311 = -0.1414 R_D$$

$$R_D = \frac{8.5}{0.1414} = 60.11 \text{ k}\Omega$$

$$V_O = 10 - 8.5 = 1.5 \text{ V}$$

#2

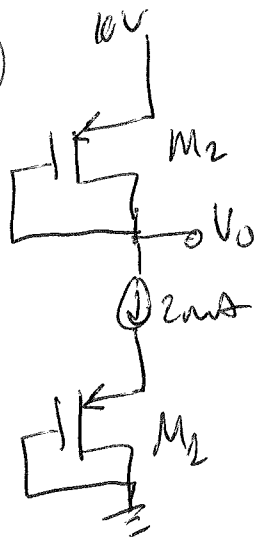

$$k_1 = 1.25 \text{ mA/V}^2$$

$$k_2 = 2.5 \text{ mA/V}^2$$

(a)  $V_O$ .

$$|V_T| = 0.8 \text{ V}$$

$$M_2: I_D = 2 \text{ mA}$$

$$2 \text{ mA} = \frac{1}{2} (1.25 \text{ mA/V}^2) (V_{GS_2} - 0.8)^2$$

$$V_{GS_2} = 2.065 \text{ V} \leftarrow$$

$$V_{OV} = \sqrt{\frac{4}{2.5}} = 1.26 \text{ V}$$

$$V_{GS} = V_{OV} + V_T$$

$$V_O = 7.935 \text{ V}$$

$$= (10 - 2.065 \text{ V})$$

(b) Replace current source by  $R_1$ . What is  $R_1$ ?

$$\begin{cases} V_O = 7.935 \text{ V} \\ R_1 ? \\ V_{S_1} = 2.589 \text{ V} \end{cases}$$

$$2 \text{ mA} = \frac{1}{2} (1.25 \text{ mA/V}^2) (V_{OV}^2)$$


$$V_{GS_1} = V_{S_1} = 2.589 \text{ V}$$

$$V_{S_1} = 2.589 \text{ V}$$

$$R = \frac{7.935 - 2.589}{2 \text{ mA}} = 2.673 \text{ k}\Omega$$

P3

② 12/5/246  
Madhu

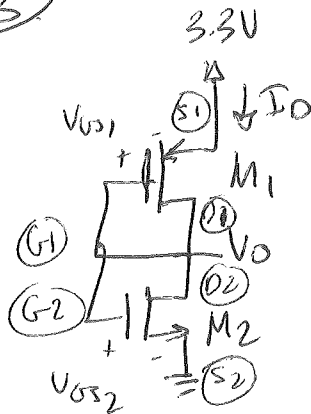

$$\mu_n C_{ox} = 0.05 \text{ mA/V}^2$$

$$\mu_p C_{ox} = 0.025 \text{ mA/V}^2$$

$$N_{T1} = 0.9 \text{ V}$$

(a)  $\frac{W}{L} = 10$  for both. Find  $I_D$  +  $V_O$

$$k_n = 10 \cdot 0.05 \text{ mA/V}^2 = 0.5 \text{ mA/V}^2$$

$$k_p = 10 \cdot 0.025 \text{ mA/V}^2 = 0.25 \text{ mA/V}^2$$

$$I_{Dn} = I_{Dp}$$

$$\frac{1}{2} 0.5 \text{ mA/V}^2 (V_{GS1} - V_T)^2 = \frac{1}{2} 0.25 \text{ mA/V}^2 (V_{GS2} - V_T)^2$$

$$\frac{V_{GS1} - 0.9}{V_{GS2} - 0.9} = \sqrt{\frac{0.25}{0.5}} = 1.414$$

$$V_{GS1} - 0.9 = 1.414 V_{GS2} - 1.273$$

2 eq, 2 unknowns

$$\begin{cases} V_{GS1} = 1.414 V_{GS2} - 0.3728 \\ V_{GS1} + V_{GS2} = 3.3 \end{cases}$$

$$V_{GS1} = 1.778 \text{ V}$$

$$V_{GS2} = 1.521 \text{ V}$$

(b)  $\left(\frac{W}{L}\right)_n = 4$   $\left(\frac{W}{L}\right)_p = 10$

$$k_n = 0.2 \text{ mA/V}^2$$

$$k_p = 0.25 \text{ mA/V}^2$$

$$0.1 (V_{GS2} - 0.9)^2 = 0.125 (V_{GS1} - 0.9)^2$$

$$\frac{V_{GS2} - 0.9}{V_{GS1} - 0.9} = \sqrt{\frac{0.125}{0.1}} = 1.118$$

$$V_{GS2} - 0.9 = 1.118 V_{GS1} - 1.006$$


$$\begin{cases} 1.118 V_{GS1} - V_{GS2} = 0.1062 \\ V_{GS1} + V_{GS2} = 3.3 \end{cases} \begin{matrix} \text{2 eq} \\ \text{2 unknowns} \end{matrix}$$

$$V_{GS1} = 1.608 \text{ V}$$

$$V_{GS2} = 1.692 \text{ V}$$



PU.

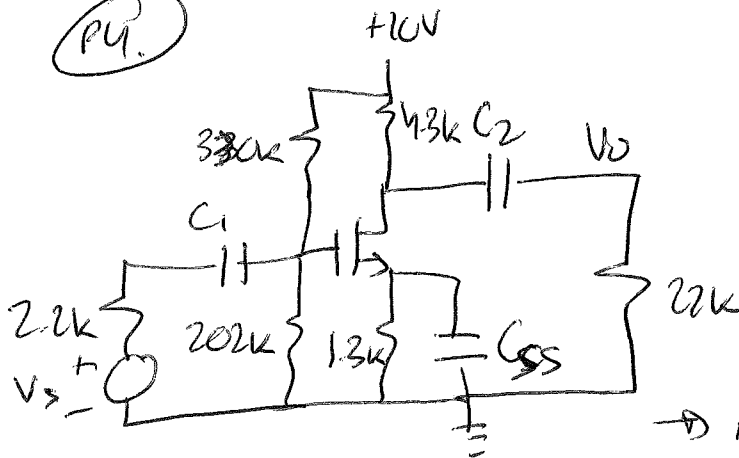

$$k = 0.9 \text{ mA/V}^2$$

$$V_T = 0.5$$

$$C_{SS} = 12 \text{ pF}$$


$$C_{sd} = 4 \text{ pF}$$

$$C_{ds} = 16 \text{ pF}$$

→ Find midband gain and upper cutoff frequency.

DC Analysis

Caps → open

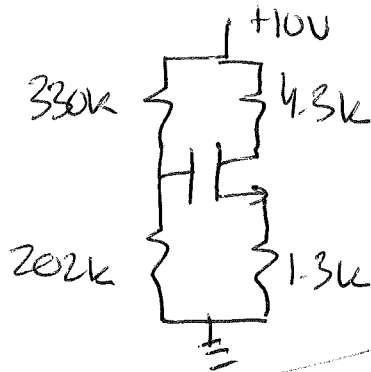

$$V_G = 10V \cdot \frac{202k}{202k + 330k} = 3.797V$$

$$V_{GS} = 3.797 - \left( \frac{1}{2} \cdot 0.9 (V_{GS} - 0.5)^2 \right) (1.3k)$$

$$V_{GS} = 3.797 - 0.585 (V_{GS} - 0.5)^2$$

$$3.797 - 0.585 V_{GS}^2 + 0.585 V_{GS} - 0.14625 = V_{GS}$$


3

$$V_{GS} = 2.168V$$

$$g_m = 1.501 \text{ mS}$$

$$g_m = k (V_{GS} - V_T)$$

Small signal midband:

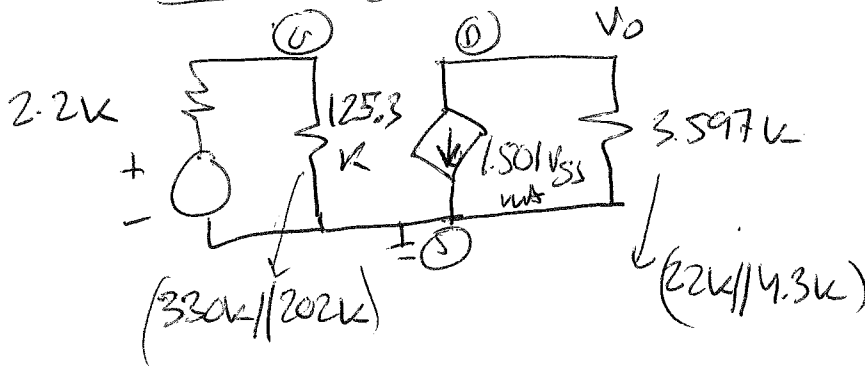

$$\frac{V_o}{V_{gs}} = -5.399$$


$$\frac{V_{gs}}{V_{sig}} = \frac{125.3}{125.3 + 2.2} = 0.9827$$

$$A_{mid} = -5.306$$

③ 12/5/2016  
Madhu

→ Upper cut-off frequency

W<sub>hi</sub> Input side:

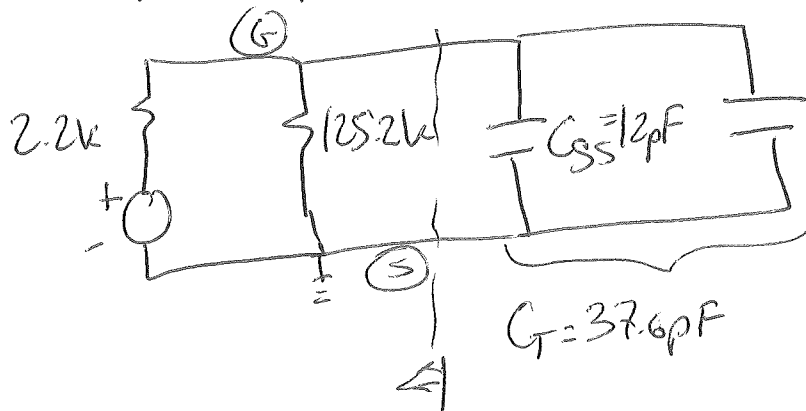

$$C_M = C_{gd}(1 + g_m R_{eq})$$

$$= 4pF(1 + 1.501ms \cdot 3.597k)$$


$$C_M = 4(1 + 5.399) = 25.6pF$$

$$C_T = 37.6pF$$

$$R_{TH} = 125.2k // 2.2k = 2.162k$$

$$\therefore W_{hi}(w) = \frac{1}{(2.162k)(37.6pF)} = 1.230 \times 10^7 \text{ 1/s}$$

W<sub>hi</sub> output side.

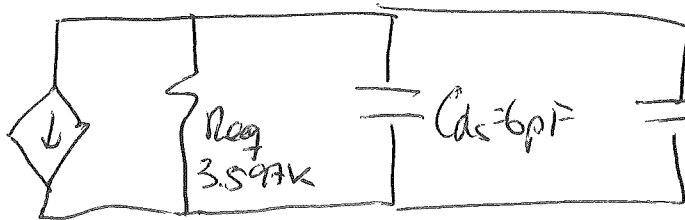

$$C'_M = C_{ds}(1 + \frac{1}{g_m R_{eq}})$$

$$C'_M = 4pF(1 + \frac{1}{5.399}) = 4.741pF$$

$$W_{hi}(w) = \frac{1}{(3.597 \times 10^3)(4.741 \times 10^{-12})} = 2.588 \times 10^7 \text{ 1/s}$$

No dominant pole


$$\left| \frac{(1.23 \times 10^7)(2.588 \times 10^7)}{(1.23 \times 10^7)(100 + 2.588 \times 10^7)} \right| = 0.707$$

→ to find 3dB pole.

$$\therefore W_{hi} = 1.044 \times 10^7 \text{ 1/s}$$

(P5)  $\rightarrow f_{co} = 30 \text{ Hz} \rightarrow \omega_{co} = 188.5 \text{ rad/s}$

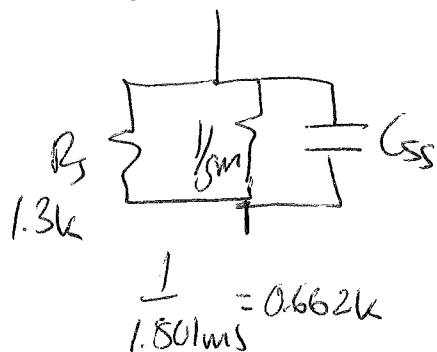Bypass capacitor  $C_{ss} \rightarrow \omega_p = 188.5 \text{ rad/s}$




$$\omega_p = 188.5 \text{ rad/s} = \frac{1}{(1.3 \text{ k} \parallel 0.662 \text{ k}) \cdot C_{ss}}$$

$$C_{ss} = \frac{1}{(188.5 \text{ rad/s})(0.4405 \times 10^3)} = 12.04 \mu\text{F}$$

$$\omega_z \text{ due to } C_{ss} = \frac{1}{R_s C_{ss}} = \frac{1}{(1.3 \times 10^3)(12.04 \times 10^{-6})} = 63.89 \text{ rad/s}$$

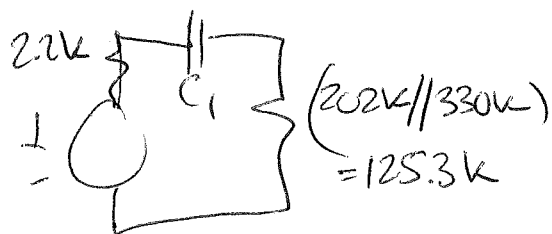$\rightarrow$  Want  $C_1$  to cancel that zero ( $\omega_z$  of  $C_{ss}$ )




$$\omega_{pc1} = \frac{1}{C_1 \cdot (127.5 \times 10^3 \Omega)} = 63.89 \text{ rad/s}$$

$$\therefore C_1 = \frac{1}{(63.89 \text{ rad/s})(127.5 \times 10^3 \Omega)}$$

$$C_1 = 122.8 \text{ nF}$$

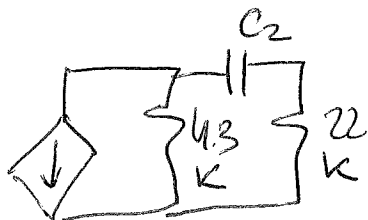$\rightarrow$  Make  $C_2$ 's pole at 0.1 rad/sec.  $= 3 \text{ Hz}$   $\omega_{pc2} = 6 \text{ rad/s}$




$$\omega_{pc2} = \frac{1}{C_2 \cdot (26.3 \text{ k})} = 6 \text{ rad/s}$$

$$C_2 = \frac{1}{(26.3 \text{ k})(6 \text{ rad/s})} = 2.07 \mu\text{F}$$

12/7/2016

Madhu

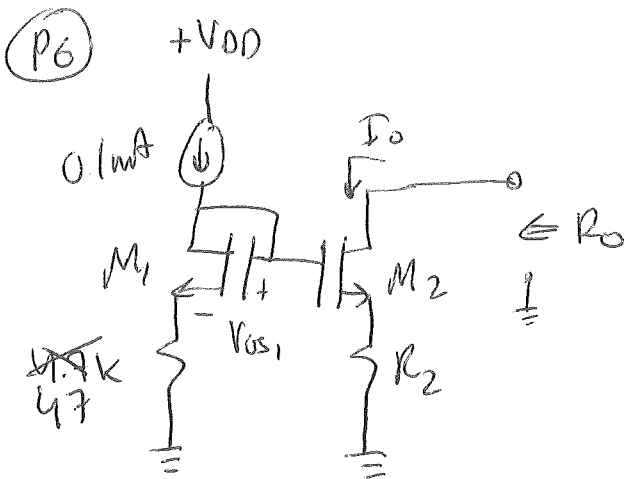

$$\mu_n C_{ox} = 0.092 \text{ mA/V}^2$$

$$|V_T| = 0.9 \text{ V}$$

$$\frac{W}{L} = 62.5, \lambda = 0.025 \text{ V}^{-1} \text{ (for both)}$$

- (a) Find  $R_2$  to make  $I_O = 0.05 \text{ mA}$   
 (b) Find output resistance  $R_o$ .

$$(a) I_{D1} = 1 \text{ mA} = \frac{1}{2} (0.092 \text{ mA/V}^2) (62.5) \cdot \underbrace{(V_{GS1} - V_T)^2}_{V_{OV}^2}$$

$$V_{OV1} = 0.186$$

$$V_{GS1} = 1.086 \text{ V}$$

$$V_{G1} = (47 \text{ k}\Omega)(0.1 \text{ mA}) + 1.086 \text{ V} = 5.786 \text{ V}$$

$$\text{Also } V_{G2} = 5.786 \text{ V}$$

$$\text{For } I_{D2} = 0.05 \text{ mA} = \frac{1}{2} (0.092 \text{ mA/V}^2) (62.5) (V_{OV})^2$$

$$V_{OV2} = \cancel{0.186} 0.132$$

$$V_{GS2} = 1.032 \text{ V}$$

$$\therefore V_{GS2} = V_{G2} - V_{S2}$$

$$1.032 \text{ V} = 5.786 - V_{S2}$$

$$V_{S2} = 4.754 = R_2 \cdot (0.05)$$

$$R_2 = 95.08 \text{ k}\Omega$$

$$\text{OR: } 1.032 = 5.786 - R_2 \cdot (0.05)$$

$$R_2 = 95.08 \text{ k}\Omega$$

b) Find output resistance  $R_o$ :

$$\frac{1.086 - 0.9}{r} = 0.186$$

Draw small signal circuit, need  $g_{m1} = 0.092 \times 62.5 (V_{ov1})$


$$g_{m1} = 1.07 \text{ mS}$$

$$\text{and } g_{m2} = 0.092 \times 62.5 (V_{ov2})^{0.132}$$

$$g_{m2} = 0.759 \text{ mS}$$

$$\text{and } r_{o2} = \frac{1}{\lambda \cdot I_{D2}} = \frac{1}{0.025 \times 0.05}$$

$$r_{o2} = 800 \text{ k}\Omega$$

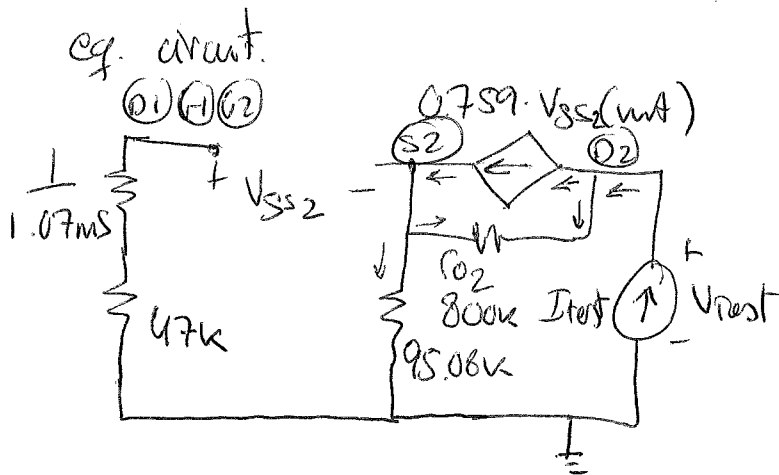

$$V_{gs2} = -V_{s2} \text{ since } V_{s2} = 0 \text{ V (no current flowing)}$$

$$\text{Node } S_2: \frac{V_{s2}}{95.08 \text{ k}} + \frac{V_{s2} - V_{test}}{800 \text{ k}} = 0.759(-V_{s2})$$

$$0.77076 V_{s2} - 1.25 \times 10^{-3} V_{test} = 0 \rightarrow (1)$$

$$\text{Node } D_2: \frac{V_{test} - V_{s2}}{800} = I_{test} - 0.759(-V_{s2})$$

$$-0.76025 V_{s2} + 1.25 \times 10^{-3} V_{test} = I_T$$

$$\text{set } I_T = 1 \text{ mA}$$

$$-0.76025 V_{s2} + 1.25 \times 10^{-3} V_{test} = 1 \text{ mA} \rightarrow (2)$$


$$V_{s2} = 95.15 \text{ V}$$

$$V_{test} = 5.867 \times 10^4$$

$$\therefore R_o = \frac{5.867 \times 10^4}{1 \times 10^{-3}} = 58.67 \text{ M}\Omega$$



12/7/2016 (2)

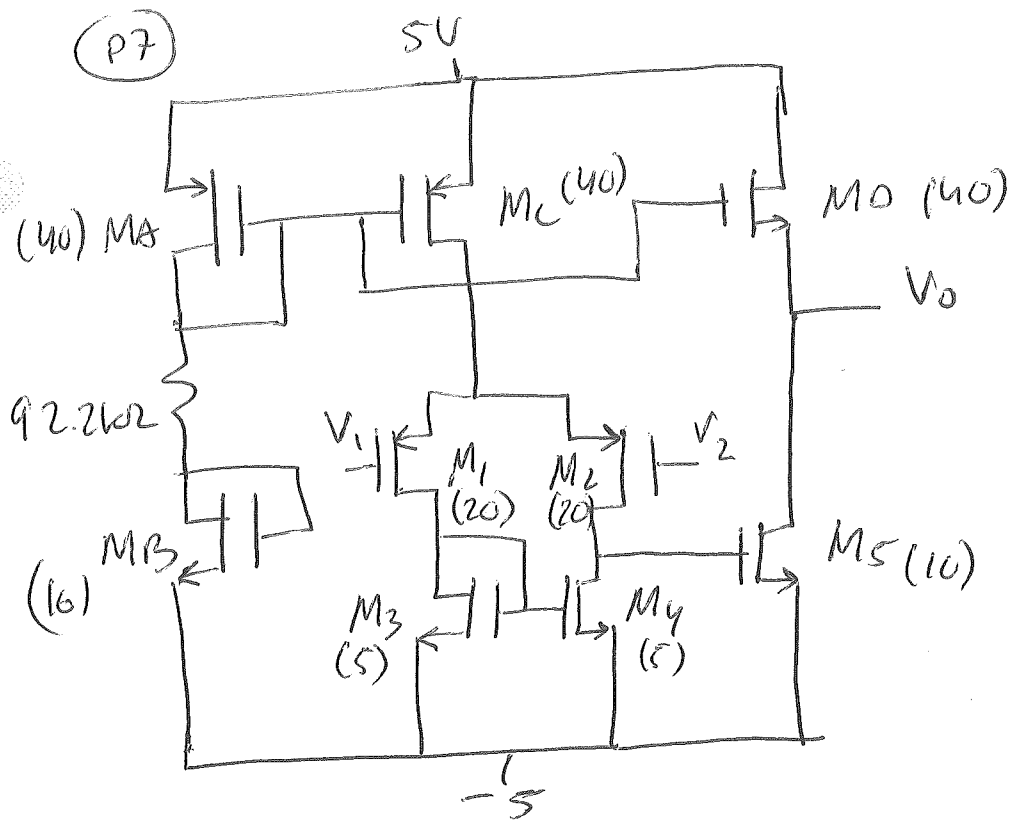

$$K_A = 0.064 \times 40 = 2.56 \text{ mA/V}^2$$

$$K_B = 0.16 \times 16 = 2.56 \text{ mA/V}^2$$

$$\therefore V_{SGA} = V_{SGB}$$

$$5 - V_{SGA} - 92.2k \left( \frac{1}{2} \right) (2.56) (V_{SGA} - 0.7)^2 - V_{SGA} = -5$$