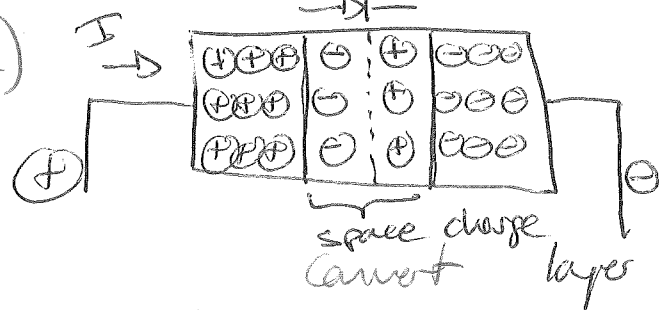


Chapter 4 - Diodes

lec 3 ↑
lec 4 ↓

→ Simplest and most fundamental nonlinear circuit element.

→ Two terminals. (just like a)



(1) Ideal diode


(2) Silicon junction diode.

→ Applications ~~① rectifying circuits (ac to dc)~~


Most common application is in rectifier circuits which convert ac to dc.

4.1.1 Current-voltage characteristics of the ideal diode.

~~Idea~~ Symbol

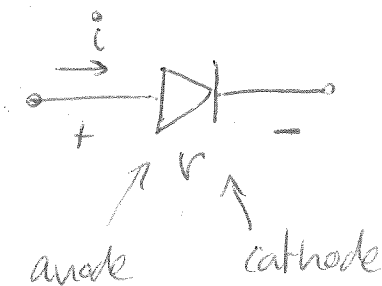

Ideal diode i-v characteristics

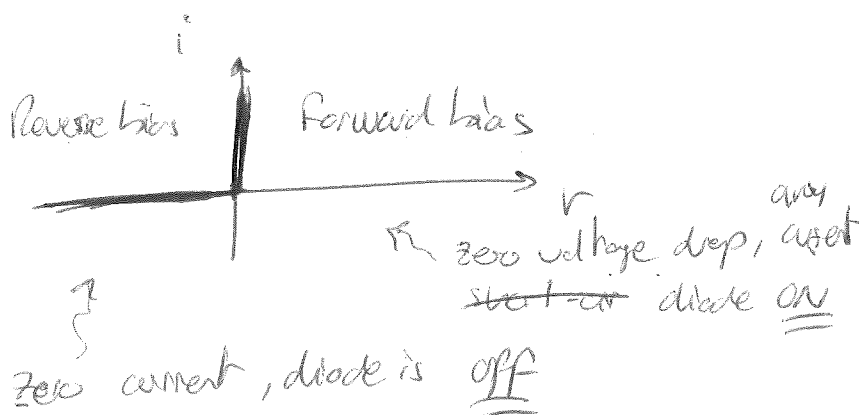




→ ~~External circuit needed to limit forward bias current and reverse bias voltage.~~

$$V < 0 \Rightarrow i = 0$$








$$V = 0 \Rightarrow i > 0$$

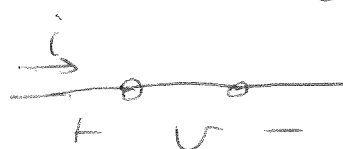

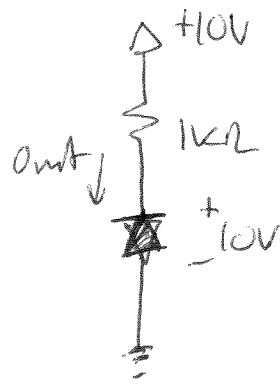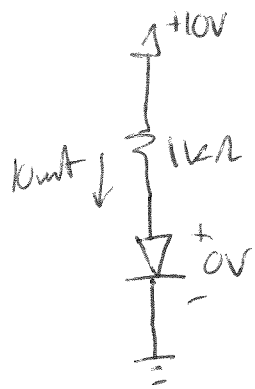

↑ External circuit need to limit forward bias current and to set reverse bias voltage.

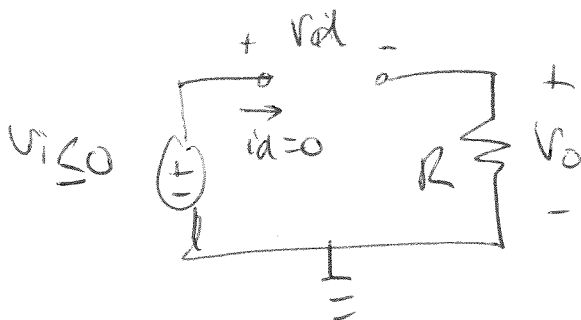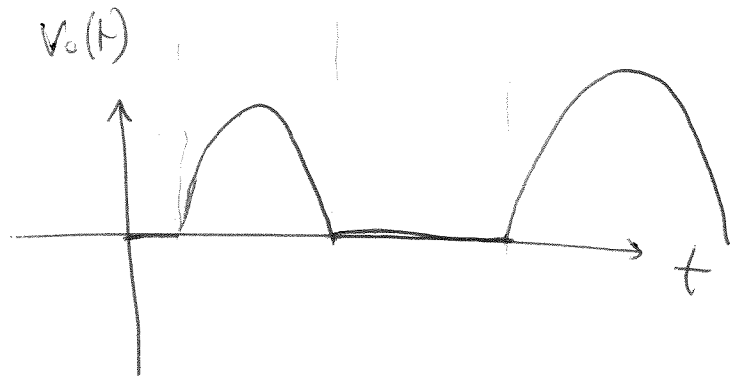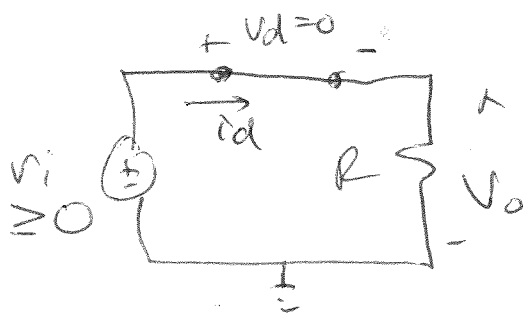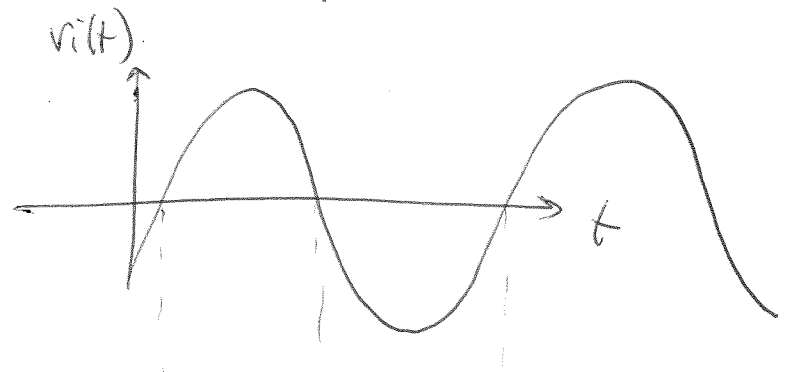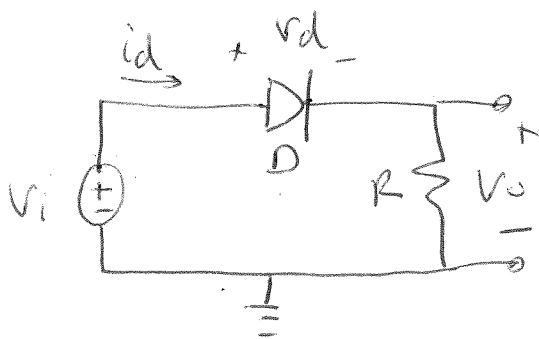
4.12. A simple application: The rectifier circuit.



4.1.3 Diode logic gates:

6


OR function

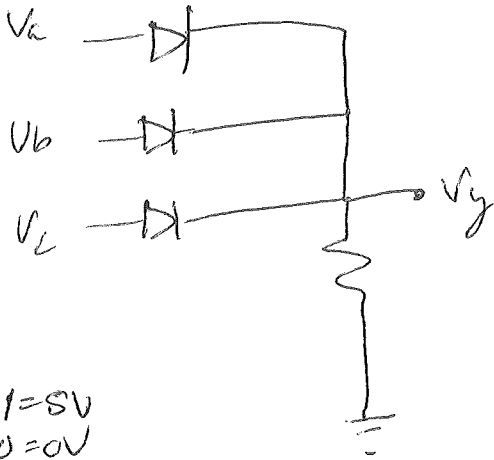

V_a	V_b	V_c	V_y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$Y = A + B + C$$

AND function

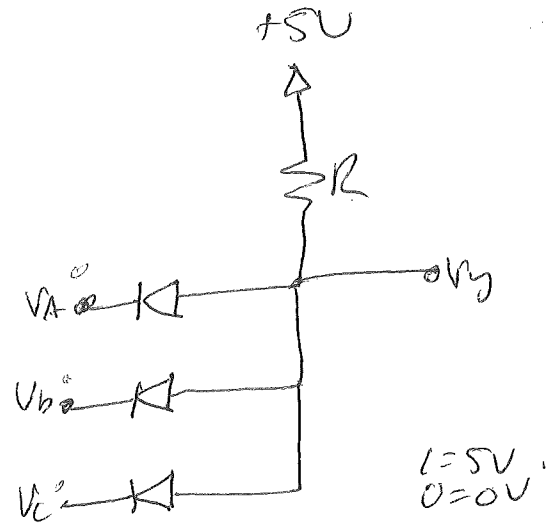


V_a	V_b	V_c	V_y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$Y = A \cdot B \cdot C$$

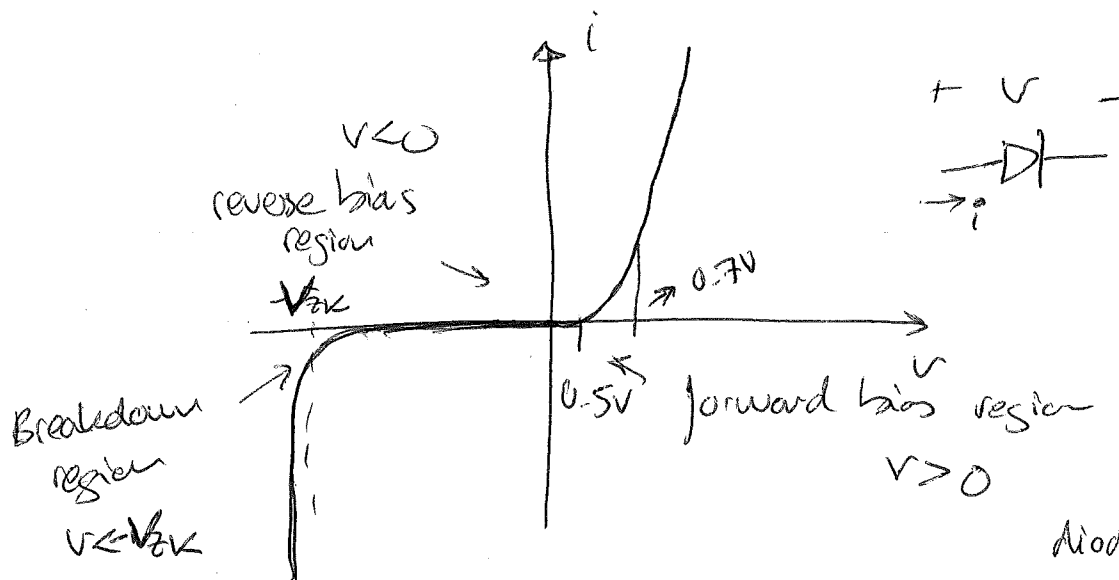4.2 - Terminal characteristic of junction diodes

i-v characteristics of a silicon junction diode:



Diode ideality factor
 $n=1$ for silicon

4.2.1 Forward-bias region.

$$v > 0 \quad i = I_S (e^{\frac{v}{nV_T}} - 1) \quad i \approx I_S (e^{\frac{v}{nV_T}})$$

I_S - constant at a given temp. for a given diode.
→ called saturation or scaled current.

$$I_S = A \cdot q \cdot n_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$$

$$(10^{-18} \text{ to } 10^{-12} \text{ A})$$

$\sim 10^{-15}$ for small signal diodes.

V_T - Thermal voltage

$$V_T = \frac{kT}{q}$$

k - Boltzmann's constant = $8.62 \times 10^{-5} \text{ eV/K}$

T - absolute temp (Kelvin) = $1.38 \times 10^{-23} \text{ J/K}$

q → electronic charge = $1.6 \times 10^{-19} \text{ coulomb}$

cont's →

of output

7

(at 20°C)

$V_T = 25.3 \text{ mV} \rightarrow$ use 25 mV at Room Temperature for quick analysis.

\rightarrow For $i \gg I_S$

$$i \approx I_S e^{v/V_T}$$


and
$$v = V_T \ln \frac{i}{I_S}$$

\rightarrow slope of 60 mV/decade of current at $i \gg I_S$

\rightarrow Current is negligible for $v < 0.5 \text{ V}$.

\rightarrow TURN-ON voltage of diode $\sim 0.7 \text{ V}$.

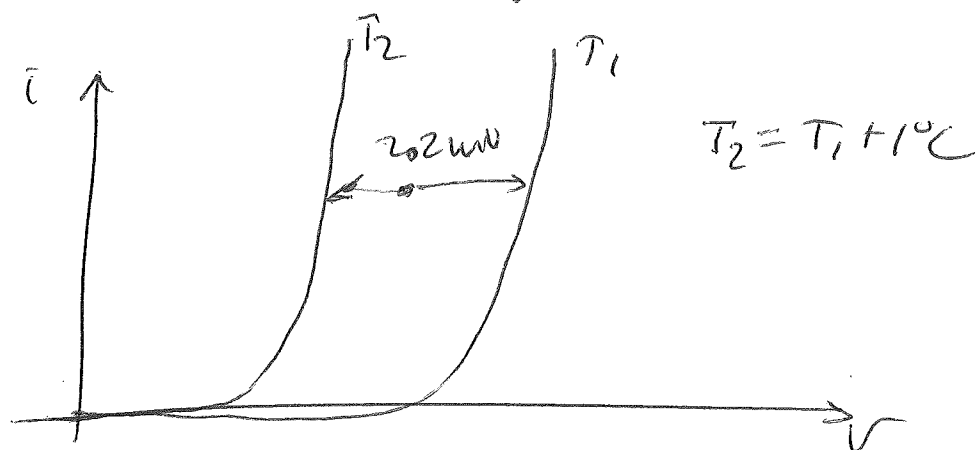\rightarrow At a constant current, the voltage drop across the diode decreases by $\sim 2.2 \text{ mV}$ for every 1°C increase in temperature. ($-2.2 \text{ mV}/^\circ\text{C}$)



$\frac{I_{CU}}{I_{CS}} \uparrow$
 $\frac{I_{CU}}{I_{CS}} \downarrow$

4.22 - The reverse bias region.

Wenn $v < 0$

$$i = I_S (e^{v/V_T} - 1)$$

$$\rightarrow (\cong - I_S)$$

Current in reverse is constant and equal to I_s .

→ directions

(reason to call it saturation current).

→ Real diodes $i(v=0)$ is larger and proportional to diode area.

→ Leakage current.

→ Leakage current doubles for every 10°C rise in temp.

4.2.3 Breakdown region

$\rightarrow V < -V_{ZK}$
 $Z \rightarrow \text{Zener}$
 $K \rightarrow \text{Knee}$
 $(\text{Zener-Knee voltage})$

→ Diode breakdown can be non-destructive if current limiting circuitry is used. (current limit in datasheet).


→ Used as voltage regulation circuits

4.3 - Modeling the diode forward characteristics.

- (1) Exponential model
- (2) Ideal diode model
- (3) ... (others)

4.3.1 Exponential model

Most accurate but most difficult to use.

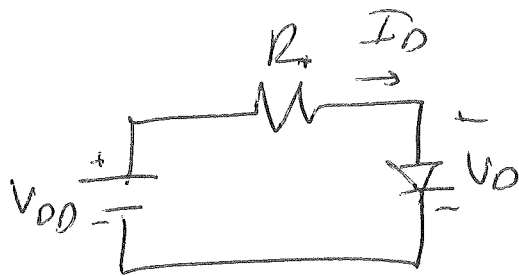

Assume $V_{DD} > 0.5$

$$\therefore i \gg I_S$$

$$I_D = I_S e^{V_D/V_T} \quad (1)$$

Also, KVL

$$-V_{DD} + I_D R + V_D = 0$$

$$I_D R = V_{DD} - V_D$$

$$I_D = \frac{V_{DD} - V_D}{R} \quad (2)$$

→ 2 equations / 2 unknowns (I_D, V_D)
if I_S is known ($V_T = 25 \text{ mV}$)


~~ex. $V_{DD} = 5\text{V}$ $R = 1\text{k}\Omega$ and find I_D at 0.7V .~~

→ If I_S is unknown → iterative solution.

h.3.2 ~~Iterative~~ ~~Graphical~~ analysis using exponential model.

~~If I_S is unknown~~

Plotting equations ① and ②.

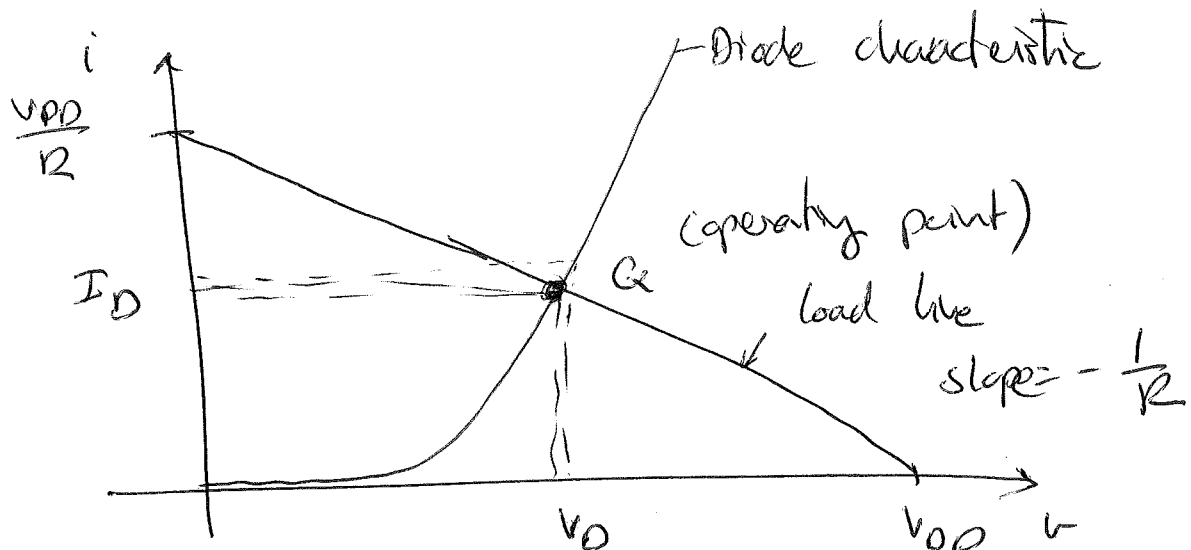

h.3.3 Iterative analysis using exponential model.

Determine I_D and V_D with $V_{DD} = 5V$, $R = 1k\Omega$
 Start by ~~And~~ assuming diode has limit of current at $0.7V$.

$$\rightarrow I_D = \frac{V_{DD} - V_D}{R} = \frac{5 - 0.7}{1k\Omega} = 4.3 \text{ mA}$$

\rightarrow Diode equation for better estimate of V_D .

$$I_2 = I_S e^{V_2/V_T}$$

$$I_2 = I_S e^{V_2/V_T}$$


$$\frac{I_2}{I_1} = e^{(V_2 - V_1)/V_T}$$

$$V_2 - V_1 = V_T \ln \frac{I_2}{I_1}$$

$$\therefore V_D = V_1 + V_T \ln \frac{I_2}{I_1}, \quad V_1 = 0.7V, \quad V_T = 25 \text{ mV}, \quad I_2 = 4 \text{ A}, \quad I_1 = 1 \text{ mA}$$

$$V_D = 0.733V$$

\rightarrow cont'd

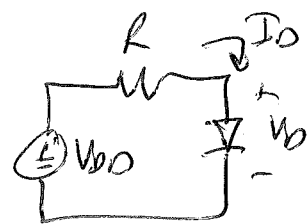

60 cents

(9)

Second iteration.

$$I_D = \frac{5 - 0.738}{1k\Omega} = 4.262 \text{ mA}$$

$$V_D = 0.738 + 26 \text{ mV} \cdot \ln\left(\frac{4.262}{4.3}\right)$$



$$V_D = 0.738 \text{ V (same as before)}$$

$$\therefore \text{Ans. } I_D = 4.262 \text{ mA}, V_D = 0.738 \text{ V}$$

4.3.5 - The constant voltage drop method

Simplest and most widely used.

Assume $V_D = 0.7 \text{ V}$ when ON.

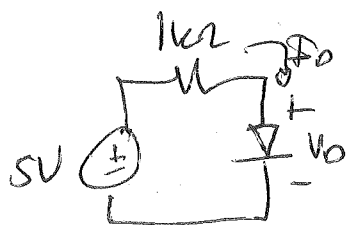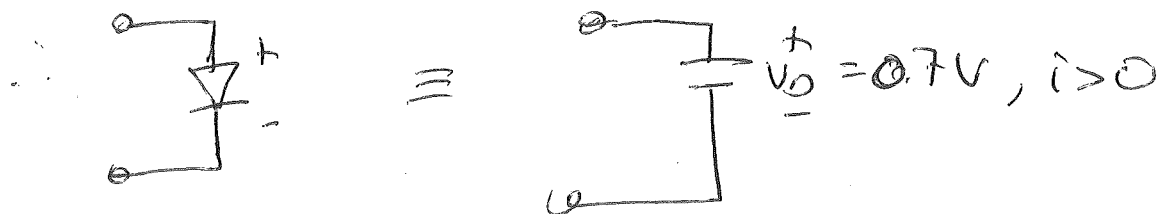

$$I_D = \frac{5 \text{ V} - 0.7 \text{ V}}{1k\Omega} = 4.3 \text{ mA (close enough)}$$


4.3.6 - Ideal-Diode Model

→ $V_D = 0 \text{ V}$, when V_{DD} is large.


$$I_D = \frac{5 - 0 \text{ V}}{1k\Omega} = 5 \text{ mA}$$

→ Also help w/ rapid analysis to determine when diode is ON or OFF.

4.3.7 The small-signal model

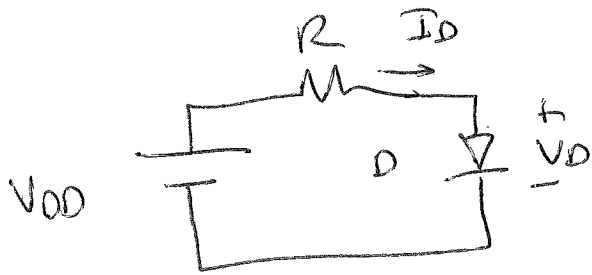


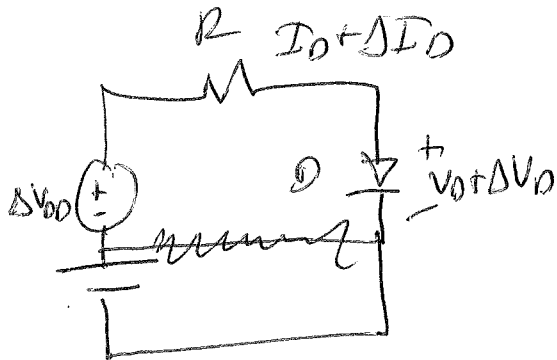- Consider DC voltage V_{DD} and current I_D .
 $\rightarrow I_D$ and V_D can be found using exponential or constant voltage drop model.



- V_{DD} undergoes a small change ΔV_{DD}
 I_D changes by ΔI_D and V_D by ΔV_D
 \rightarrow Need quick way to determine incremental values Δ .
 \rightarrow Small-signal model for the diode.

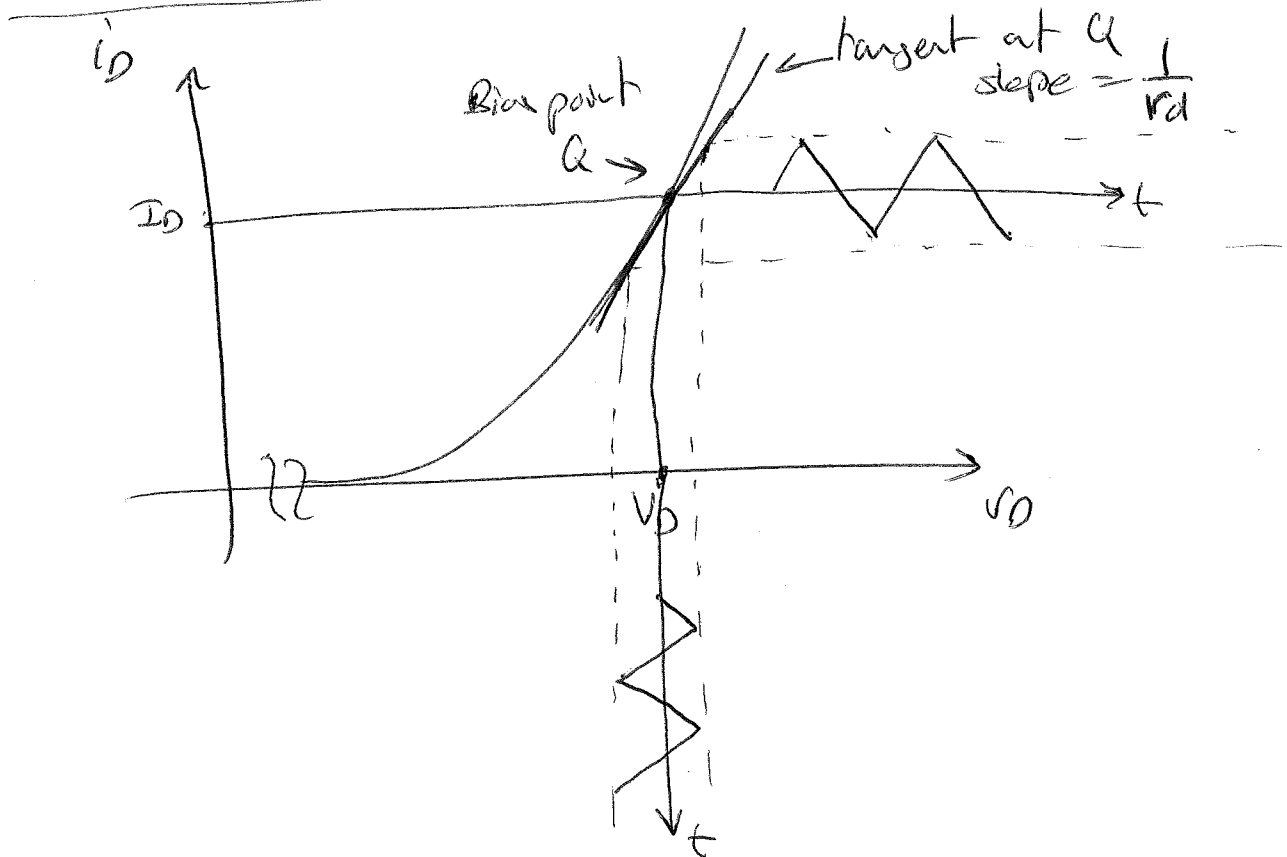- $\rightarrow \Delta V_{DD}$ can be time-varying
- \rightarrow small so ΔV_D is kept sufficiently small.



8/31/2016 (10)

Voltage across diode:

$$v_D(t) = V_D + v_d(t)$$

$$i_D(t) = I_S e^{v_D/V_T}$$

$$i_D(t) = I_S e^{(V_D + v_d(t))/V_T}$$

or

$$i_D(t) = I_S e^{V_D/V_T} e^{v_d/V_T}$$

no small signal $\rightarrow i_D(t) = I_S e^{V_D/V_T} = I_D$ (DC current)

$$\therefore i_D(t) = I_D e^{v_d/V_T}$$

If amplitude of $v_d(t)$ is small.

$$\frac{v_d}{V_T} \ll 1$$

Then, series expansion approximation of exponent:

$$i_D(t) \approx I_D \left(1 + \frac{v_d}{V_T} \right)$$

→ Small-signal approximation for signals with amplitudes smaller than 5mV ($V_T = 25\text{mV}$)

Then: $i_D = I_D + i_d$ $i_D(t) = I_D + \frac{I_D}{V_T} v_d$

$$i_D = I_D + i_d$$

\swarrow DC current \swarrow small signal current


$$i_d = \frac{I_D}{V_T} v_d$$

→ $\frac{I_D}{V_T}$ is diode small-signal conductance

Also diode small-signal resistance
or incremental resistance $r_d = \frac{V_T}{I_D}$


Small signal analysis is done independently of
DC analysis by short-circuiting DC voltage sources
and open-circuiting current sources and replacing

the diode by its small-signal resistance

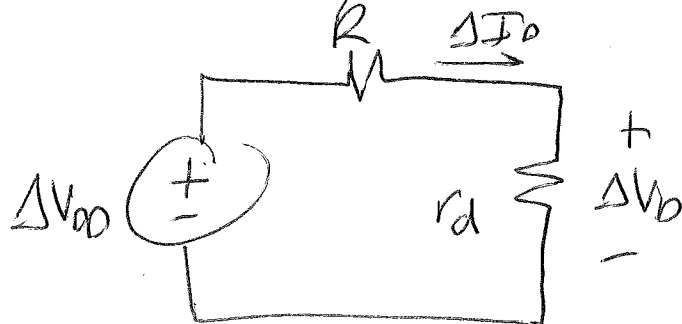

$$r_d = \frac{V_T}{I_D}$$

ex. 4.5

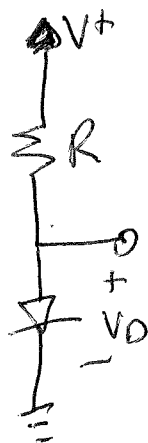

$$R = 10k\Omega$$

$V_{in} = 10V$ DC + 60Hz sinusoid of 1-V peak.

→ Calculate DC voltage of diode
and amplitude of the sine-wave
signal appearing across it.

Assume diode has a 0.7V drop
at 1-mA current.



$$I_D = \frac{10 - 0.7}{10k\Omega} = 0.93mA$$

(near 1-mA assumed current)

$$r_d = \frac{V_T}{I_D} = \frac{25mV}{0.93mA} = 26.9\Omega$$

(diode incremental resistance)


→ cont'd

↑ cont'd

8/31/2016

(11)

Small signal model:

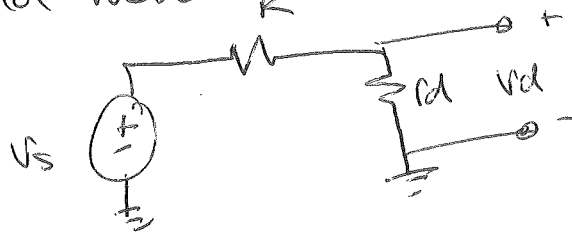

For 1V sine wave.

$$v_d(\text{peak}) = \hat{V}_s \frac{r_d}{R + r_d} = 1V \cdot \frac{26.9\Omega}{10k + 26.9\Omega}$$

$$v_d(\text{peak}) = 2.68\text{mV} \quad \leftarrow \text{2.68mV} < 5\text{mV}$$


RES ↑
REG ↓

4.3.3 Diode forward drop in voltage regulation.

Provide constant DC voltage between output terminals.
in spite of $\left\{ \begin{array}{l} \text{a) changes in load current at output.} \\ \text{b) changes in DC power supply} \end{array} \right.$
Diode remains at ~0.7V for large changes in current.
In previous example a 10V-dc w/ 2V peak-to-peak
±1V (±10%)

only ±2.7mV seen on diode.
(±0.4%)

ex. 10±1V

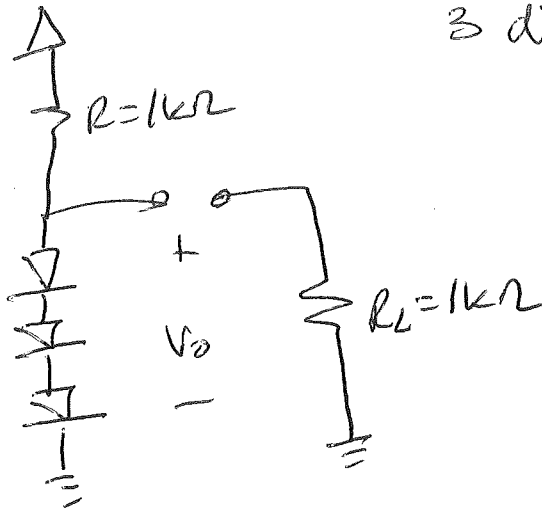

3 diodes ≈ 2.1V constant.

? a) ±10% voltage source.


$$I = \frac{10 - 2.1}{1k\Omega} = 7.9\text{mA}$$

$$r_d = \frac{V_T}{I} = \frac{25\text{mV}}{7.9\text{mA}} = 3.2\Omega$$

$$\therefore r = 3 \times 3.2 = 9.6\Omega \quad (\text{total } r_d \text{ diodes})$$

$$\Delta v_o = 2 \cdot \frac{r}{r + R} = 2 \cdot \frac{9.6}{9.6 + 10k} = 19\mu\text{V}$$

peak-to-peak
1% total → ±0.5%

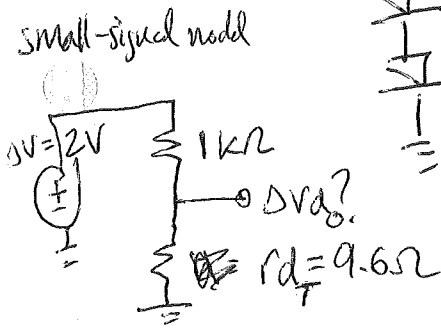


b) load resistor of $1k\Omega$ connected.

$$I_L = \frac{2.1V}{1k\Omega} = 2.1mA$$

$$\Delta V_o = 9.6\Omega (-2.1mA) = -20mV$$

$$r_{d1} \cdot (\Delta I)$$

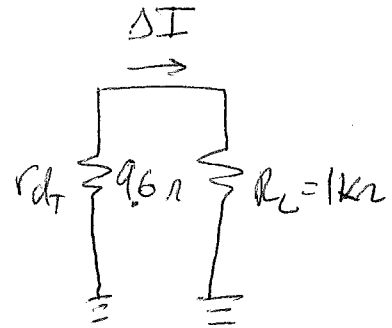


This implies that voltage across each diode decreases by $\sim 6.7mV \rightarrow$ small-signal model may not be entirely justified but is a good approximation. Detailed analysis yields $\Delta V_o = -23mV$.

Ex 3 detailed:

Calculate percentage change of regulated voltage V_o caused by

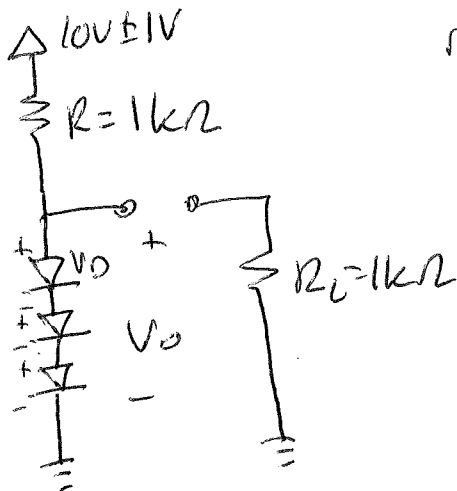- a $\pm 10\%$ change in power supply
- connecting a $1k\Omega$ load resistor



a) KVL w/ diodes. $3V_o = V_o = 2.1V$

$$-V_{SS} + IR + 3V_o = 0$$

$$IR = V_{SS} - 3V_o$$

$$I = \frac{V_{SS} - 3V_o}{R}$$

$$I_o = \frac{10 - 2.1}{1k\Omega} = 7.9mA$$


$$r_d = \frac{25mV}{7.9mA} = \frac{V_T}{I_D} = 3.2\Omega$$

$$3r_d = 9.6\Omega$$

$$V_{app} = 2V_{pp} \frac{9.6\Omega}{9.6\Omega + 10k\Omega}$$

$$V_{app} = 19mV \text{ or } \pm 0.5\%$$

DC analysis

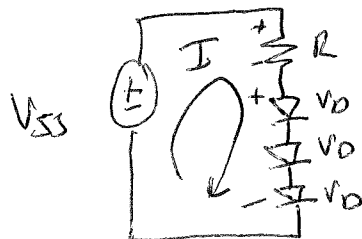


Small signal.

turn off DC source

keep small signal sources, replace diode with r_d



b)

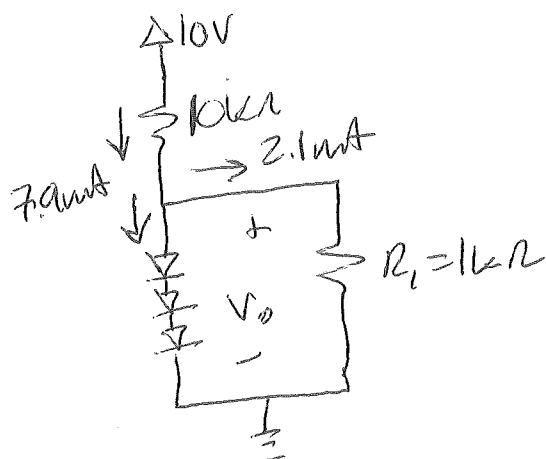

$$\Delta I = -2.0 \text{ mA}$$

$$\therefore \Delta V_o = \Delta I \cdot 96 \Omega$$

$$\Delta V_o = (-2.0 \text{ mA})(96 \Omega)$$

$$\boxed{\Delta V_o = -20 \text{ mV}}$$

4.13 Find the value of the diode ~~signal~~ small-signal resistance r_d at bias currents of 0.1mA, 1mA and 10mA.

$$r_d = \frac{\Delta V}{\Delta I}$$

$$r_{d1} = \frac{25 \text{ mV}}{0.1 \text{ mA}} = 250 \Omega$$

$$r_{d2} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

$$r_{d3} = \frac{25 \text{ mV}}{10 \text{ mA}} = 2.5 \Omega$$

4.14 Consider a diode biased at 1mA. Find the change in current as a result of changing the voltage by (a) -10mV, (b) -5mV, (c) +5mV and (d) +10mV. In each case, do the calculations (i) using small-signal model and (ii) exponential model.

4.14 (ans)

For small-signal model $\Delta i_D = \frac{\Delta v_d}{r_d} \rightarrow (1)$ $r_d = \frac{V_T}{I_D}$

exponential model $i_D = I_S e^{v_D/V_T}$

Need Δi_D } and $i_{D1} = I_S e^{v_1/V_T}$
 not knowing I_S } then $\rightarrow i_{D2} = I_S e^{v_2/V_T}$
 $\frac{i_{D2}}{i_{D1}} = \frac{I_S e^{v_2/V_T}}{I_S e^{v_1/V_T}} = e^{(v_2 - v_1)/V_T}$

$$\Delta v_d = v_2 - v_1$$

$$\frac{i_{D2}}{i_{D1}} = e^{\Delta v_d/V_T}$$

$$\text{and } i_{D2} = i_{D1} e^{\Delta v_d/V_T}$$

$$\Delta i_D = i_{D2} - i_{D1} = i_{D1} e^{\Delta v_d/V_T} - i_{D1} = i_{D1} (e^{\Delta v_d/V_T} - 1) \quad (2)$$

\rightarrow knowing $I_D = 1 \text{ mA}$, $V_T = 25 \text{ mV}$ and eq. (1) + (2)
 $i_{D1} = 1 \text{ mA} \rightarrow r_d = 25 \Omega$

$\Delta v_d (\text{mV})$	$\Delta i_D (\text{mA})$ small-signal	$\Delta i_D (\text{mA})$ exponential
-10 mV	-0.4 mA	-0.491 mA -0.329 mA
-5 mV	-0.2 mA	-0.245 mA -0.181 mA
+5 mV	+0.2 mA	0.221 mA
+10 mV	+0.4 mA	0.491 mA


$$\Delta i_D = 1 \times 10^{-3} \left(e^{\frac{-10 \times 10^{-3}}{25 \times 10^{-3}}} - 1 \right)$$

$$\Delta i_D = 1 \times 10^{-3} (670.3 \times 10^{-3} - 1) = 1 \times 10^{-3} (-329.6 \times 10^{-3})$$

$$= -329.67 \times 10^{-6} \text{ A}$$

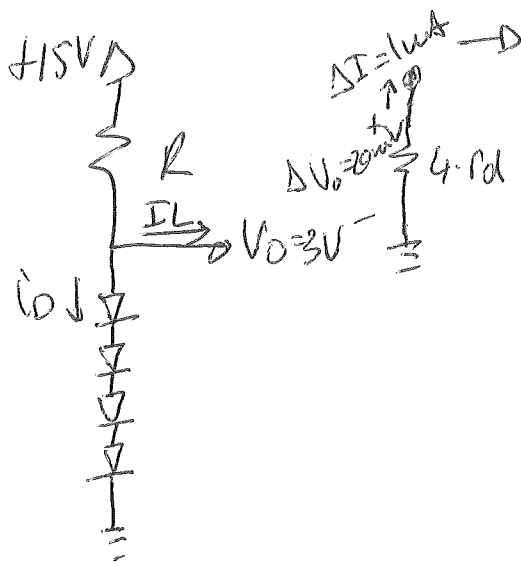Q4.15 - Design circuit so that $V_o = 3V$ when

$I_L = 0$ and V_o changes by 20mV per 1mA of load current.



$\Delta V_o = 20\text{mV}$ when $\Delta I = 1\text{mA}$

$$\therefore r_d = \frac{20\text{mV}}{1\text{mA}} = 20\Omega$$

4 diodes $r_d = \frac{20\Omega}{4} = 5\Omega$

And $r_d = \frac{V_T}{I_D} = \frac{25\text{mV}}{I_D} = 5\Omega$

$$I_D = 5\text{mA} =$$

$$I_D = \frac{15V - 3V}{R} = 5\text{mA} \quad \begin{matrix} \text{ice } 6 \uparrow \\ \text{ice } 7 \downarrow \end{matrix}$$

$$R = \frac{15 - 3}{5\text{mA}} = 2.4\text{k}\Omega$$

(b) Value of I_S of each diode.

$$i_D = I_S e^{V/V_T}$$

$$5\text{mA} = I_S e^{0.75/25\text{mV}}$$

$$I_S = \frac{5\text{mA}}{e^{0.75/25\text{mV}}} = 4.67 \times 10^{-16} \text{ Amps.}$$

$$V = \frac{3V}{4} = 0.75$$

HW#2

4, 2, 3, 16, 19, 41
56, 60, 61

ex: 4.66
(assign at end
of each diode leg.)

(c) Use diode exponential model to find change in V_o when current $I_L = 1\text{mA}$ is drawn from regulator.

$$i_D = 5\text{mA} - 1\text{mA} = 4\text{mA}$$

$$i_D = I_S e^{V/V_T} \rightarrow 4\text{mA} = 4.67 \times 10^{-16} \text{ A} \cdot e^{V/25\text{mV}}$$

$$V_o = V_T \ln\left(\frac{i_D}{I_S}\right)$$

$$e^{V/25\text{mV}} = \frac{4\text{mA}}{4.67 \times 10^{-16} \text{ A}}$$


$$V_o = 0.744V$$

$$V_o = 4 \times 0.744 = 2.977 - 25\text{mV}$$


$$\Delta V = 3 - 2.977 = 22.3\text{mV}$$

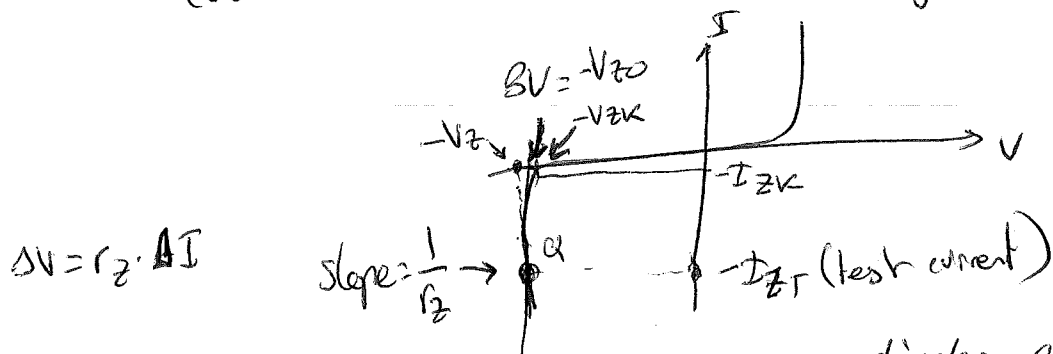4.4 - Operation in the reverse breakdown region - Zener diodes

→ Diodes operating in the breakdown region can be used in the design of voltage regulators.



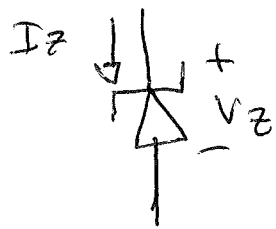→ Breakdown diodes or Zener diodes are designed to operate in BV condition.



Current flows into the cathode.

Cathode positive w.r.t. anode.

I_z and V_z have positive values.

→ Datasheet indicates V_z at certain I_{zt} .

Q-point → operating parameters.

(i.e.) $V_z = 6.8V$ Zener diode at $I_{zt} = 10mA$

→ Deviations from I_{zt} result in changes in V_z

$$\Delta V = r_z \Delta I$$


r_z → dynamic resistance of Zener diode (datasheet)

Avoid running w/ low current settings as r_z is larger.

zener diodes with voltages V_Z (few volts \rightarrow few hundred)
 spec sheet $\rightarrow V_Z$ (at I_{ZT}), r_z , I_{ZK} and max. power.

i.e. 0.5-W, 6.8-V zener diode
 $\rightarrow I_{max} = 70 \text{ mA}$

\rightarrow zener diode model:

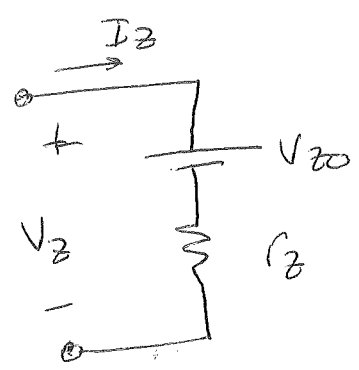


$V_{Z0} \rightarrow$ point where $1/r_z$ line intersects x -axis ($\sim V_{ZK}$)

$V_Z = V_{Z0} + I_Z r_z$ when $I_Z > I_{ZK}$, $V_Z > V_{Z0}$

4.4.2 zener diode as shunt regulator


\rightarrow Regulator circuit appears in parallel (shunt) with the load.

lec 71
lec 91

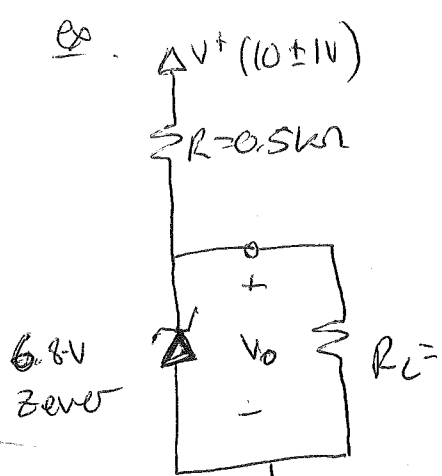

6.8-V zener $\rightarrow [V_Z = 6.8 \text{ V (at } I_Z = 5 \text{ mA)}]$
 $r_z = 20 \Omega$ and $I_{ZK} = 0.2 \text{ mA}$

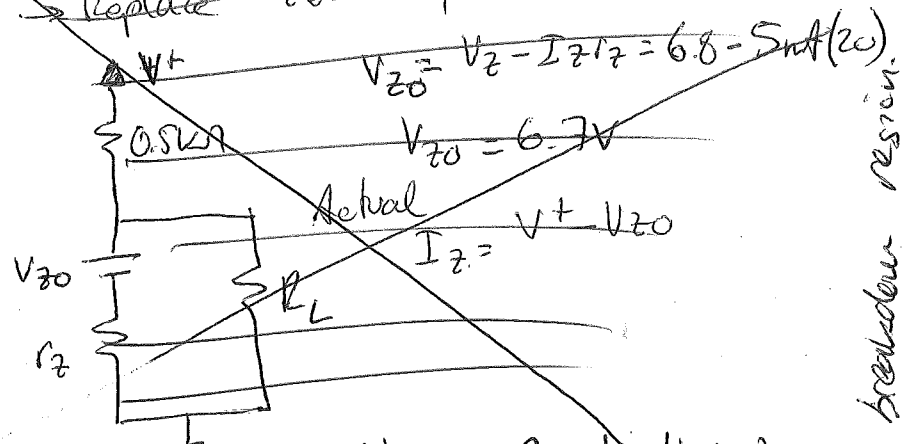- a) Find V_O with no load at $V^+ = 10 \text{ V}$
- b) ~~Find line~~ ~~Replace zener w/ model~~




- a) V_O w/ load
- b) line regulation $(\frac{\Delta V_O}{\Delta V^+}) [\frac{\text{mV}}{\text{V}}]$
- c) load regulation $(\frac{\Delta V_O}{\Delta I_L}) [\frac{\text{mV}}{\text{mA}}]$
- d) V_O w/ $R_L = 2 \text{ k}\Omega$

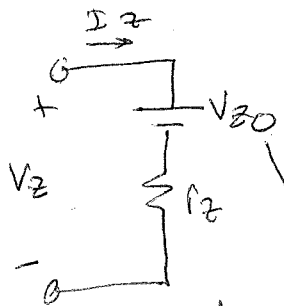e) V_O w/ $R_L = 0.5 \text{ k}\Omega$ f) Min. R_L for diode in reverse.

breakdown region.

→ First find actual V_{Z0} value for set current so that model can be used.



$$V_Z = V_{Z0} + r_z I_Z$$


$$V_{Z0} = 6.8V - (20\Omega)(5mA) = 6.7V$$

→ Then find V_0 with no load:

$$I = I_Z$$

$$-V^+ + IR + V_{Z0} + I r_z = 0$$

$$I(R + r_z) = V^+ - V_{Z0}$$

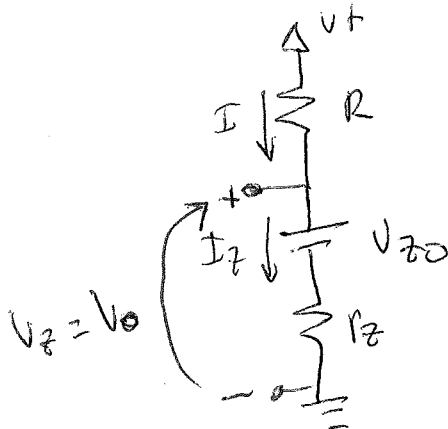


$$I = I_Z = \frac{V^+ - V_{Z0}}{R + r_z}$$

$$I = \frac{10 - 6.7}{0.5k\Omega + 20\Omega} = 6.35mA$$

thus: $V_Z = V_0 = V_{Z0} + I r_z = 6.7V + (6.35mA)(20\Omega) = 6.83V$

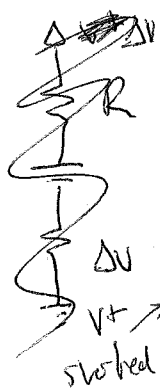b) For a $\pm 1V$ change in V^+ , find change in output voltage:




$$\Delta V_0 = \Delta V^+ \frac{r_z}{R + r_z} = \pm 1V \cdot \frac{20}{500 + 20} = \pm 38.5mV$$

∴ Line regulation = 38.5mV/V

$$\hookrightarrow \frac{\Delta V_0}{\Delta V^+} \left(\frac{mV}{V} \right)$$

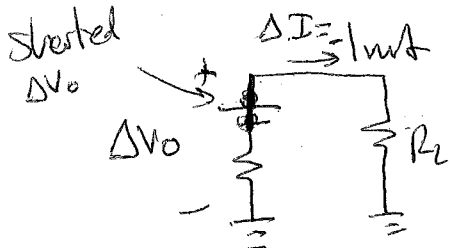c) Find change in V_0 resulting from connecting R_L that draws $I_L = 1mA$, and load regulation $\left(\frac{\Delta V_0}{\Delta I_L} \right)$



$$\Delta V_0 = (\Delta I) \cdot r_z$$

$$\Delta V_0 = (-1mA)(20\Omega) = -20mV$$

Load regulation = $\frac{\Delta V_0}{\Delta I_L} = -20mV/mA$

Assign HW #2: ✓ → Design

4.2, 3, 16, 19, 41, 56, 60, 61

extra 4.66 (Design problem)

9/7/2016

15

Qs (cont'd)

d) Find change in V_o when $R_L = 2k\Omega$

Load current becomes approx. $I_L \sim \frac{6.8V}{2k\Omega} = 3.4\mu A$


Zero current change $\Delta I_Z = -3.4\mu A$.

$$\therefore \Delta V_o = r_z \Delta I_Z = 20\Omega(-3.4\mu A) = -68mV$$

or from load regulation rule of c)

$$(-20mV/\mu A) \cdot (3.4\mu A) = -68mV$$

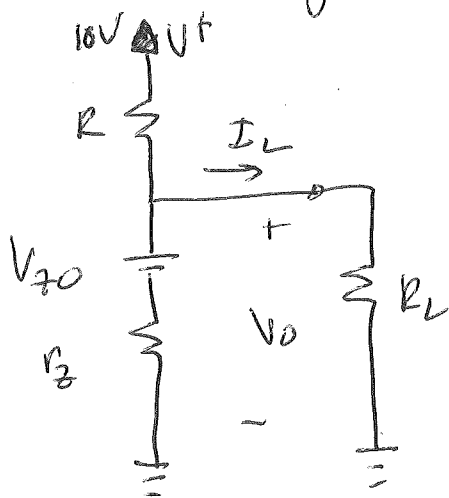e) Find value of V_o when $R_L = 0.5k\Omega$



$$I_L = \frac{6.8V}{0.5k\Omega} = 13.6\mu A$$


$$\text{but } I_Z = 6.8\mu A$$

\therefore Zener is cut off (no current flows through Zener diode).

→ new circuit.

$$V_o = 10 \cdot \frac{R}{R_L + R}$$
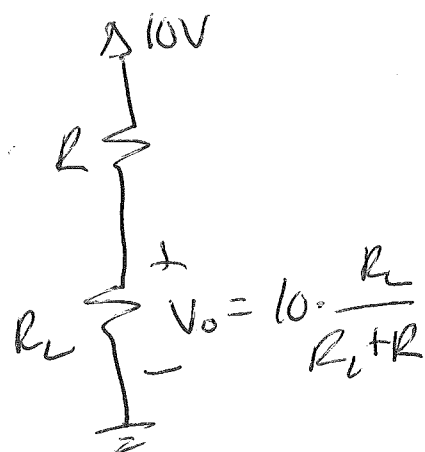
$$V_o = 10 \cdot \frac{0.5}{0.5 + 0.5} = 5V$$



Also checks that $V_o < V_{Z0}$

f) what is minimum value of R_L for which diode still operates in breakdown region.

At edge of Breakdown region / $I_Z = I_{ZK} = 0.2 \text{ mA}$
 $V_Z = V_{ZK} = 6.7 \text{ V} = V_{Z0}$

\therefore Current applied by R $I = \frac{10 - 6.7}{0.5 \text{ k}\Omega} = 4.6 \text{ mA}$

Since $I_Z = 0.2 \text{ mA}$, then $I_L = 4.6 - 0.2 = 4.4 \text{ mA}$


$$\therefore \boxed{R_L = \frac{6.7 \text{ V}}{4.4 \text{ mA}} \approx 1.5 \text{ k}\Omega}$$

lec 8.1

lec 9.5

9.5 - Rectifier circuits


Block diagram of a dc power supply

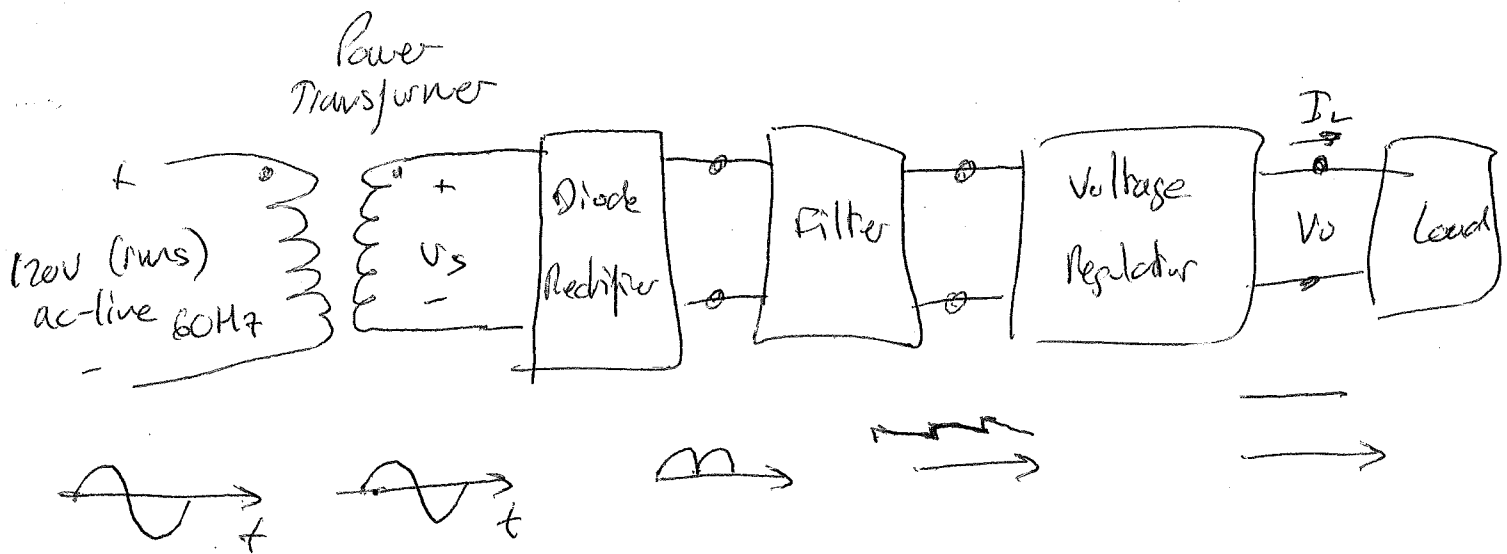

N-turns to step down voltage	Rectify signal	Filter signal	Regulate signal variation
	(1)	(2)	(3)


4.5.1 - The half-wave rectifier

9/7/2016
16

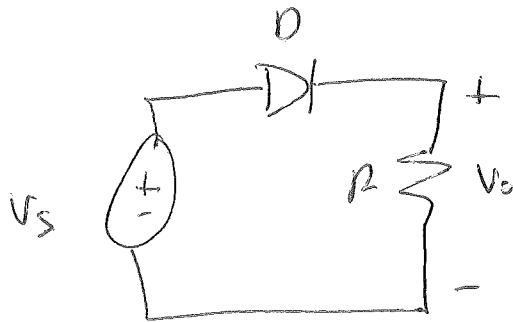

Constant-voltage drop model: V_D
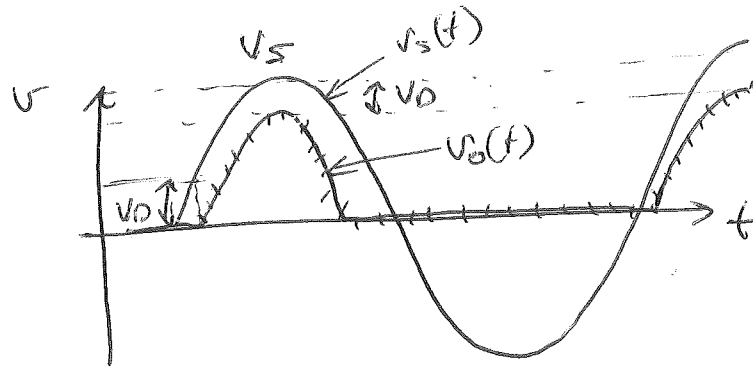
$$\begin{cases} v_o = 0 & v_s < V_D \\ v_o = v_s - V_D & v_s \geq V_D \end{cases}$$




Important: (i) current carrying rating of diode

(ii) Peak inverse voltage (PIV) capability of diode (i.e. $BV_{diode} > |V_s|$)

ex 4.19

(iii) Not appropriate for small V_s .

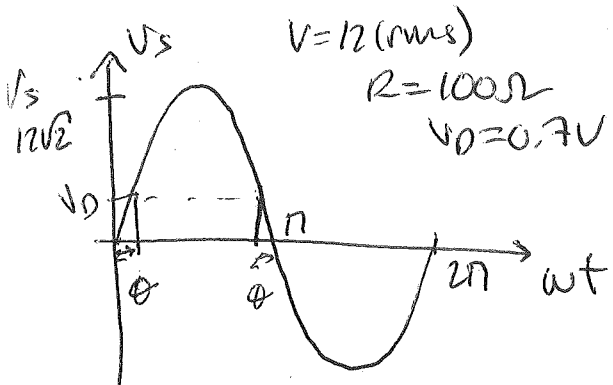

a) Diode starts conduction: $v_s = V_D = 0.7V$
 $v_s = V_s \sin \omega t$ $V_s = 12\sqrt{2}$ $\omega t = \theta$

$$V_s = 12\sqrt{2} \cdot \sin \theta = V_D = 0.7V$$

$$12\sqrt{2} \sin \theta = 0.7 \rightarrow \theta = \sin^{-1}\left(\frac{0.7}{12\sqrt{2}}\right) \approx 2.4^\circ$$

\therefore Conduction starts at 2.4° , ends at $(180 - \theta) = 177.6^\circ$

Total conduction angle = 175.2°


$$v_{o, avg} = \frac{1}{2\pi} \int_{\theta}^{\pi-\theta} (V_s \sin \phi - V_D) d\phi$$

$$= \frac{1}{2\pi} [-V_s \cos \phi - V_D \phi]_{\phi=\theta}^{\phi=\pi-\theta} = \frac{1}{2\pi} [-V_s \cos \theta - V_s \cos(\pi-\theta) - V_D(\pi-2\theta)]$$

$$\therefore v_{o, avg} = \frac{2V_s}{2\pi} - \frac{V_D}{2} = \frac{V_s}{\pi} - \frac{V_D}{2} = \frac{12\sqrt{2}}{\pi} - \frac{0.7}{2} = 5.05V$$

$$\begin{cases} \cos \theta \approx 1 \\ \cos(\pi - \theta) \approx -1 \\ \pi - 2\theta \approx \pi \end{cases}$$


4.5.2 - The full-wave rectifier.

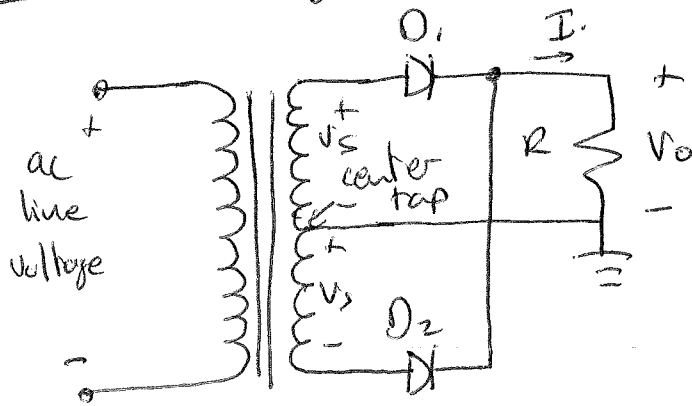

D_1 conducts during positive, + of cycle

D_2 conducts during negative part of cycle.

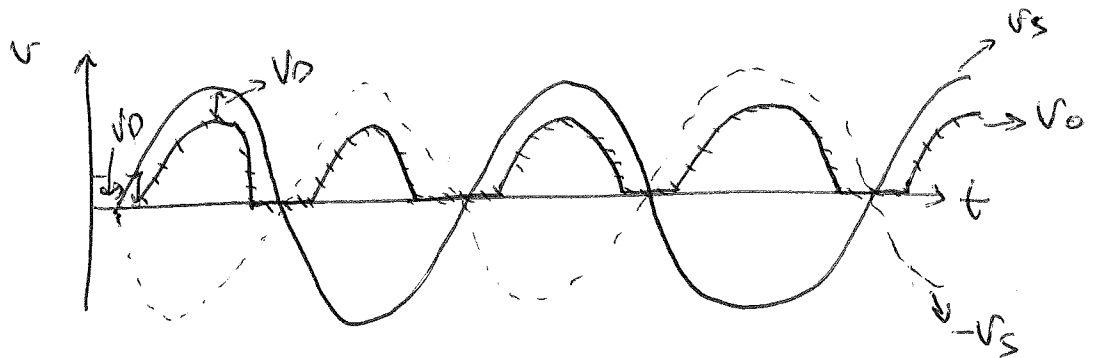Current I always flows in same direction.



$$PIV = 2V_s - V_0 \quad \text{approx. (twice that of half-wave circuit)}$$

Ex. 4.19 (cont'd) Half-wave rectifier example continued...


c) Peak current at peak diode voltage.

$$\therefore \hat{I}_D = \frac{V_s - V_D}{R} = \frac{12\sqrt{2} - 0.7}{100} = 163 \text{ mA}$$

$$PIV = V_s = 12\sqrt{2} = 17 \text{ V}$$

4.5.3 - The Bridge Rectifier

9/7/2016 (17)

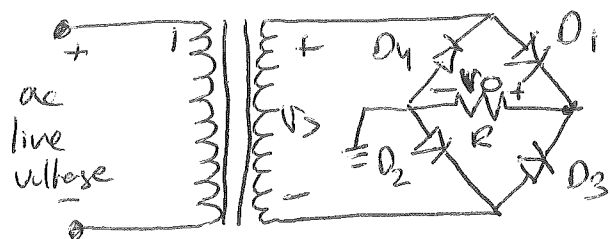

(From Wheatstone bridge similarity)

→ Does not require a center-tap.
(advantage over full-wave)

→ Diode bridge in single package.

→ Positive half-cycle: v_s is positive

→ current flows through D_1 , R and D_2 .


→ $D_1 + D_3 \rightarrow$ reversed biased

→ Negative half-cycle: v_s is negative [$(-v_s)$ is positive]

→ current flows thru D_3 , R and D_4

→ $D_1 \neq D_2 \rightarrow$ reversed.

→ Current flows in same direction during both cycles.

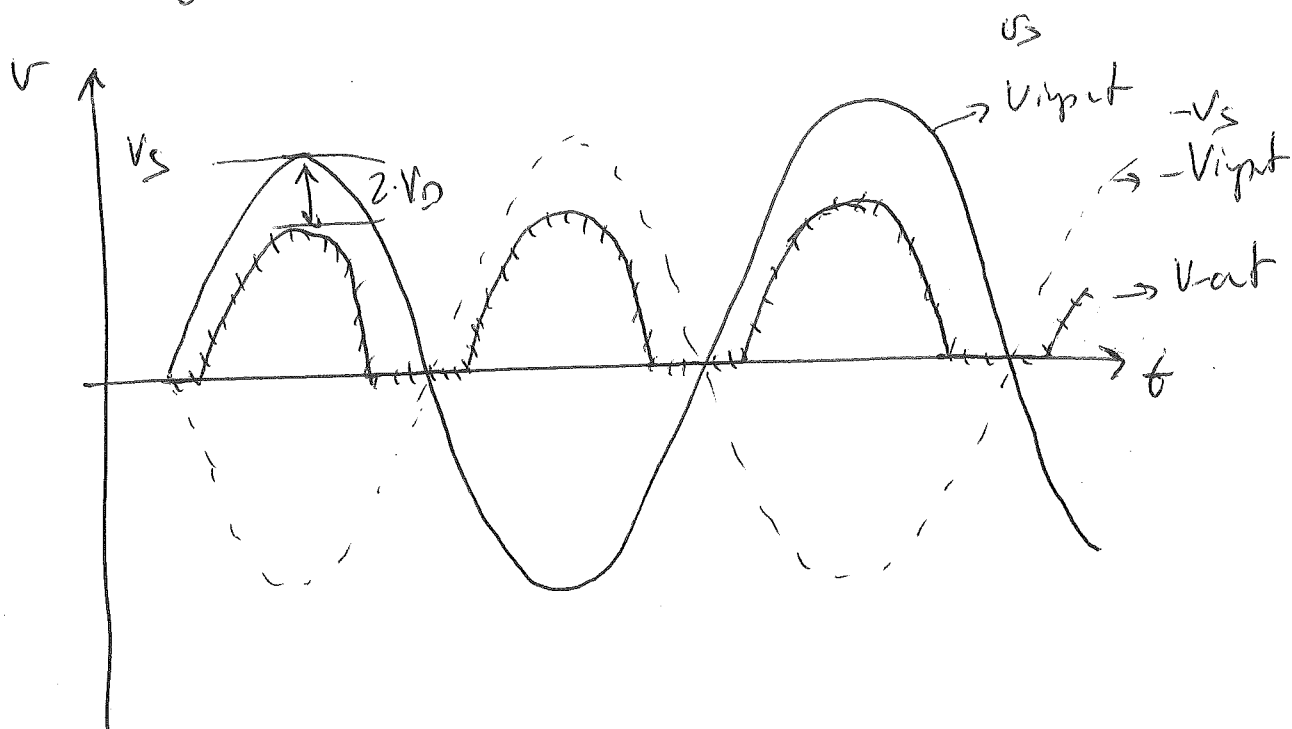


ex. 4.21 For bridge-rectifier circuit in previous page:

(a) Use constant-voltage-drop diode model to show that: (a) the average (or dc component) of the output voltage is $V_o \approx \left(\frac{2}{\pi}\right) V_s - V_D$

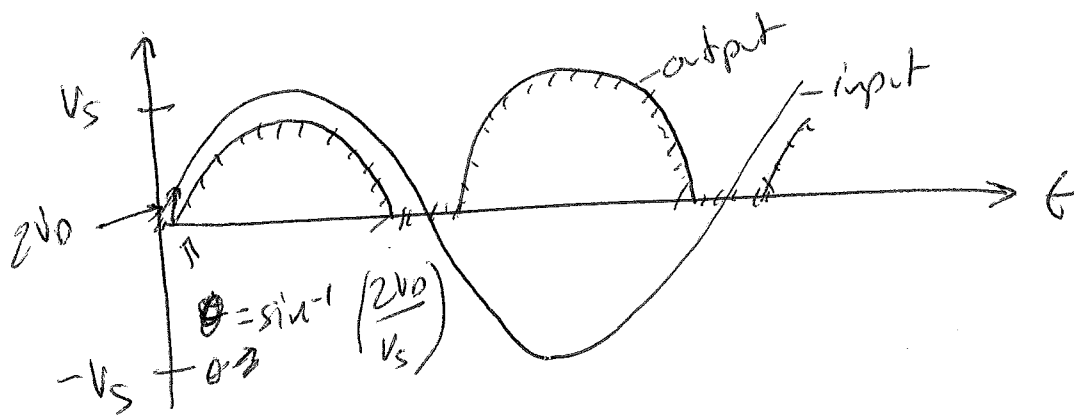(b) the peak diode current is $\frac{V_s - 2V_D}{R}$

→ Find numerical values for the quantities in (a) and (b) and the PIV for the case in which $V_s = 12\text{V (rms)}$, $V_D \approx 0.7\text{V}$, and $R = 100\Omega$.



$$(a) V_{o,avg} = \frac{1}{2\pi} \int_{\theta=\theta}^{\pi-\theta} (V_s \sin\phi - 2V_D) d\phi = \frac{2}{2\pi} [-V_s \cos\phi - 2V_D\phi]_{\phi=\theta}^{\pi-\theta}$$

$$= \frac{1}{\pi} [V_s \cos\theta - V_s \cos(\pi-\theta) - 2V_D(\pi-2\theta)] \text{, but } \cos\theta \approx 1,$$

$$\cos(\pi-\theta) \approx -1, \pi-2\theta \approx \pi.$$

$$\text{Thus, } V_{o,avg} \approx \frac{2V_s}{\pi} - 2V_D = \frac{2 \times 12\sqrt{2}}{\pi} - 1.4 = \boxed{9.4\text{V}}$$

$$(b) \text{ Peak diode current} = \frac{\text{Peak voltage}}{R} = \frac{V_s - 2V_D}{R} = \frac{12\sqrt{2} - 1.4}{100}$$

$$= \boxed{156 \text{ mA}}$$

$$\text{PIV} = V_s - V_D = 12\sqrt{2} - 0.7 = \boxed{16.3\text{V}}$$



9/14/2016

lec 9.1
lec 10.1

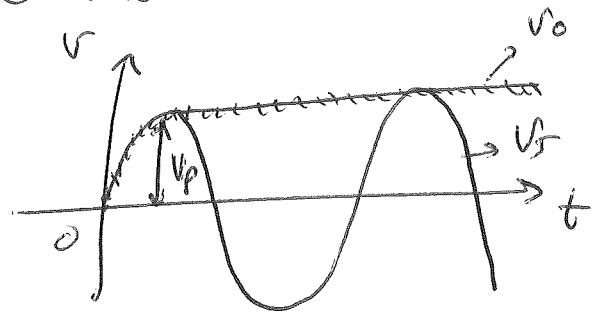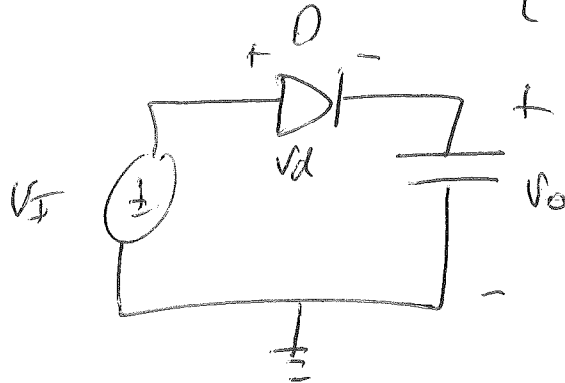4.5.4 - The rectifier w/ a filter capacitor - The peak rectifier.



→ Place a capacitor across the load resistor.

→ First: simple example: { ideal capacitor only
ideal diode



↑ Diode on during positive cycle
and $V_O \rightarrow V_P$.
Diode off as soon as $V_I < V_P$
since $V_D < 0$ when $V_O = V_P$.

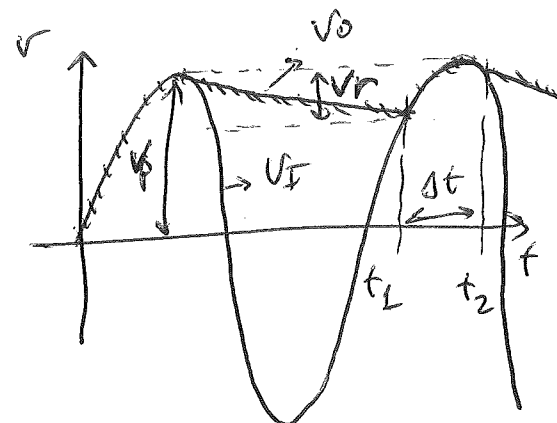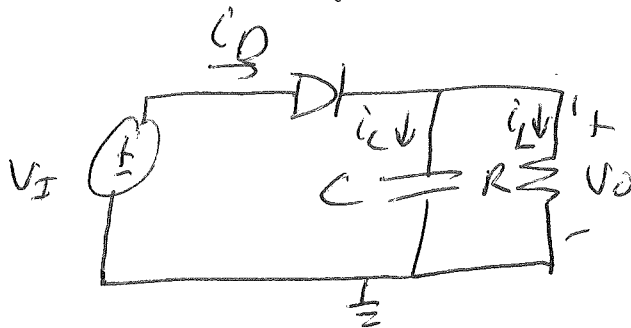→ More practical: load resistance across capacitor.
{ assume ideal diode for analysis.




→ Select large RC so that
time constant is greater than discharge
interval.

Analyzing the circuit in detail:

→ Assume $CR \gg T$

$$i_L = \frac{V_0}{R}$$
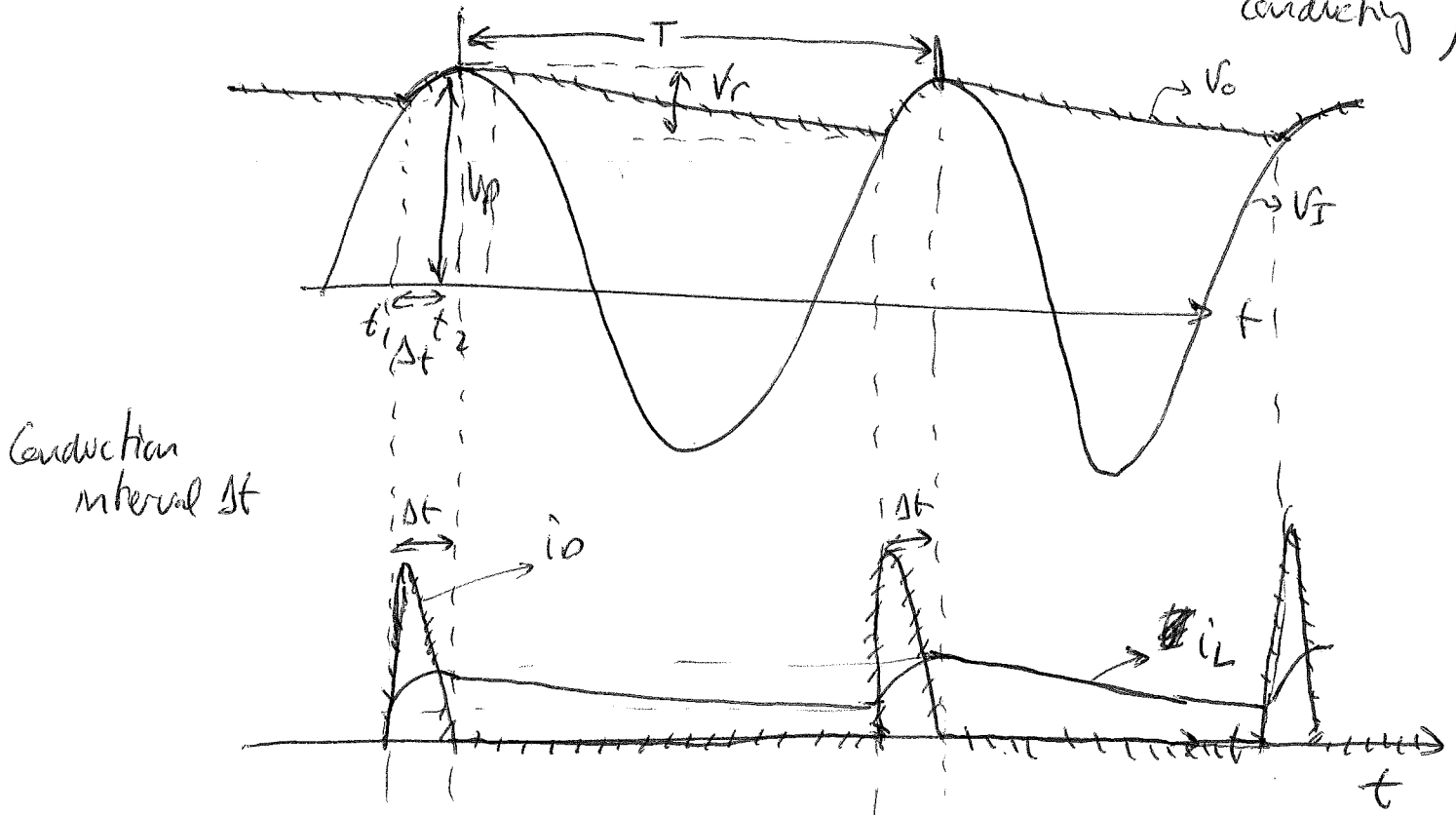
$$i_D = i_C + i_L = C \frac{dv_D}{dt} + i_L \quad (\text{when diode conducting})$$



Observations: ① Diode conducts during time interval Δt and supplies charge equal to that lost during discharge.

② Diode conduction starts at t_1 , when $v_i = v_o$. Conduction stops at t_2 , shortly after peak of v_i (when $i_D = 0$).

③ During ^{diode} off interval, C discharges through R , and v_o decays exponentially with time constant RC . At end of discharge $v_o = V_p - V_r$, where V_r is ripple voltage. V_r is small when $RC \gg \Delta t$.

④ When V_r is small, $v_o \approx V_p$. And i_L almost constant with RC

$$I_L = \frac{V_p}{R}$$

Control 7

↑ cont's

9/14/2016
(2)

$$I_L \approx \frac{V_p}{R} \quad (\text{for small } V_r, \text{ ripple voltage})$$

$$\text{and DC value of } V_{o,t} = V_p - \frac{1}{2} V_r \quad (\text{average of ripple})$$

→ Derive expression for V_r and for average and peak values of diode current:

→ Diode-off interval:

$$V_o = V_p e^{-t/RC}$$

→ At end of discharge interval: $(V_p - V_r) \approx V_p e^{-T/RC}$

$$\text{Assuming } RC \gg T \rightarrow e^{-T/RC} \approx 1 - T/RC$$

$$\therefore V_p - V_r = V_p \left(1 - \frac{T}{RC}\right)$$

$$-V_r = V_p - V_p \frac{T}{RC} - V_p$$

$$V_r \approx V_p \frac{T}{RC}$$

→ select a large C to keep V_r small.

→ Expressing as frequency $f = \frac{1}{T}$

$$V_r = \frac{V_p}{fRC}$$

$$\text{, and knowing } I_L = \frac{V_p}{R}$$

$$\rightarrow V_r = \frac{I_L}{fC}$$

→ Determine conduction interval: Δt .

→ assume conduction ends at peak $v_T = V_p$

$$V_p \cos(\omega \Delta t) = V_p - V_r \quad \omega = 2\pi f = \frac{2\pi}{T}$$

→ assume $\omega \Delta t$ to be small

$$\cos(\omega \Delta t) = 1 - \frac{1}{2}(\omega \Delta t)^2$$

$$\therefore V_p \left(1 - \frac{1}{2}(\omega \Delta t)^2\right) = V_p - V_r$$

$$V_p - \frac{V_p}{2}(\omega \Delta t)^2 = V_p - V_r$$

$$-\frac{V_p}{2}(\omega \Delta t)^2 = -V_r$$

$$(\omega \Delta t)^2 = 2 \frac{V_r}{V_p}$$

$$\boxed{\omega \Delta t = \sqrt{2 \frac{V_r}{V_p}}}$$

$$\omega = \frac{2\pi}{T} = 2\pi f$$

→ Determine average diode current during conduction i_{Davg} , by equating charge that diode supplies to capacitor: $Q_{\text{supplied}} = i_{\text{Davg}} \Delta t$

$$\text{and } i_{\text{Davg}} = i_{\text{Davg}} - I_L \quad \text{and } Q_{\text{lost}} = C V_r$$

$$\therefore i_{\text{Davg}} = I_L \left(1 + \pi \sqrt{\frac{2V_p}{V_r}}\right)$$

$$\text{and } i_{\text{Dmax}} = I_L \left(1 + 2\pi \sqrt{\frac{2V_p}{V_r}}\right)$$

For half-wave
→ rectifiers

For full-wave rectifiers: $V_r = \frac{V_p}{2fCR}$

$$i_{\text{Davg}} = I_L \left(1 + \pi \sqrt{\frac{V_p}{2V_r}}\right)$$

$$i_{\text{Dmax}} = I_L \left(1 + 2\pi \sqrt{\frac{V_p}{2V_r}}\right)$$

9/14/2016

(3)

example:

→ Peak rectifier fed by 60-Hz sinusoid

w/ $V_p = 100V$. $R_L = 10k\Omega$. Find C for peak-to-peak ripple of 2V. Also fraction of cycle where diode conducts and average and peak values of diode current.

$$\rightarrow C = \frac{V_p}{V_r f R} = \frac{100}{(2)(60)(10 \times 10^3)} = 83.3 \mu F$$

$\downarrow \quad \uparrow \quad \uparrow$
 $V_r \quad Hz \quad R_L$

$$\rightarrow \omega \Delta t \approx \sqrt{\frac{2V_r}{V_p}} = \sqrt{\frac{2 \times 2}{100}} = 0.2 \text{ rad.}$$

$$\rightarrow \text{Diode conducts } \frac{0.2}{2\pi} \times 100 = 3.18\% \text{ of the cycle.}$$

$$\rightarrow I_{\text{OAV}} = I_L \left(1 + \pi \sqrt{\frac{2V_p}{V_r}} \right) = 10 \text{ mA} \left(1 + \pi \sqrt{\frac{2 \times 100}{2}} \right) = 324 \text{ mA}$$

$$I_L = \frac{100V}{10k\Omega} = 10 \text{ mA}$$

$$I_{\text{Dmax}} = I_L \left(1 + 2\pi \sqrt{\frac{2V_p}{V_r}} \right) = 10 \text{ mA} \left(1 + 2\pi \sqrt{\frac{2 \times 100}{2}} \right) = 638 \text{ mA}$$