

Homework 6 – Due Wednesday 11/2/2016

Problems (not review questions): **9.1, 9.5, 9.6, Exercise 9.5** (page 611), **Exercise 9.17** (page 648) – where $G_m = g_{m1,2}$, $R_o = r_{o2} || r_{o4}$, **Exercise 9.20** (page 657)

Solutions for odd problems are on mycourses: Book_solutions.pdf,

Answer for 9.6: $R_D = 4 \text{ k}\Omega$, $(W/L)_{1,2} = 44.4$, $(W/L)_3 = 88.8$, $(W/L)_4 = 22.2$, $R = 12.5 \text{ k}\Omega$, $V_{CMmin} = -0.2 \text{ V}$, $V_{CMmax} = 0.5 \text{ V}$

Answers for exercises (9.5, 9.17, 9.20) are given in the book in pages 622, 648, and 657.

EEEE381 HOMEWORK FORMAT GUIDELINES

GENERAL: NEATNESS AND ORGANIZATION WILL BE GRADED. THE SAME GUIDELINES SHOULD BE FOLLOWED FOR EXAMS.

- ALL HOMEWORK IS TO BE HANDED ON ENGINEERING GRAPH PAPER or PLAIN WHITE PAPER (8.5 inch x 11 inch).
- NUMBER EACH PROBLEM INCLUDING CHAPTER IT COMES FROM
- HIGHLIGHT EACH FINAL ANSWER WITH A BOX AND INCLUDE APPROPRIATE UNITS.
- INCLUDE YOUR NAME ON EVERY PAGE
- ALL PROBLEMS SHOULD BE TURNED IN, IN ORDER!
- IF WORK IS NOT LEGIBLE, IT WILL NOT BE GRADED
- CROSS OUTS ARE NOT ACCEPTABLE. USE A PENCIL AND ERASER OR PEN AND WHITE-OUT. (Green-out?)
- PRESENT SOLUTION IN A FORMAT THAT PROCEEDS FROM LEFT TO RIGHT, TOP TO BOTTOM. IF ORGANIZATION OF SOLUTION IS NOT CLEAR, PROBLEM WILL NOT BE GRADED.
- PROVIDE A CONCISE DESCRIPTION OF YOUR METHOD OF SOLUTION. IF NONE IS PROVIDED, NO PARTIAL CREDIT WILL BE AFFORDED.
- PROVIDE AN APPROPRIATELY LABELED CIRCUIT DIAGRAM. IF CIRCUIT IS MODIFIED, INCLUDE MODIFIED DIAGRAM(S).
- MAKE SURE ALL PAGES ARE ATTACHED TO EACH OTHER SECURELY. STAPLES ARE A CLASSIC WAY TO DO THIS.
- -REMEMBER- HOMEWORK ASSIGNMENTS ARE NOT JUST ABOUT LEARNING TO DO THE PROBLEM. IT IS ABOUT LEARNING TO PRESENT YOUR WORK SO OTHERS CAN UNDERSTAND WHAT YOU DO - A VALUABLE SKILL IN THE WORKPLACE.

Things to remember

- 1) Re-Draw the Circuit on your homework sheet.
- 2) Show all work.
- 3) Final answer should be in decimal form.
- 4) Final answers should be boxed.
- 5) Your name should be on every page.

Homework 6 – Solutions

9.1 Refer to Fig. 9.2.

$$(a) \frac{I}{2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_{1,2} V_{OV}^2$$

$$0.08 = \frac{1}{2} \times 0.4 \times 10 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.2 \text{ V}$$

$$V_{GS} = V_{in} + V_{OV} = 0.4 + 0.2 = 0.6 \text{ V}$$

$$(b) V_{CM} = 0$$

$$V_S = 0 - V_{GS} = -0.6 \text{ V}$$

$$I_{D1} = I_{D2} = \frac{I}{2} = 0.08 \text{ mA}$$

$$V_{D1} = V_{D2} = V_{DD} - I_{D1,2} R_D$$

$$= 1 - 0.08 \times 5 = +0.6 \text{ V}$$

$$(c) V_{CM} = +0.4 \text{ V}$$

$$V_S = 0.4 - V_{GS} = 0.4 - 0.6 = -0.2 \text{ V}$$

$$I_{D1} = I_{D2} = \frac{I}{2} = 0.08 \text{ mA}$$

$$V_{D1} = V_{D2} = V_{DD} - I_{D1,2} R_D$$

$$= 1 - 0.08 \times 5 = +0.6 \text{ V}$$

Since $V_{CM} = 0.4 \text{ V}$ and $V_D = 0.6 \text{ V}$, $V_{GD} = -0.2 \text{ V}$, which is less than V_{in} (0.4 V), indicating that our implicit assumption of saturation-mode operation is justified.

$$(d) V_{CM} = -0.1 \text{ V}$$

$$V_S = -0.1 - V_{GS} = -0.1 - 0.6 = -0.7 \text{ V}$$

$$I_{D1} = I_{D2} = \frac{I}{2} = 0.08 \text{ mA}$$

$$V_{D1} = V_{D2} = V_{DD} - I_{D1,2} R_D$$

$$= 1 - 0.08 \times 5 = +0.6 \text{ V}$$

(e) The highest value of V_{CM} for which Q_1 and Q_2 remain in saturation is

$$V_{CM\max} = V_{D1,2} + V_{in}$$

$$= 0.6 + 0.4 = 1.0 \text{ V}$$

(f) To maintain the current-source operating properly, we need to keep a minimum voltage of 0.2 V across it, thus

$$V_{S\min} = -V_{SS} + V_{CS} = -1 + 0.2 = -0.8 \text{ V}$$

$$V_{CM\min} = V_{S\min} + V_{GS}$$

$$= -0.8 + 0.6$$

$$= -0.2 \text{ V}$$


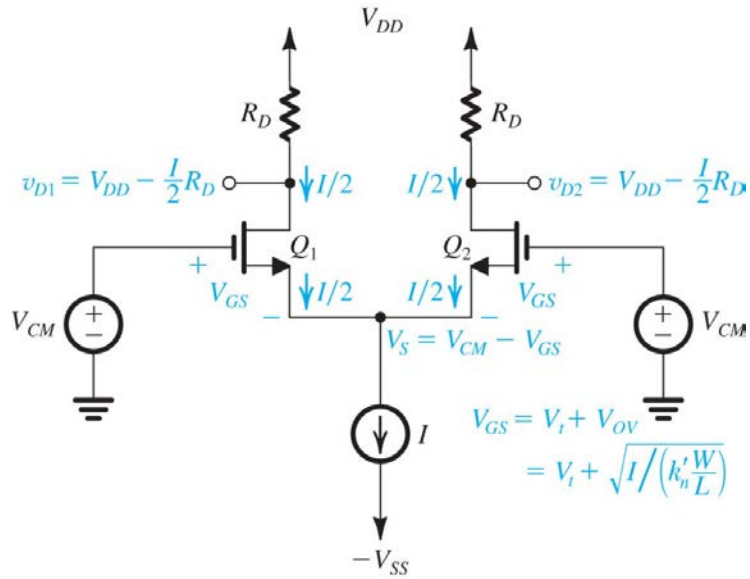


Figure 9.2 The MOS differential pair with a common-mode input voltage V_{CM} .

9.5

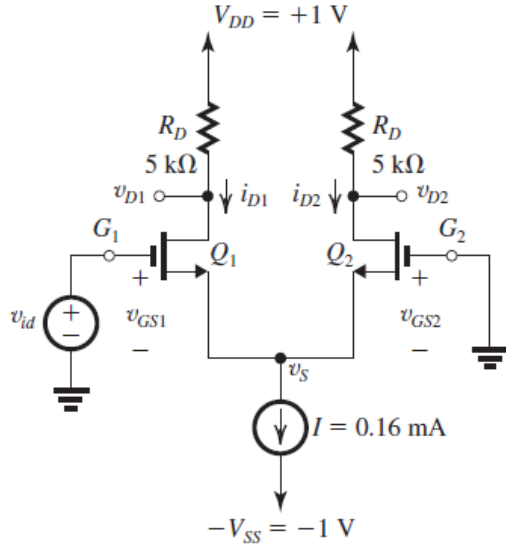

For $i_{D1} = 0.09$ mA and $i_{D2} = 0.07$ mA,

$$i_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (v_{GS2} - V_{tn})^2$$

$$0.07 = \frac{1}{2} \times 0.4 \times 10 (v_{GS2} - 0.4)^2$$

$$\Rightarrow v_{GS2} = 0.587 \text{ V}$$

and

$$v_S = -0.587 \text{ V}$$

$$i_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (v_{GS1} - V_{tn})^2$$

$$0.09 = \frac{1}{2} \times 0.4 \times 10 (v_{GS1} - 0.4)^2$$

$$\Rightarrow v_{GS1} = 0.612 \text{ V}$$

$$v_{id} = v_S + v_{GS1} = -0.587 + 0.612$$

$$= 0.025 \text{ V}$$

$$v_{D2} = V_{DD} - i_{D2} R_D$$

$$= 1 - 0.07 \times 5 = 0.65 \text{ V}$$

$$v_{D1} = 1 - 0.09 \times 5 = 0.55 \text{ V}$$

$$v_{D2} - v_{D1} = 0.65 - 0.55 = 0.10 \text{ V}$$

$$\text{Voltage gain} = \frac{v_{D2} - v_{D1}}{v_{id}} = \frac{0.10}{0.025} = 4 \text{ V/V}$$

To obtain the complementary split in current, that is, $i_{D1} = 0.07$ mA and $i_{D2} = 0.09$ mA,

$$v_{id} = -0.025 \text{ V}$$

$$-0.2 \text{ V} \leq V_{ICM} \leq +0.5 \text{ V}$$

Ex: 9.5 With $I = 200 \mu\text{A}$, for all transistors,

$$I_D = \frac{I}{2} = \frac{200 \mu\text{A}}{2} = 100 \mu\text{A}$$

$$L = 2(0.18 \mu\text{m}) = 0.36 \mu\text{m}$$

$$r_{o1} = r_{o2} = r_{o3} = r_{o4} = \frac{|V'_A| L}{I_D}$$

$$= \frac{(10 \text{ V} / \mu\text{m}) (0.36 \mu\text{m})}{0.1 \text{ mA}} = 36 \text{ k}\Omega$$

$$\text{Since } I_{D1} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) V_{OV}^2,$$

$$\left(\frac{W}{L} \right)_1 = \left(\frac{W}{L} \right)_2 = \frac{2I_D}{\mu_n C_{ox} V_{OV}^2}$$

$$\frac{2(100 \mu\text{A})}{(400 \mu\text{A}/\text{V}^2) (0.2 \text{ V})^2} = 12.5$$

$$\left(\frac{W}{L} \right)_3 = \left(\frac{W}{L} \right)_4 = \frac{2I_D}{\mu_p C_{ox} |V_{OV}|^2}$$


$$\frac{2(100 \mu\text{A})}{(100 \mu\text{A}/\text{V}^2) (0.2)^2} = 50$$

$$g_m = \frac{I_D}{V_{OV}/2} = \frac{(100 \mu\text{A}) (2)}{0.2 \text{ V}} = 1 \text{ mA/V},$$

so

$$A_d = g_{m1}(r_{o1} \parallel r_{o3}) = 1(\text{mA/V}) (36 \text{ k}\Omega \parallel 36 \text{ k}\Omega)$$

$$= 18 \text{ V/V}$$

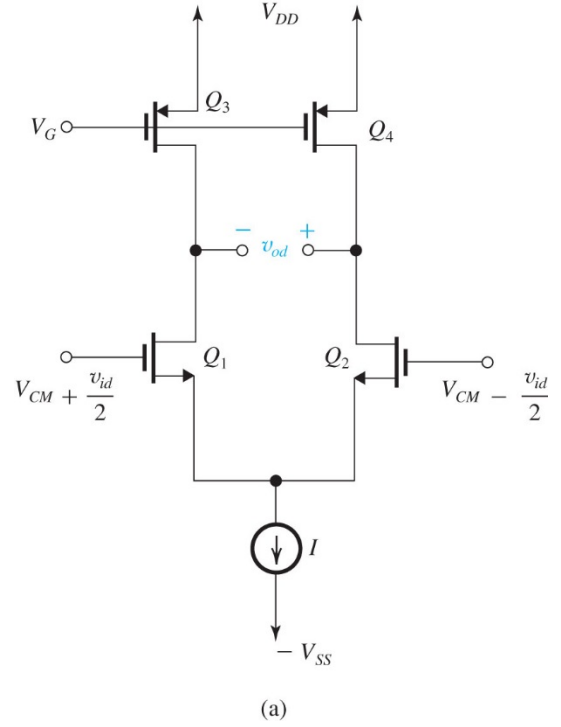

Ex: 9.17 $I_D = \frac{1}{2}I = 0.4 \text{ mA}$

$$I_D = \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L} \right)_n V_{OV}^2$$

$$0.4 = \frac{1}{2} \times 0.2 \times 100 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.2 \text{ V}$$

$$g_{m1,2} = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.4}{0.2} = 4 \text{ mA/V}$$

$$G_m = g_{m1,2} = 4 \text{ mA/V}$$

$$r_{o2} = \frac{V_{An}}{I_D} = \frac{20}{0.4} = 50 \text{ k}\Omega$$

$$r_{o4} = \frac{|V_{Ap}|}{I_D} = \frac{20}{0.4} = 50 \text{ k}\Omega$$

$$R_o = r_{o2} \parallel r_{o4} = 50 \parallel 50 = 25 \text{ k}\Omega$$

$$A_d = G_m R_o = 4 \times 25 = 100 \text{ V/V}$$

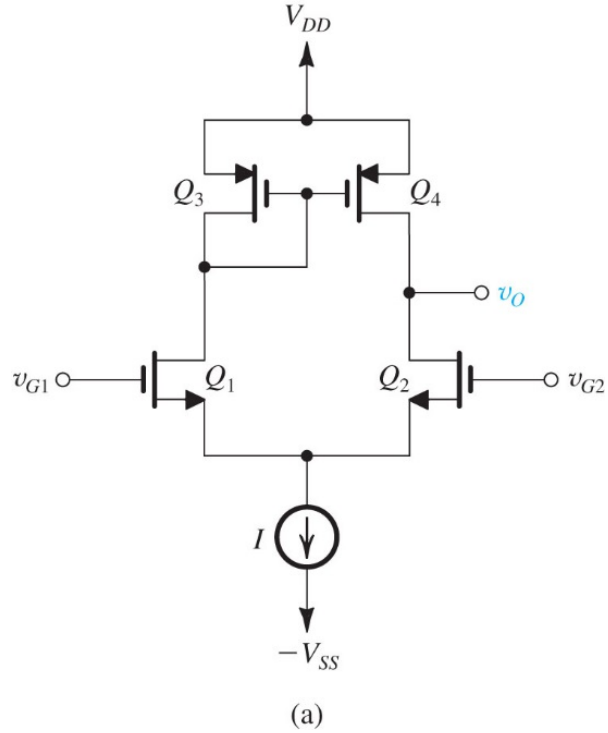


Figure 9.32 (a)

Ex: 9.20 From Exercise 9.17, we get

$$I_D = 0.4 \text{ mA}$$

$$V_{OV} = 0.2 \text{ V} \quad g_{m1,2} = 4 \text{ mA/V}$$

$$G_m = 4 \text{ mA/V} \quad A_d = 100 \text{ V/V}$$

Now,

$$R_{SS} = 25 \text{ k}\Omega$$

$$g_{m3} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L} \right)_p I_D}$$

$$= \sqrt{2 \times 0.1 \times 200 \times 0.4} = 4 \text{ mA/V}$$

$$|A_{cm}| = \frac{1}{2g_{m3}R_{SS}} = \frac{1}{2 \times 4 \times 25} = 0.005 \text{ V/V}$$

$$\text{CMRR} = \frac{|A_d|}{|A_{cm}|} = \frac{100}{0.005}$$

$$= 20,000 \text{ or } 20 \log 20,000 = 86 \text{ dB}$$