

Homework 8 – Due 11/16/2016




Problems (not review questions): 10.1, 10.3, 10.5, 10.32, 10.34

Solutions for 10.1, 10.3 and 10.5 are in book_solutions.pdf on mycourses

For 10.32, 10.34 use the following equation to find transmission zero frequency $\rightarrow f_z = gm / (2\pi C_{gd})$

Solutions for 10.32: $A_M = -36.4$ V/V, $f_H = 15.2$ kHz, $f_z = 1.6$ GHz

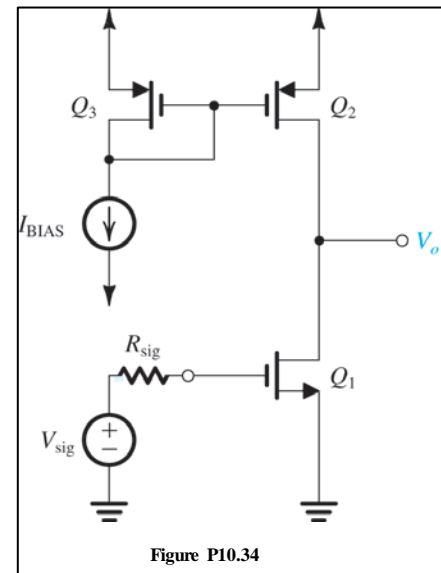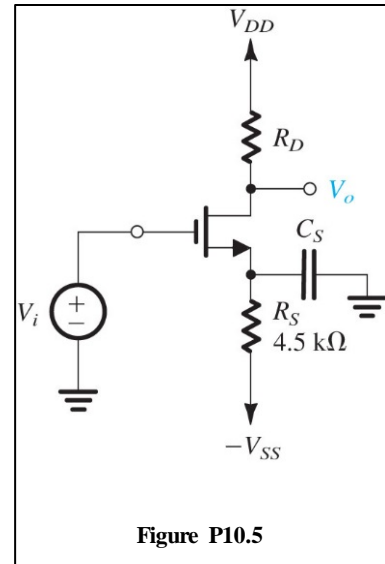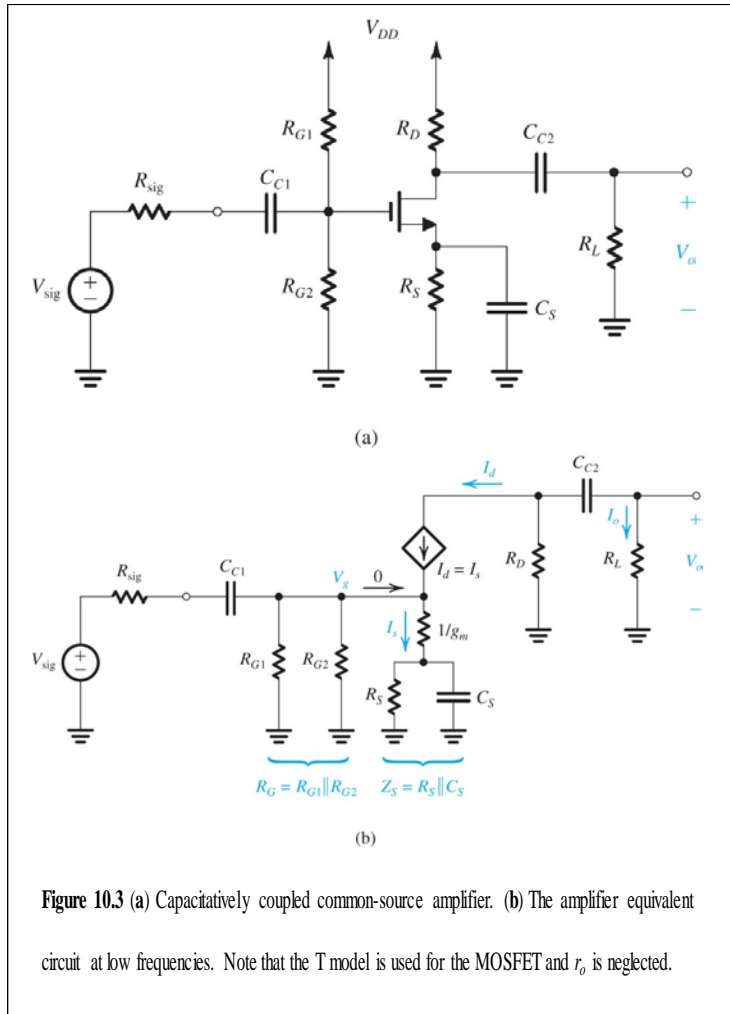Solutions for 10.34: $A_M = -81$ V/V, $f_H = 554$ kHz, $f_z = 11.2$ GHz



EE381 HOMEWORK FORMAT GUIDELINES

Things to remember

- 1) Re-Draw the Circuit on your homework sheet.
- 2) Show all work.
- 3) Final answer should be in decimal form.
- 4) Final answers should be boxed.
- 5) Your name should be on every page.

10.1 Refer to Fig. 10.3(b).

$$\frac{V_g}{V_{sig}} = \frac{R_G}{R_G + R_{sig} + \frac{1}{sC_{C1}}}$$

where

$$R_G = R_{G1} \parallel R_{G2} = 2 \text{ M}\Omega \parallel 1 \text{ M}\Omega = 667 \text{ k}\Omega$$

and

$$R_{sig} = 200 \text{ k}\Omega$$

$$\frac{V_g}{V_{sig}} = \frac{R_G}{R_G + R_{sig}} \frac{s}{s + \frac{1}{C_{C1}(R_G + R_{sig})}}$$

Thus,

$$f_{P1} = \frac{1}{2\pi C_{C1}(R_G + R_{sig})}$$

We required

$$f_{P1} \leq 10 \text{ Hz}$$

thus we select C_{C1} so that

$$\frac{1}{2\pi C_{C1}(R_G + R_{sig})} \leq 10$$

$$C_{C1} \geq \frac{1}{2\pi \times 10 \times (667 + 200) \times 10^3} = 18.4 \text{ nF}$$

$$\Rightarrow C_{C1} = 20 \text{ nF}$$

10.3 Refer to Fig. 10.3(b).

$$I_s = \frac{V_g}{\frac{1}{g_m} + Z_S}$$

$$I_s = \frac{g_m V_g Y_S}{Y_S + g_m}$$

$$\begin{aligned} \frac{I_s}{V_g} &= \frac{g_m \left(\frac{1}{R_S} + sC_S \right)}{g_m + \frac{1}{R_S} + sC_S} \\ &= g_m \frac{s + 1/C_S R_S}{s + \frac{g_m + 1/R_S}{C_S}} \end{aligned}$$

Thus,

$$f_{p2} = \frac{g_m + 1/R_S}{2\pi C_S}$$

$$f_z = \frac{1}{2\pi C_S R_S}$$

where

$$g_m = 5 \text{ mA/V and } R_S = 1.8 \text{ k}\Omega$$

To make $f_{p2} \leq 100 \text{ Hz}$,

$$\frac{g_m + 1/R_S}{2\pi C_S} \leq 100$$

$$\Rightarrow C_S \geq \frac{5 \times 10^{-3} + (1/1.8 \times 10^3)}{2\pi \times 100} = 8.8 \text{ }\mu\text{F}$$

Select $C_S = 10 \text{ }\mu\text{F}$.

Thus,

$$f_{p2} = \frac{5 \times 10^{-3} + (1/1.8 \times 10^3)}{2\pi \times 10 \times 10^{-6}} = 88.4 \text{ Hz}$$

and

$$f_z = \frac{1}{2\pi \times 10 \times 10^{-6} \times 1.8 \times 10^3} = 8.84 \text{ Hz}$$

10.5

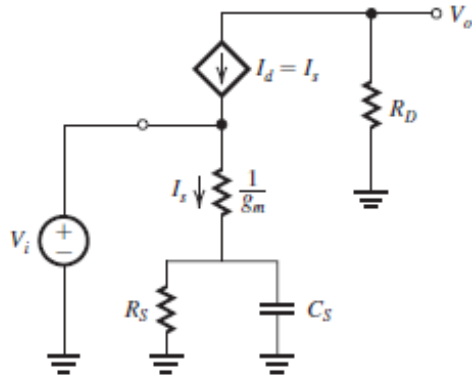


Figure 1

Replacing the MOSFET with its T model results in the circuit shown in Fig. 1.

$$(a) A_M \equiv \frac{V_o}{V_i} = -g_m R_D$$

$$-20 = -2 \times R_D$$

$$\Rightarrow R_D = 10 \text{ k}\Omega$$

$$(b) f_p = \frac{g_m + 1/R_S}{2\pi C_S}$$

$$100 = \frac{2 \times 10^{-3} + (1/4.5 \times 10^3)}{2\pi C_S}$$

$$\Rightarrow C_S = 3.53 \text{ }\mu\text{F}$$

$$(c) f_z = \frac{1}{2\pi C_S R_S} =$$

$$\frac{1}{2\pi \times 3.53 \times 10^{-6} \times 4.5 \times 10^3} = 10 \text{ Hz}$$

$$(d) \text{ Since } f_p \gg f_z,$$

$$f_L \simeq f_p = 100 \text{ Hz}$$

(e) The Bode plot for the gain is shown in Fig. 2.

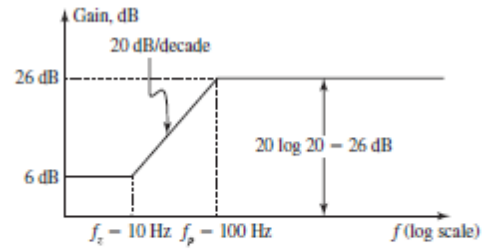


Figure 2

Observe that the dc gain is 6 dB, i.e. 2 V/V. This makes perfect sense since from Fig. 1 we see that at dc, capacitor C_S behaves as open circuit and the gain becomes

$$\begin{aligned} \text{DC gain} &= -\frac{R_D}{\frac{1}{g_m} + R_S} = -\frac{10 \text{ k}\Omega}{\left(\frac{1}{2} + 4.5\right)} \\ &= -2 \text{ V/V} \end{aligned}$$

$$10.32 \text{ (a) } A_M = -\frac{R_G}{R_G + R_{\text{sig}}} g_m R'_L$$

where

$$R'_L = R_D \parallel R_L \parallel r_o$$

$$= 20 \text{ k}\Omega \parallel 20 \text{ k}\Omega \parallel 100 \text{ k}\Omega$$

$$= 9.1 \text{ k}\Omega$$

$$A_M = -\frac{2 \text{ M}\Omega}{2 \text{ M}\Omega + 0.5 \text{ M}\Omega} \times 5 \times 9.1$$

$$= -36.4 \text{ V/V}$$

$$\text{(b) } f_H = \frac{1}{2\pi C_{\text{in}} R'_{\text{sig}}}$$

where

$$C_{\text{in}} = C_{gs} + C_{gd}(1 + g_m R'_L)$$

$$= 3 + 0.5(1 + 5 \times 9.1)$$

$$= 26.25 \text{ pF}$$

and

$$R'_{\text{sig}} = R_{\text{sig}} \parallel R_G$$

$$= 500 \text{ k}\Omega \parallel 2000 \text{ k}\Omega$$

$$= 400 \text{ k}\Omega$$

Thus,

$$f_H = \frac{1}{2\pi \times 26.25 \times 10^{-12} \times 400 \times 10^3}$$

$$= 15.2 \text{ kHz}$$

$$\text{(c) } f_Z = \frac{g_m}{2\pi C_{gd}}$$

$$= \frac{5 \times 10^{-3}}{2\pi \times 0.5 \times 10^{-12}}$$

$$= 1.6 \text{ GHz}$$

$$10.34 \quad g_m = \sqrt{2\mu_n C_{ox}(W/L)_1 I_{D1}}$$

$$= \sqrt{2 \times 0.09 \times 100 \times 0.1}$$

$$= 1.34 \text{ mA/V}$$

$$r_{o1} = \frac{|V_{A1}|}{I_{D1}} = \frac{12.8}{0.1} = 128 \text{ k}\Omega$$

$$r_{o2} = \frac{|V_{A2}|}{I_{D2}} = \frac{19.2}{0.1} = 192 \text{ k}\Omega$$

The total resistance at the output node, R'_L , is given by

$$R'_L = r_{o1} \parallel r_{o2} = 128 \text{ k}\Omega \parallel 192 \text{ k}\Omega$$

$$= 76.8 \text{ k}\Omega$$

$$A_M = -g_m R'_L$$

$$= -1.34 \times 76.8 = -103 \text{ V/V}$$

$$f_H = \frac{1}{2\pi C_{in} R_{sig}}$$

where

$$C_{in} = C_{gs} + C_{gd}(1 + g_m R'_L)$$

$$= 0.2 + 0.015(1 + 103)$$

$$= 1.76 \text{ pF}$$

Thus,

$$f_H = \frac{1}{2\pi \times 1.76 \times 10^{-12} \times 200 \times 10^3}$$

$$= 452 \text{ kHz}$$

$$f_Z = \frac{g_m}{2\pi C_{gd}} = \frac{1.34 \times 10^{-3}}{2\pi \times 0.015 \times 10^{-12}}$$

$$= 14.2 \text{ GHz}$$