

Homework 2 - Solutions

Problems (not review questions) :

4.2, 4.3, 4.16, 4.19, 4.41, 4.56, 4.60, 4.61

Extra problem (not graded): 4.66

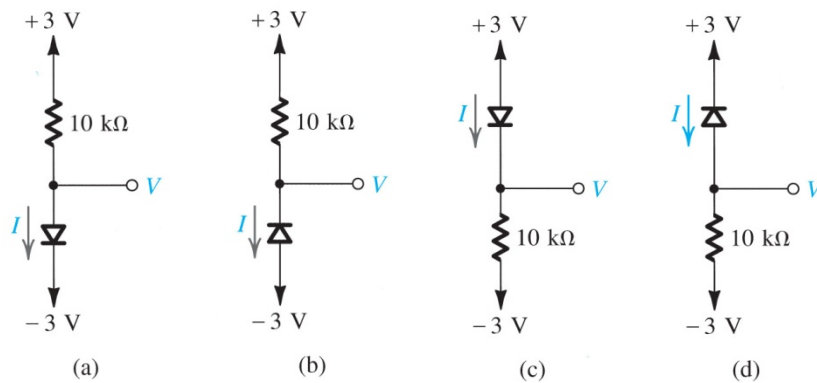


Figure P4.2

4.2 Refer to Fig. P4.2.

(a) Diode is conducting, thus

$$V = -3 \text{ V}$$

$$I = \frac{+3 - (-3)}{10 \text{ k}\Omega} = 0.6 \text{ mA}$$

(b) Diode is reverse biased, thus

$$I = 0$$

$$V = +3 \text{ V}$$

(c) Diode is conducting, thus

$$V = +3 \text{ V}$$

$$I = \frac{+3 - (-3)}{10 \text{ k}\Omega} = 0.6 \text{ mA}$$


(d) Diode is reverse biased, thus

$$I = 0$$



$$V = -3 \text{ V}$$

4.3

(a)

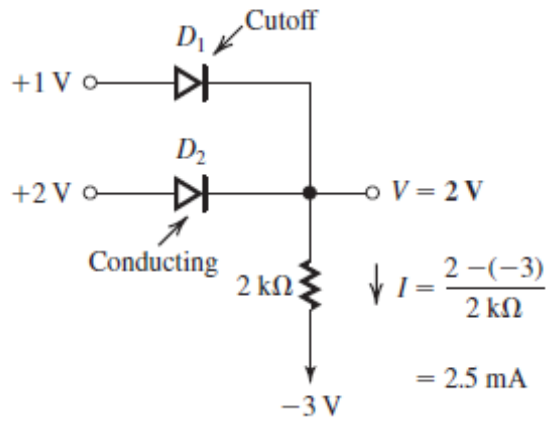

(b)

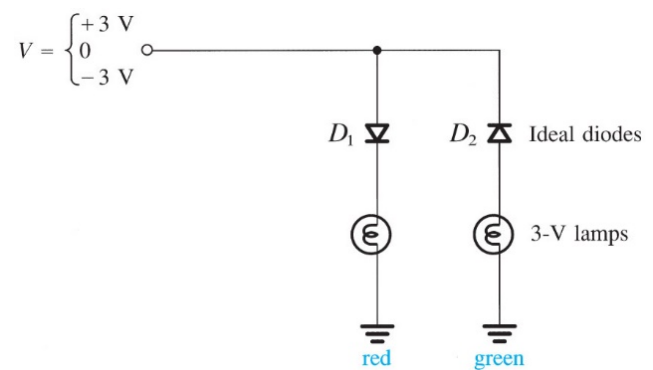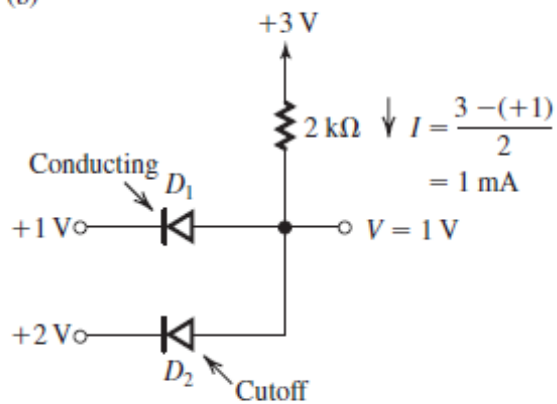

4.16

V	RED	GREEN	
3 V	ON	OFF	- D_1 conducts
0	OFF	OFF	- No current flows
-3 V	OFF	ON	- D_2 conducts

Figure P4.16

4.19 $I_1 = I_S e^{0.7/V_T} = 10^{-3}$


$i_2 = I_S e^{0.5/V_T}$

$\frac{i_2}{i_1} = \frac{i_2}{10^{-3}} = e^{\frac{0.5-0.7}{0.025}}$

$i_2 = 0.335 \mu\text{A}$

4.41


(a)

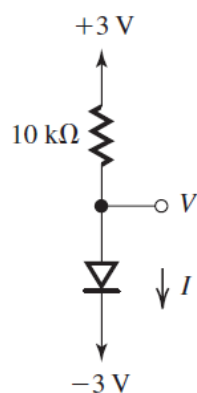

$V = -3 + 0.7 = -2.3 \text{ V}$

$I = \frac{3 + 2.3}{10}$
 $= 0.53 \text{ mA}$


(b)

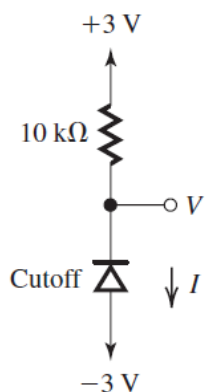

$I = 0 \text{ A}$

$V = 3 - I(10) = 3 \text{ V}$


(c)

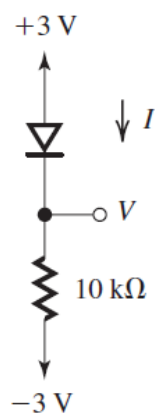

$V = 3 - 0.7 = 2.3 \text{ V}$

$I = \frac{2.3 + 3}{10} = 0.53 \text{ mA}$

(d)

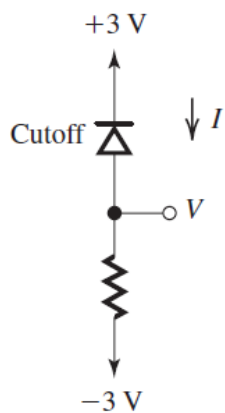

$I = 0 \text{ A}$

$V = -3 \text{ V}$

$$I_L = 1.5/1.5 = 1 \text{ mA}$$

$$I = I_D + I_L = 7.39 \text{ mA} + 1 \text{ mA}$$

$$= 8.39 \text{ mA}$$

$$\therefore R = \frac{5 - 1.5}{8.39 \text{ mA}} = 417 \Omega$$

Use a small-signal model to find voltage ΔV_O when the value of the load resistor, R_L , changes:

$$r_d = \frac{V_T}{I_D} = \frac{0.025}{7.39} = 3.4 \Omega$$

When load is disconnected, all the current I flows through the diode. Thus

$$\Delta I_D = 1 \text{ mA}$$

$$\Delta V_O = \Delta I_D \times 2r_d$$

$$= 1 \times 2 \times 3.4$$

$$= 6.8 \text{ mV}$$

With $R_L = 1 \text{ k}\Omega$,

$$I_L \simeq \frac{1.5 \text{ V}}{1} = 1.5 \text{ mA}$$

$$\Delta I_L = 0.5 \text{ mA}$$

$$\Delta I_D = -0.5 \text{ mA}$$

$$\Delta V_O = -0.5 \times 2 \times 3.4$$

$$= -3.4 \text{ mV}$$

With $R_L = 750 \Omega$,

$$I_L \simeq \frac{1.5}{0.75} = 2 \text{ mA}$$

$$\Delta I_L = 1 \text{ mA}$$

$$\Delta I_D = -1 \text{ mA}$$

$$\Delta V_O = -1 \times 2 \times 3.4$$

$$= -6.8 \text{ mV}$$

With $R_L = 500 \Omega$,

$$I_L \simeq \frac{1.5}{0.5} = 3 \text{ mA}$$


$$\Delta I_L = 2.0 \text{ mA}$$

$$\Delta I_D = -2.0 \text{ mA}$$

$$\Delta V_O = -2 \times 2 \times 3.4$$

$$= -13.6 \text{ mV}$$

4.56

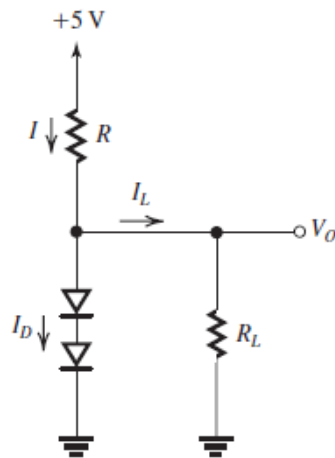

Diode has 0.7 V drop at 1 mA current

$V_O = 1.5 \text{ V}$ when $R_L = 1.5 \text{ k}\Omega$

$$I_D = I_S e^{V/V_T}$$

$$1 \times 10^{-3} = I_S e^{0.7/0.025}$$

$$\Rightarrow I_S = 6.91 \times 10^{-16} \text{ A}$$

$$\text{Voltage drop across each diode} = \frac{1.5}{2} = 0.75 \text{ V.}$$

$$\therefore I_D = I_S e^{V/V_T} = 6.91 \times 10^{-16} \times e^{0.75/0.025}$$

$$= 7.38 \text{ mA}$$

4.60 (a) Three 6.8-V zeners provide $3 \times 6.8 = 20.4$ V with $3 \times 10 = 30\text{-}\Omega$ resistance. Neglecting R , we have


$$\text{Load regulation} = -30 \text{ mV/mA.}$$

(b) For 5.1-V zeners we use 4 diodes to provide 20.4 V with $4 \times 30 = 120\text{-}\Omega$ resistance.

$$\text{Load regulation} = -120 \text{ mV/mA}$$

For part (b) of our problem the zener resistance of the diodes was 25 Ohm. Therefore the total zener resistance would have been 100 Ohm and the load regulation -120 mV/mA.

4.61

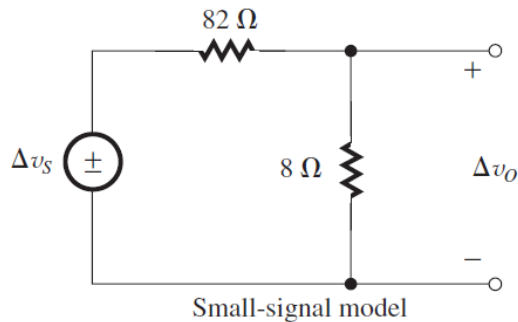

From the small-signal model we obtain

$$\frac{\Delta v_O}{\Delta v_S} = \frac{8}{8 + 82} = \frac{8}{90}$$

Now $\Delta v_S = 1.0$ V.


$$\begin{aligned} \therefore \Delta v_O &= \frac{8}{90} \Delta v_S = \frac{8}{90} \times 1.0 \\ &= 88.9 \text{ mV} \end{aligned}$$

4.66 (a) $V_{ZT} = V_{Z0} + r_z I_{ZT}$

$$10 = V_{Z0} + 7(0.025)$$

$$\Rightarrow V_{Z0} = 9.825 \text{ V}$$

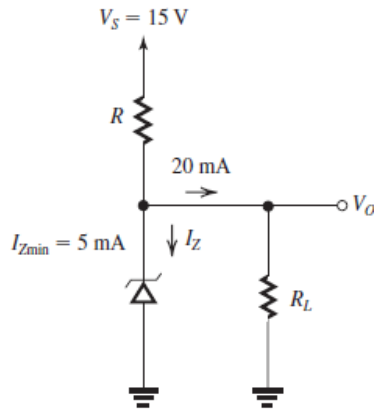(b) The minimum zener current of 5 mA occurs when $I_L = 20 \text{ mA}$ and V_S is at its minimum of $20(1 - 0.25) = 15 \text{ V}$. See the circuit below:



$$R \leq \frac{15 - V_{Z0}}{20 + 5}$$

where we have used the minimum value of V_S , the maximum value of load current, and the minimum required value of zener diode current, and we assumed that at this current $V_Z \simeq V_{Z0}$. Thus,

$$R \leq \frac{15 - 9.825 + 7}{25}$$

$$\leq 207 \Omega.$$

\therefore use $R = 207 \Omega$

(c) Line regulation $= \frac{7}{207 + 7} = 33 \frac{\text{mV}}{\text{V}}$

$$\pm 25\% \text{ change in } v_S \equiv \pm 5 \text{ V}$$

$$V_O \text{ changes by } \pm 5 \times 33 = \pm 0.165 \text{ mV}$$

$$\text{corresponding to } \frac{\pm 0.165}{10} \times 100 = \pm 1.65\%$$

(d) Load regulation $= -(r_z \parallel R)$

$$= -(7 \parallel 207) = -6.77 \Omega$$

$$\text{or } -6.77 \text{ V/A}$$


$$\Delta V_O = -6.77 \times 20 \text{ mA} = -135.4 \text{ mV}$$

$$\text{corresponding to } -\frac{0.1354}{10} \times 100 = -1.35\%$$

(e) The maximum zener current occurs at no load $I_L = 0$ and the supply at its largest value of

$$20 + \frac{1}{4}(20) = 25 \text{ V.}$$

$$V_Z = V_{Z0} + r_z I_Z$$

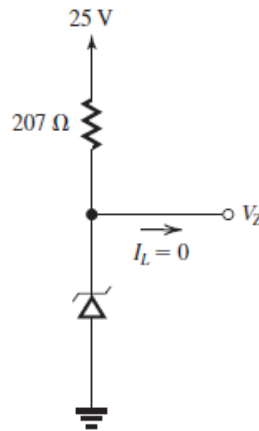

$$= 9.825 + 7 \times \frac{25 - V_Z}{207}$$

$$207V_Z = 207(9.825) + 7(25) - 7V_Z$$

$$\Rightarrow V_Z = 10.32 \text{ V}$$

$$I_{Z\text{max}} = \frac{25 - 10.32}{0.207} = 70.9 \text{ mA}$$

$$P_Z = 10.32 \times 70.9$$

$$= 732 \text{ mW}$$