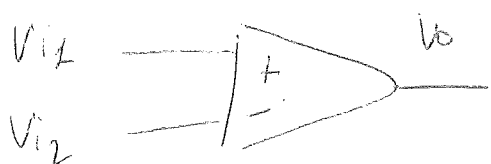


DIFFERENTIAL AMPLIFIER - CHAPTER 9

DIFF AMP. \rightarrow similar to op-amp w/o feedback loop.



• advantages: diff mode gain.

$$\frac{V_o}{V_{i1} - V_{i2}} \quad \text{made very large (noise rejection)}$$

• Common mode gain

$$\frac{V_o}{\frac{1}{2}(V_{i1} + V_{i2})} \quad \text{made as close to 0.}$$

\rightarrow Dominant configuration for amplifiers since active load resistances can be easily made.

A_d = Diff mode gain

V_d = Diff mode input = $V_{i1} - V_{i2}$

A_{cm} = Common mode gain.

V_{cm} = Common mode input = $\frac{1}{2}(V_{i1} + V_{i2})$

\rightarrow average of 2 inputs.

V_o has 2 components

$$V_o = \underbrace{A_d \cdot V_d}_{\text{diff mode}} + \underbrace{A_{cm} \cdot V_{cm}}_{\text{common mode.}}$$

Make $A_d \gg A_{cm}$

\rightarrow Ideal diff. amp. $A_{cm} \rightarrow 0$


\rightarrow Non-ideal diff. amp. Common mode rejection ratio.
CMRR (in dB)

10/12/2016
②

$$CMRR = 20 \log \left(\frac{A_d}{A_{cm}} \right) \quad \text{typical } > 100 \text{ dB}$$

Circuit: Basic diff. amp:

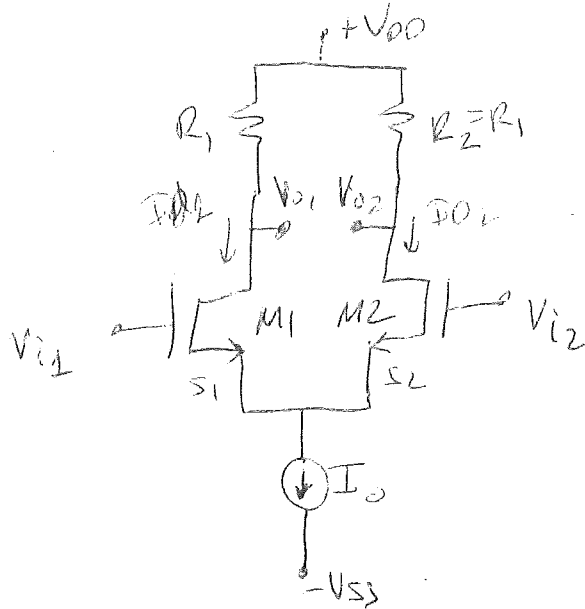
→ Source-coupled diff. amp (w/ resistive load)



* M_1, M_2 are identical
same k, V_T

* DC analysis:

(No small signal $V_{i1} = V_{i2} = 0V$)

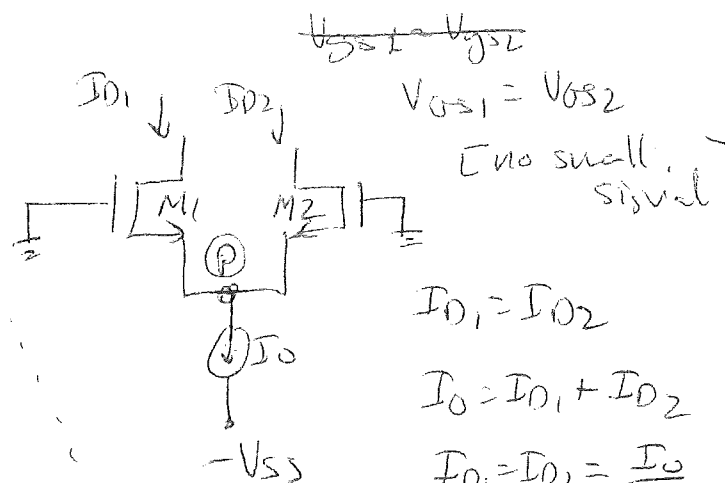

$$I_{D1} = I_{D2}$$

$$I_0 = I_{D1} + I_{D2}$$

$$I_{D1} = I_{D2} = \frac{I_0}{2}$$

whether or not
 $R_1 = R_2$

Small-signal analysis: (1) → diff mode
* signal analysis (2) → common mode

① Strictly diff mode operation:

$$\begin{aligned} \text{make } V_{i1} &= -V_{i2} \\ V_d &= V_{i1} - V_{i2} \\ V_d &= \frac{1}{2}V_d - (-\frac{1}{2}V_d) = V_d \end{aligned}$$

If $V_d > 0$: I_{D1} will increase from its Q-point value by ΔI_{D1}

$$I_{D1} = \frac{1}{2} I_0 + \Delta I_{D1}$$

$$I_{D2} = \frac{1}{2} I_0 - \Delta I_{D2}$$

I_{D2} will decrease from its Q-point value.

And $V_{01} = V_{DD} - R_1 I_{D1}$

$V_{02} = V_{DD} - R_1 I_{D2}$

$$V_{01} - V_{02} = -R_1 (I_{D1} - I_{D2})$$


$$V_{01} - V_{02} = -R_1 (2 \Delta I_{D1})$$

② Strictly common mode input.

$$V_{i1} = V_{i2} = V_{CM}$$

$$V_{CM} = \frac{1}{2} (V_{i1} + V_{i2})$$

← make it average of both inputs.

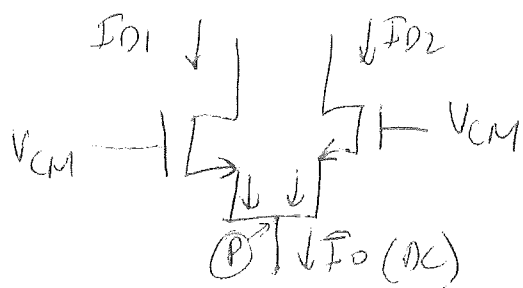

$$I_{D1} = \frac{1}{2} I_0 + \Delta I_{D1}$$

$$I_{D2} = \frac{1}{2} I_0 + \Delta I_{D2}$$

$$\Delta I_{D1} = \Delta I_{D2}$$

At node (P) $I_{D1} + I_{D2} = I_0$

$$I_{D1} = \frac{1}{2} I_0 + \Delta I_{D1}$$

$$I_{D2} = \frac{1}{2} I_0 + \Delta I_{D1}$$

$$I_{D1} + I_{D2} = I_0 + 2 \Delta I_{D1}$$

But $I_{D1} + I_{D2} = I_0$

$\therefore \Delta I_{D1} = 0$ (only possible solution)

\therefore No change in the outputs V_{o1} or V_{o2}


\therefore Common mode gain = 0. \rightarrow Ideal diff. amp.

$$A_{CM} = 0$$

What happens when not ideal \rightarrow Friday.

10/14/2016

Madhu Satish

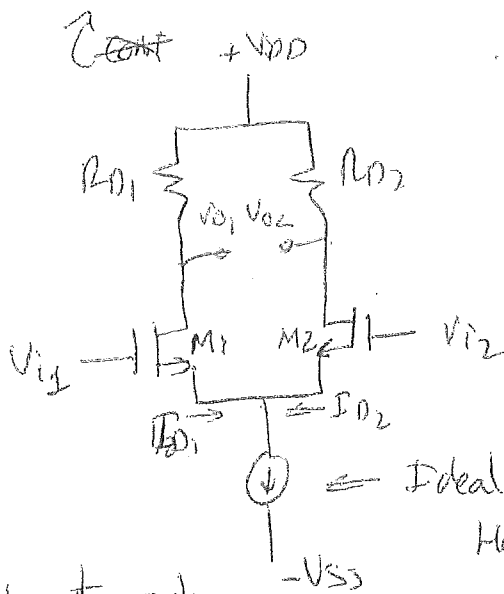

$M1, M2$: identical

$RO1$ may not be equal to $RO2$

How to solve:

① DC analysis (no signals), find Q-points.

$$ID_1 = ID_2 = \frac{1}{2} I_0 \quad (\text{regardless of } RO_1, RO_2 \text{ being equal})$$

Calculate V_{O1} and V_{O2} at Q-point.

Calculate g_m .

② Small-signal analysis

Find \rightarrow (a) Differential mode gain

$$V_{i1} = -V_{i2} = \frac{1}{2} V_d$$

Find \rightarrow (b) Common mode gain.

$$V_{i1} = V_{i2} = V_{cm}$$

For general input situation:

$$V_o = A_d \cdot V_d + A_{cm} \cdot V_{cm}$$

$$V_d = V_{i1} - V_{i2}$$


$$V_{cm} = \frac{1}{2} (V_{i1} + V_{i2})$$

Ideal diff. amp:

R_o of current source $\rightarrow \infty$

$$\therefore A_{cm} = 0$$

Example 1

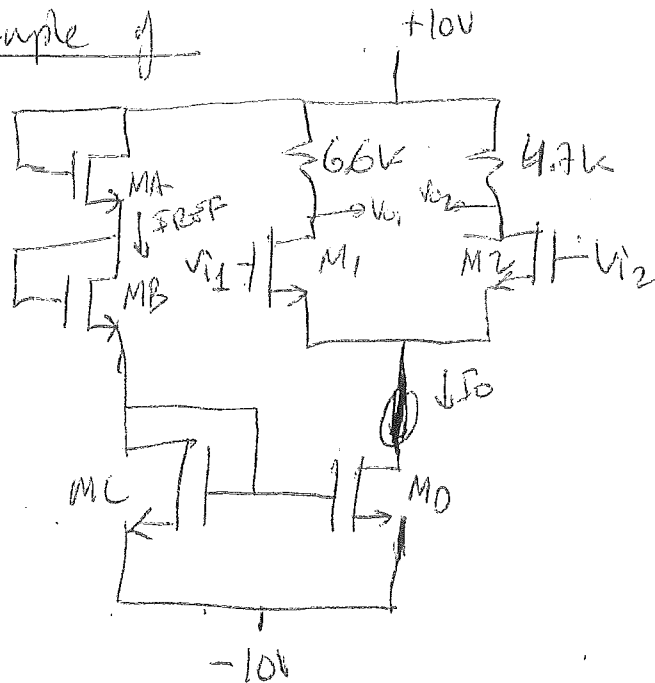
$$\left. \begin{array}{l} K = 15 \mu A/V^2 \\ V_T = 0.3V \end{array} \right\} \text{ for all transistors}$$

⑤ M_A, M_B, M_C, M_D make up the current source
→ Basic current mirror with two additional transistors.

DC M_A, M_B, M_C are identical and same current I_{prof} flows through them.

V_{GS} must be the same for M_A , M_B , M_C .

Total voltage available: $20V$, $\therefore V_{GS} = \frac{20V}{3} = 6.67V$

$$\therefore I_{DOP} = \frac{1}{2} (18 \text{ mA/V}) (V_{DD} - 0.8)^2$$

$$I_{R_{OP}} = 1.72 \text{ mA} = I_0$$

At Q-point (meaning that $v_{i1} = v_{i2} = 0$)

$$I_{O1} = I_{O2} = \frac{1.72 \text{ mA}}{2} = 0.8605 \text{ mA} = \frac{I_o}{2} = \frac{I_{\text{REF}}}{2}$$

$$\underline{V_{OS1}}: \quad 0.8605 \text{ mV} = \frac{1}{2} (0.1 \text{ mV/V}^2) (V_{OS1} - 0.8)^2$$

2 17.21
Nov 4, 202

$$V_{ow} = 4.14$$

$$V_{GS} - V_T = 4.14$$

VSS = 24.940

$$\rightarrow V_{GS1} = 4.948 \text{ V}$$

And $g_{m2} = k(V_{GS} - V_T) = 0.1 \text{ mA/V}^2 (4.948 - 0.8)$

1 gms = 0.4148 m \$

10/14/2016
(3)

→ identify saturation operation of M_0 .
(M_A, M_B, M_C always in sat.)

Want V_{GD} of $M_0 < 0.8V$

$$V_{DS_D} > (V_{GS_D} - V_T)$$

→ V_{GS} of $M_0 = V_{GS}$ of M_C

$$V_G \text{ of } M_0 = -10 + V_{GS} = -10 + (6.667) = -3.33V$$


$$\rightarrow V_D \text{ of } M_0 = 0 - V_{GS1} = 0 - 4.948V \rightarrow ? \quad V_D = 4.948V$$

$$V_{GD} \text{ of } M_0 < 0.8V \rightarrow ?$$


$$V_{GD} = V_G - V_D = -3.33V - (-4.948V) = 1.61$$

Small-signal analysis.

Q point $V_{I1} = V_{I2} = 0$

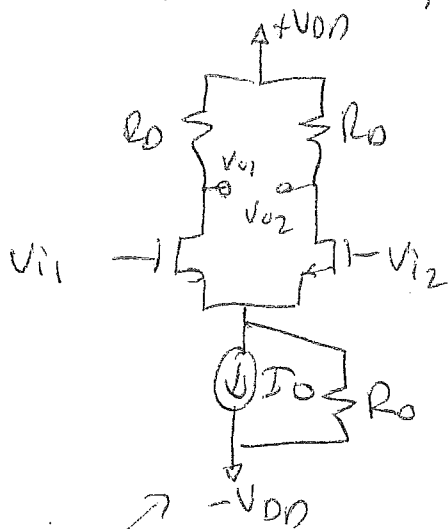

Non-ideal current source.

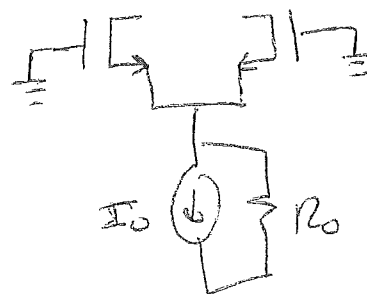

$$I_{D1} + I_{D2} = I_0 - I_{R_0}$$


$$I_{R_0} \ll I_0$$

Ignore I_{R_0} at Q-point

$$\therefore I_{D1} = I_{D2} = \frac{1}{2} I_0 \text{ at Q-point}$$

Diff. mode analysis

$$V_{i1} - V_{i2} = v_d$$

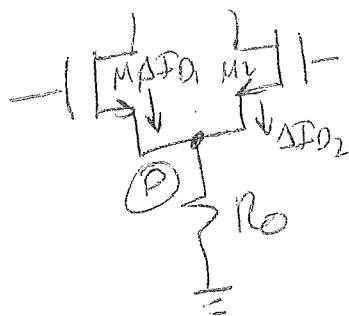


$\Delta I_{D1} = -\Delta I_{D2}$ \therefore no current flows through R_O .
 $I_{R_O} \rightarrow 0$ for diff. mode.

\rightarrow Diff. mode \rightarrow voltage at (P) is not affected since no current in R_O .


\therefore (P) acts as an a.c. ground.

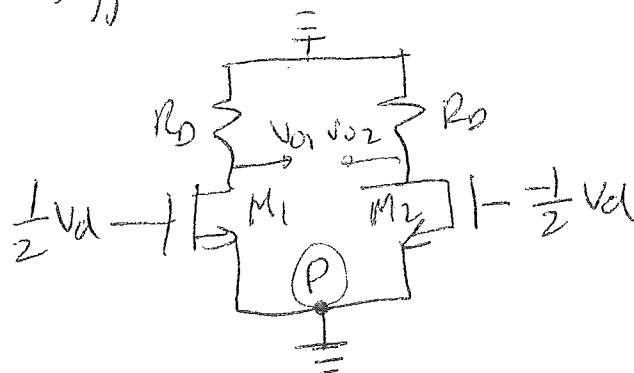\rightarrow Diff. mode \rightarrow ckt can be changed to:




\leftarrow two halves look the same. Only sign of input voltage is different.
 Find output voltage of $1/2$ half and change sign for other half.

\rightarrow One-half of Diff. amp.

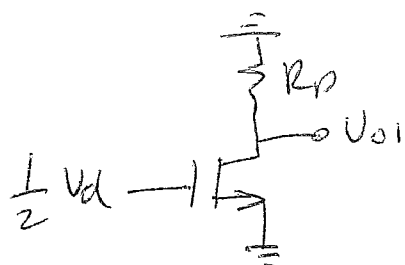

\uparrow
CS amplifier.

\Rightarrow
Small signal model

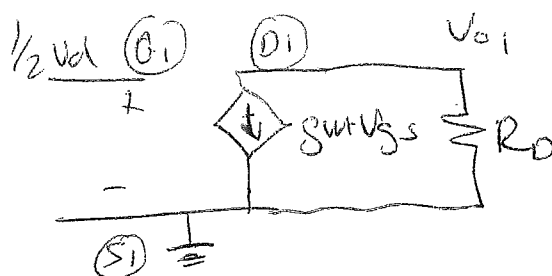

$$\frac{v_{o1}}{v_{gs1}} = -g_{m1} R_O$$

$$\frac{v_{gs1}}{v_d} = \frac{1}{2}$$

6/14/2016

(4)

$$A_d (\text{single-ended}) = \frac{V_{o1}}{V_d} = -\frac{1}{2} g_m R_{o1}$$

Other half:

$$\frac{V_{o2}}{V_d} = \frac{1}{2} g_m R_{o2}$$

$$A_d (\text{double-ended}) = \frac{V_{o1} - V_{o2}}{V_d} = -g_m (R_{o1} - R_{o2})$$


$$A_d = -g_m (R_{o1} - R_{o2})$$

↑
double ended

END ↑

START ↓

Common-mode analysis

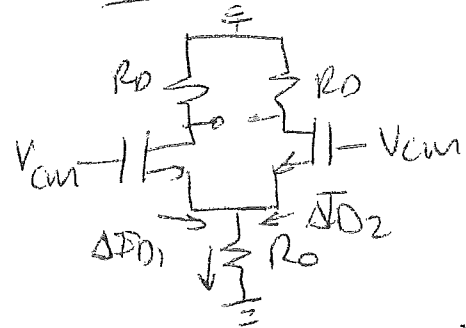


$$\Delta I_{D1} = \Delta I_{D2}$$

$\Delta I_{D1} + \Delta I_{D2}$ same sign.


$$\therefore \Delta I_{D1} + \Delta I_{D2} = I_{R_o} \neq 0$$

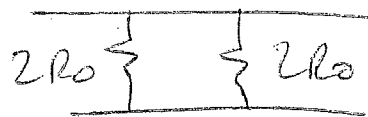→ Cannot cut ckt in half as is.
But Replace R_o with $2R_o$ and divide
in $1/2$.




New lecture:


DIFF AMP

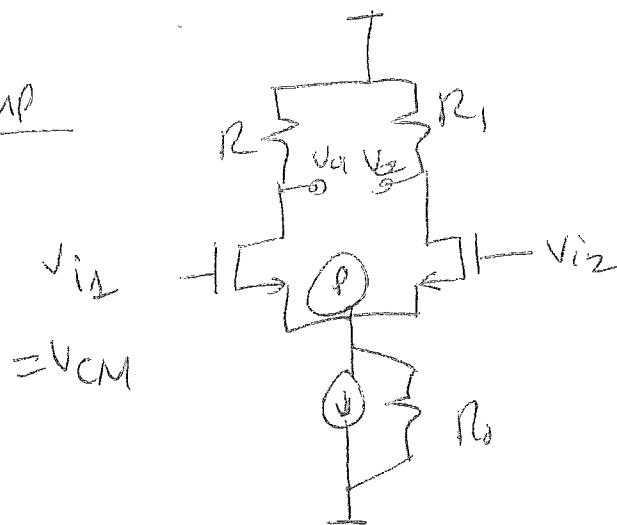

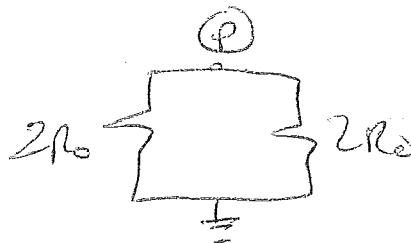
Common-mode analysis - $I_{Source} \rightarrow$ open
 $V_{Source} \rightarrow$ shorted.



One-half diff amp:

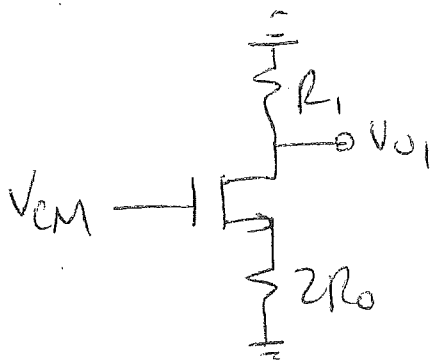

\Rightarrow small signal

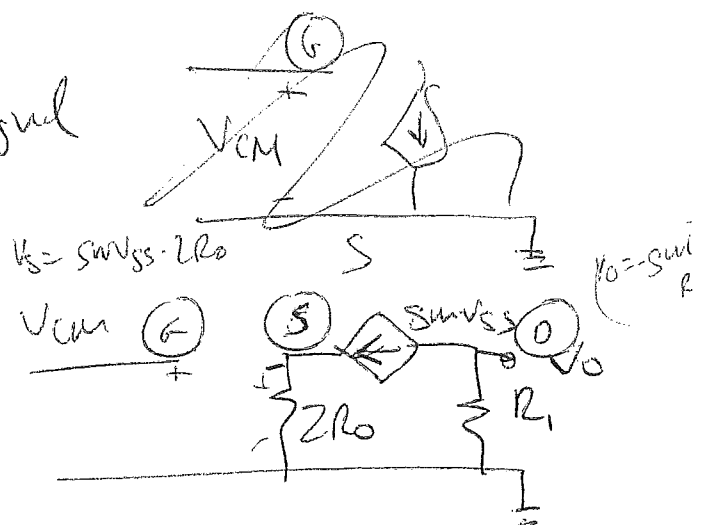

$$\frac{V_0}{V_{gs}} = -gmR_1$$

$$V_{gs} = V_{cm} - 2R_0(gmV_{gs})$$

$$V_{gs}(1 + 2gmR_0) = V_{cm}$$

$$\frac{V_{gs}}{V_{cm}} = \frac{1}{1 + 2gmR_0}$$


$$\therefore A_{cm} = \left(\frac{V_0}{V_{gs}} \right) \left(\frac{V_{gs}}{V_{cm}} \right) \ll 1$$

↳ $CMRR = 20 \log \left(\frac{A_{ol}}{A_{cm}} \right)$

CMRR can be made large
by increasing R_o

Actively loaded D.I. Amp.

PMOS FETs $\rightarrow I_D = \frac{1}{2} \underbrace{\mu_p C_{ox} \left(\frac{W}{L} \right)}_{K_p} (V_{SG} - |V_T|)^2$

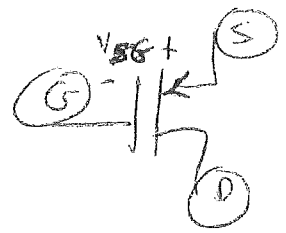

Saturation condition: $V_{DG} < |V_T|$

$V_{SD} \geq V_{SG} - |V_T|$


1. $V_D \geq V_G - |V_T|$

$-V_D + V_G \geq |V_T|$

$V_{GD} \geq -|V_T|$

$V_{DG} < |V_T|$

single
Typical PMOS ap.

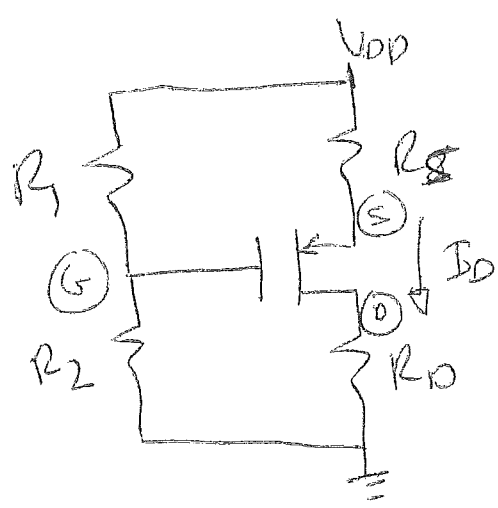

$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$

$V_G + V_{SG} + R_3 I_D = V_{DD}$

$V_G + V_{SG} + R_3 \frac{K_p}{2} (V_{SG} - |V_T|)^2 = V_{DD}$


→ Solve for V_{SG} .

→ Find I_D

→ Find V_D

check $V_{GD} = V_G - V_D < V_T$

Example:

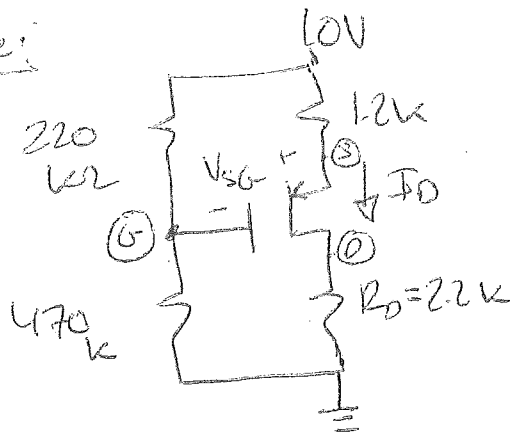

$$K_p = 1.2 \text{ mA/V}^2 \quad V_T = -0.85 \text{ V}$$

$$V_G = \left(\frac{470}{470 + 220} \right) 10 = 6.812 \text{ V}$$

KVL equation:

$$10 - 1.2k I_D - V_{SG} = V_G$$

$$10 - 1.2 \left[\frac{1}{2} \cdot 1.2 \frac{\text{mA}}{\text{V}^2} (V_{SG} - 0.85)^2 \right] - V_{SG} = 6.812$$

$$10 - 0.72 V_{SG}^2 + 1.224 V_{SG} - 0.5202 - V_{SG} = 6.812$$

$$\boxed{V_{SG} = 2.087 \text{ V}}$$

$$\therefore I_D = 0.6 (2.087 - 0.87)^2 = 0.9206 \text{ mA}$$

$$\boxed{V_D = R_D I_D = (2.2k)(0.9206 \text{ mA}) = 2.025 \text{ V}}$$

But $V_{GD} < V_T$? $V_G - V_D = 6.812 - 2.025 = 4.787 \text{ V}$

\therefore Make $R_D = 8k$.

$$\text{Then } V_D = 8k(0.9206 \text{ mA}) = 7.365 \text{ V}$$

$$\text{And } V_{GD} = 6.812 - 7.365 = -0.553 < 0.85$$

And saturation!

→ CMOS Diff Amp stage


→ w/ load resistance → small gain due to ~~large~~ finite R -value.

→ Increase gain by increasing R_D .
Use mosfet as load to increase gain as effective R_D is large.

2 possibilities

NMOS vs. PMOS

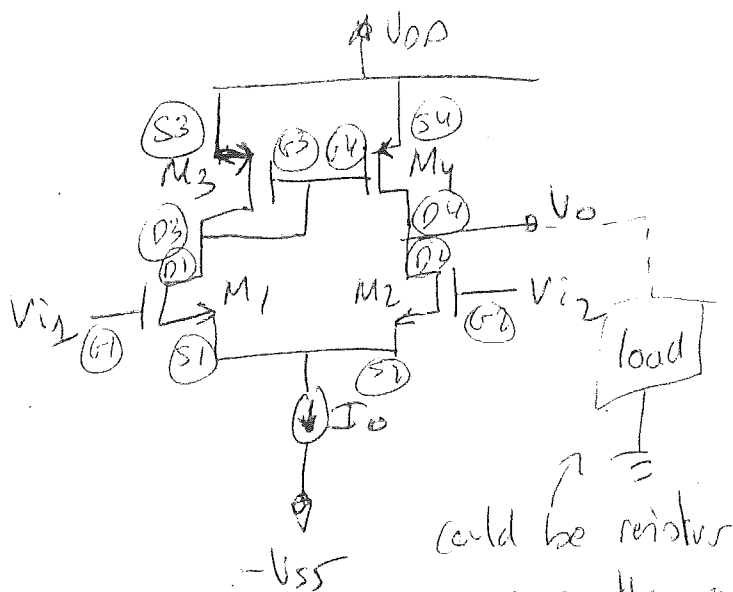- (1) Drive transistors: receives input signal
- (2) Load transistors: output taken at the drain of \pm I's.



Drive transistors: M_1, M_2 (NMOS)

Load transistors: M_3, M_4 (PMOS)

could be resistor
or another amplifying
stage

Current follows the arrows

of MOSFETS

M_1, M_2 are identical → same k_n and same V_T

M_3, M_4 are identical → " " " " "


→ often all 4 identical which requires width of PMOS to be $\sim 4\times$ larger than NMOS.

Q-point (DC analysis)

10/19/2016

Machmu

$$V_{i1} = V_{i2} = 0V$$

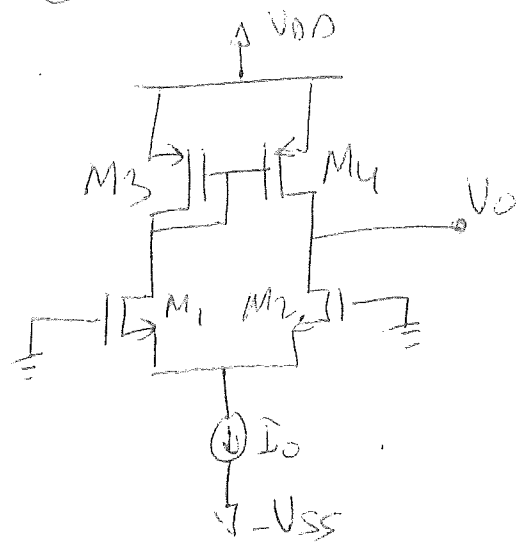

Note: $V_{GS1} = V_{GS2}$

$$M_1 = M_2$$

$$\therefore I_{D1} = I_{D2} = \frac{I_O}{2}$$

I_O is known.

Find V_{GS1} and V_{GS2} from $\frac{I_O}{2}$

M_3 in series w/ M_1

$$\therefore I_{D3} = I_{D1} \rightarrow \text{Find } V_{GS3}$$

M_2 in series w/ M_4

$$\therefore I_{D4} = I_{D2} \rightarrow \text{Find } V_{GS4}$$

when circuit is perfectly balanced. $\leftarrow \therefore$ No current to the load at Q-point

\rightarrow Find $g_{m1}, g_{m2}, g_{m3}, g_{m4}$ and $r_{o1}, r_{o2}, r_{o3}, r_{o4}$ } From α -point analysis.

Note: $g_{m1} = g_{m2}$ and $g_{m3} = g_{m4}$

$$r_{o1} = r_{o2}$$

$$r_{o3} = r_{o4}$$


Small-signal analysis - Diff mode

→ Cannot analyze only one-half of circuit.

$$\rightarrow V_{i1} = \frac{1}{2} v_d \quad v_{i2} = -\frac{1}{2} v_d$$


→ Small signal eq. circuit.

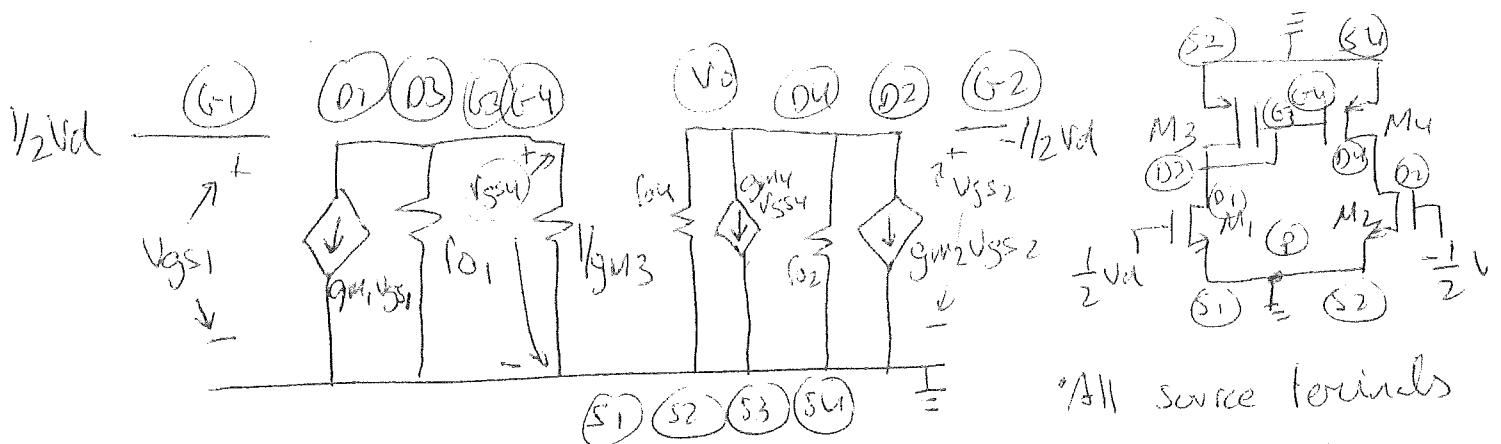- * Node (P) is ac. ground
- * Ground power supplies
- * Start of ground line



$$V_{GS1} = \frac{1}{2} v_d$$

$$V_{GS2} = -\frac{1}{2} v_d$$

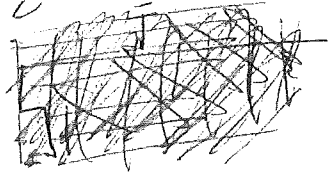

→ Find $V_{GS4} = -g_{m1} V_{GS1} \left(r_{o1} \parallel \frac{1}{g_{m3}} \right)$

$$V_{GS4} = -g_{m1} V_{GS1} \left(\frac{1}{g_{m3}} \right)$$

$$V_{GS1} = \frac{1}{2} v_d \rightarrow$$

$$V_{GS4} = -\frac{1}{2} \frac{g_{m1}}{g_{m3}} v_d$$

- * All source terminals are ground.
- * Diode connected $\rightarrow 1/g_m = R$

$$r_o \rightarrow 100k \Omega$$

$$g_m \rightarrow mS$$

$$\therefore \frac{1}{g_{m3}} \ll r_{o1} \frac{1}{g_{m1}}$$

→ ignore r_{o1} in parallel combination

cont'd 2

Eqn's

10/10/2016
Module 2

$$V_o = -(g_{m4} V_{gs4} + g_{m2} V_{gs2}) (r_{o2} \parallel r_{o4}) = V_o$$

$$V_o = - \left[g_{m4} \left(-\frac{1}{2} \frac{g_{m1}}{g_{m3}} V_d \right) + g_{m2} \left(-\frac{1}{2} V_d \right) \right] (r_{o2} \parallel r_{o4})$$

$$V_{gs2} = -\frac{1}{2} V_d$$

$$V_{gs4} = -\frac{1}{2} V_d \frac{g_{m1}}{g_{m3}}$$

(from before)

$$g_{m4} = g_{m3}$$

and

$$g_{m1} = g_{m2}$$


$$V_o = \left(\frac{1}{2} g_{m1} + \frac{1}{2} g_{m2} \right) V_d (r_{o2} \parallel r_{o4})$$

$$V_o = g_{m2} V_d (r_{o2} \parallel r_{o4})$$


→ $r_{o2} + r_{o4}$ we
have larger than resistor
and smaller. Large
gains can be
obtained.

⇒ Ckt eq:

$g_{m2} V_d$

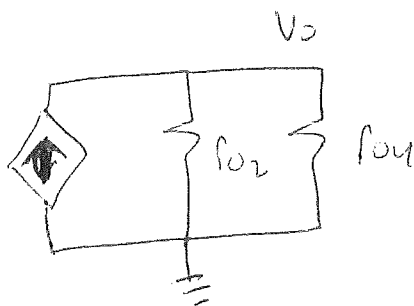

only right half of circuit.

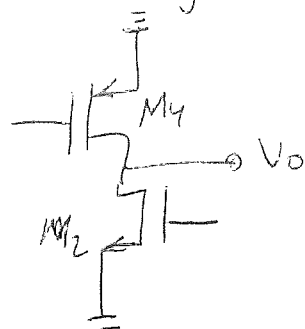


→ only the two transistors
connected to V_o .
Right hand side.

→ Common-mode mode complex to derive formula

→ What happens when a load is added

END

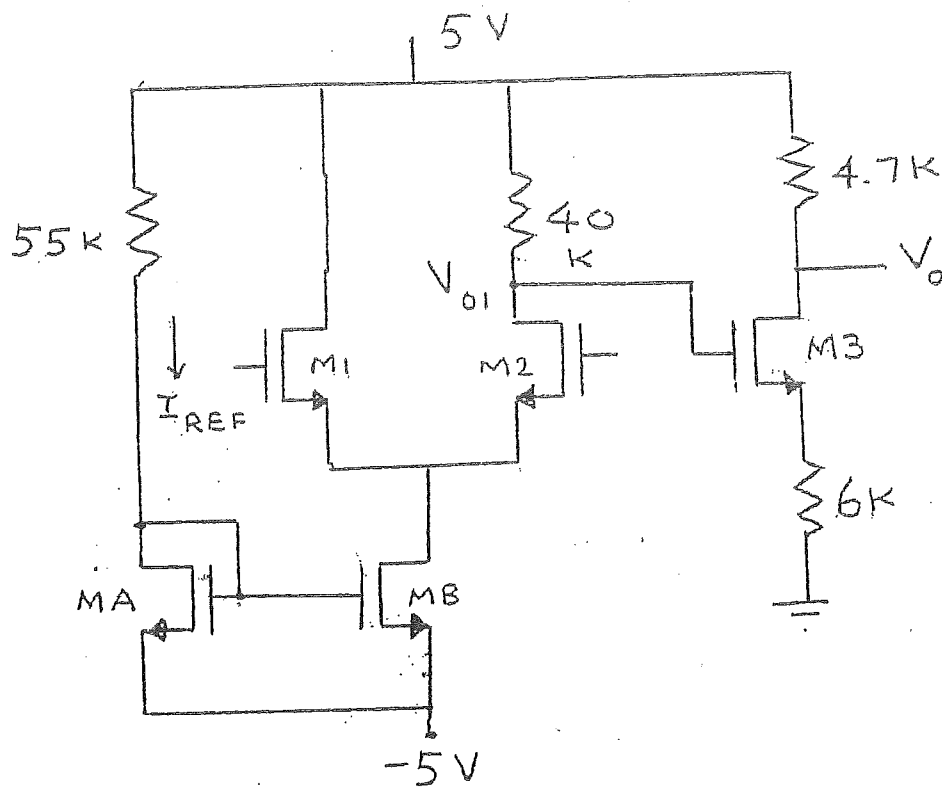


$$k_n = 0.2 \text{ mA/V}^2$$

$$V_T = 1.2 \text{ V}$$

$$\lambda = 0.01 \text{ V}^{-1}$$

DIFFAMP (RESISTIVE LOAD)

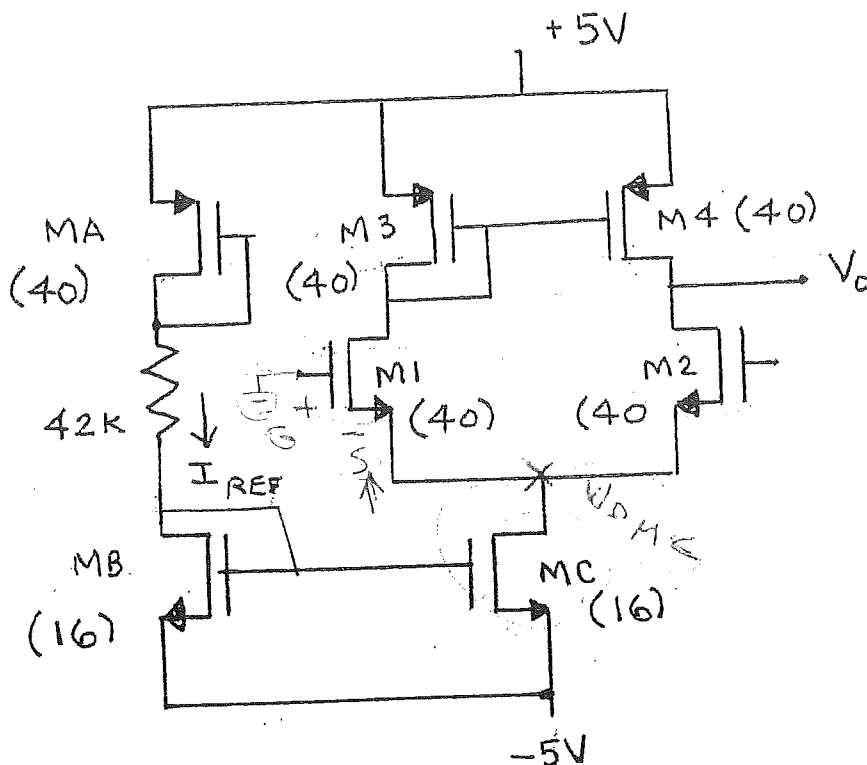

$$\mu_n C_{ox} = 0.05 \text{ mA/V}^2$$

$$\mu_p C_{ox} = 0.02 \text{ mA/V}^2$$



$$|V_T| = 1.1 \text{ V}$$

$$\lambda = 0.01 \text{ V}^{-1}$$

NEW 10/21/2016
LECTURE.

→ DIFF. AMP EXAMPLE.

① DC analysis

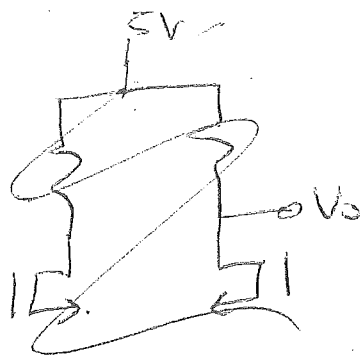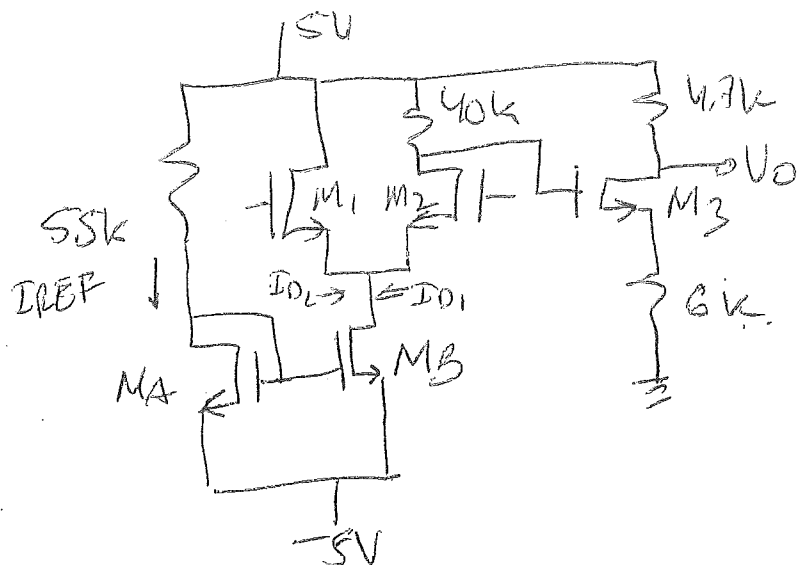

$$\begin{aligned} \mu &= 0.2 \text{ mA/V}^2 \\ V_T &= 1.2 \text{ V} \\ \lambda &= 0.01 \text{ V}^{-1} \end{aligned}$$

$$5 - 55k \cdot I_{REF} - V_{OS1} - (-5) = 0$$

$$5 - 55k \cdot \frac{1}{2} (0.2 \text{ mA}) (V_{OS1} - V_T)^2 - V_{OS1} - (-5) = 0$$

$$5 - 5.5 V_{OS1}^2 + 13.2 V_{OS1} - 7.92 - V_{OS1} + 5 = 0$$

$$V_{OS1} = 2.377 \text{ V}$$

$$\text{And } I_{REF} = 0.1 (2.377 - 1.2)^2 = 0.1385 \text{ mA}$$

$$\therefore I_{D1} = I_{D2} = 0.06926 \text{ mA (irrespective of load resistor)}$$

$$V_{OS1}, V_{OS2} \Rightarrow 0.06926 = \frac{1}{2} (0.2 \text{ mA}) \underbrace{(V_{OS1} - V_T)^2}_{V_{OV}^2}$$

$$V_{OV} = \sqrt{\frac{2 \times 0.06926 \text{ mA}}{0.2 \text{ mA}}}$$


$$\text{and } V_{OS1} = V_{OS2} = 2.032 \text{ V}$$

Cont'd →

Cont'ds
→ Find V_{DS3} at $M3$

6/21/2016

Mogaku

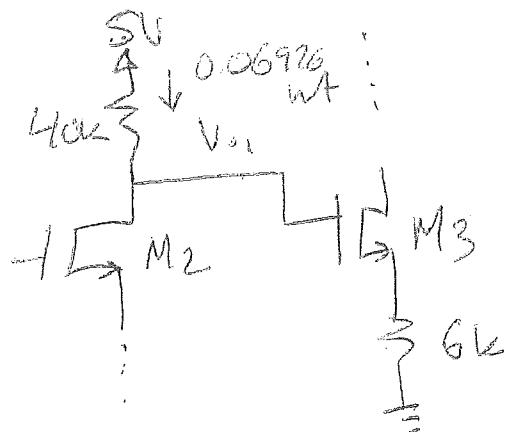

$$V_{O1} = 2.229V$$

$$2.229V - V_{DS3} - 6 \cdot I_{D3} = 0$$

$$2.229 - V_{DS3} - 6 \left(\frac{1}{2} 0.2 \mu A/V (V_{DS3} - V_T)^2 \right) = 0$$


$$2.229 - V_{DS3} - 0.6 V_{DS3}^2 + 1.44 V_{DS3} - 0.864 = 0$$

Solving polynomial $\rightarrow V_{DS3} = 1.919V$

and $I_{D3} = 0.0517 \mu A$

→ Check for saturation:

M_B : In DC M_1 & M_B are grounded.

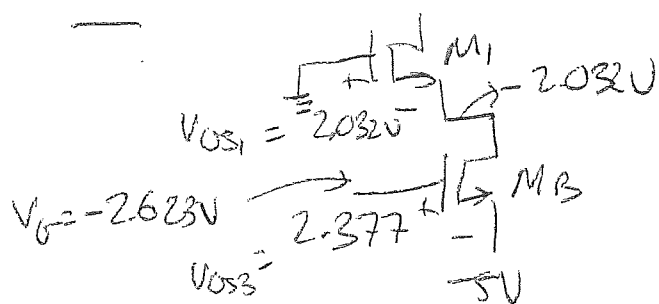

V_{GS} of M_B

$$= -2.623 + 2.032$$

$$= -0.591 < V_T \quad \text{OK}$$

or V_{DS} of M_B

$$V_{DS} = 5 - 2.032 = 2.9 > 2.377 - 1.2$$

$$V_{DS} > V_{GS} - V_T$$

OK

$$M_2: V_{DS2} = 2.229V$$

$$V_{GS2} = 0$$

$$V_{DS2} = -2.229 < V_T \quad \text{OK}$$


$$\cancel{V_{DS3} = 1.919V}$$

$$M_3: V_{DS3} = 2.229V$$

$$V_{DS3} = 5 - 4.7(0.0517) = 4.757V$$

$$V_{DS3} = -2.528V < V_T$$

OK

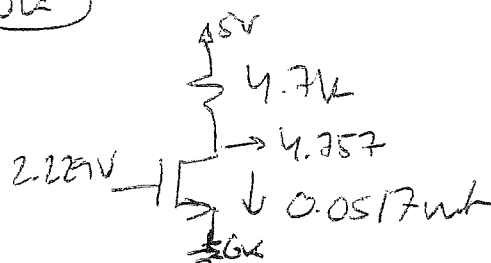

Small-signal


Need g_{m2} and g_{m3}

$$g_{m2} = 0.2 \text{ mA/V} (2.032 - 1.2) = 0.1664 \text{ mS}$$

$$g_{m3} = 0.2 \text{ mA/V} (1.919 - 1.2) = 0.1438 \text{ mS}$$

Diff. mode small-signal analysis:

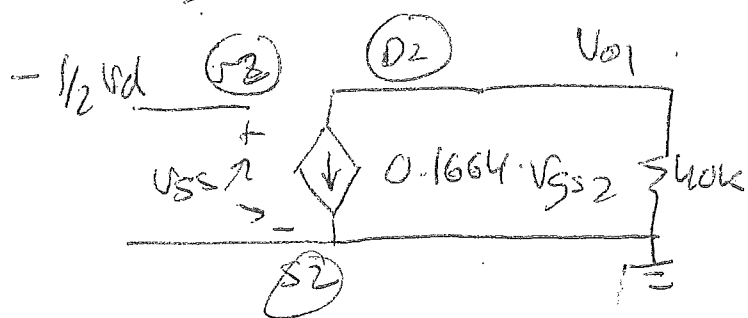
\rightarrow M2 stage and M3 stage. $V_{o1} = -g_{m2} \cdot R_D$



$$\frac{V_{o1}}{V_{ss2}} = -40k \cdot 0.1664 \text{ mS}$$

$$\frac{V_{o1}}{V_{ss2}} = -6.656$$

M3 stage

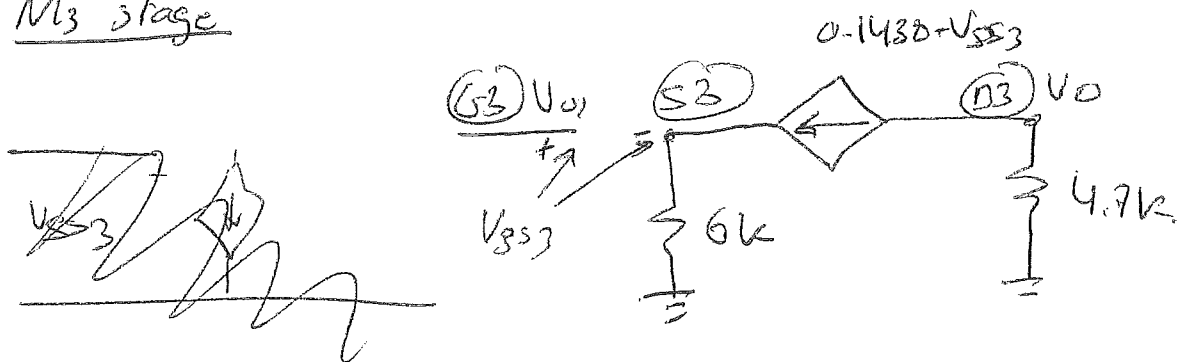

C-S stage w/o bypass across $6k$.

$$\frac{V_o}{V_{ss3}} = -0.1438 \times 4.7 = -0.6759$$

$$\frac{V_o}{V_{ss3}} = -g_{m3} \cdot 4.7k$$

$$\frac{V_{ss3}}{V_{ss3}} = \frac{1}{1 + g_{m3} \cdot 6k}$$

$$\frac{V_{ss3}}{V_{ss3}} = \frac{1}{1 + 0.1438 \times 6} = 0.5368$$

$$\frac{V_{ss3}}{V_{o1}} = 1$$

\therefore M3 stage gain:

$$(-0.6759)(0.5368)(1) = -0.3628$$

conf'd 7

Contr's⁹ Knowing

10/21/2020
Madhu C

$$\rightarrow \frac{V_{gs2}}{v_d} = -0.5 \quad \text{for } M_2 \text{ stage and } \frac{V_{o1}}{V_{ss2}} = -6.656$$

$$\rightarrow \left[\frac{V_o}{v_d} = (-0.3628)(-6.656)(-0.5) = -1.208 \right] \quad \downarrow$$

small gain due

to small gain values.

→ load resistances are low
→ w/ MOS loads → gains higher


Common-mode small-signal gain:

Need R_o of current source (M_B)

which is equal to $r_{o_{MB}} = \frac{1}{\lambda I_O} = \frac{1}{(0.01)(0.1385 \text{ mA})}$

$$r_o = R_o = 722 \text{ k}\Omega.$$

M_2 stage

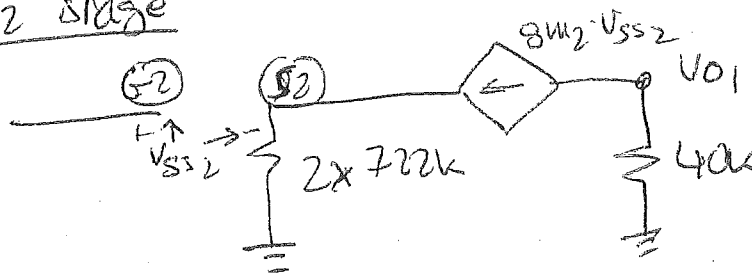

$$\frac{V_{o1}}{V_{ss2}} = -g_{m2} \cdot 40k$$

$$V_{ss2} = -0.1664 \text{ mA} (40k)$$

$$\frac{V_{o1}}{V_{ss2}} = -6.656$$

$$\frac{V_{gs2}}{V_{cm}} = 1$$

∴ Common-mode gain of M_2 stage.

$$A_v = \frac{V_{o1}}{V_{ss2}} \times \frac{V_{ss2}}{V_{gs2}} \times \frac{V_{gs2}}{V_{cm}} = 0.02759$$

$$\frac{V_{ss2}}{V_{gs2}} = \frac{1}{1 + g_m (2 \times 722k)}$$

$$\frac{V_{ss2}}{V_{gs2}} = \frac{1}{1 + (0.1664 \text{ mA})(2 \times 722k)}$$

$$\frac{V_{ss2}}{V_{gs2}} = 4.144 \times 10^{-3}$$

Common-mode gain of M_3 stage

→ same as before because it is not a diff stage.


$$A_{M_3} = -0.3628$$

$$\therefore A_{CM} = (-0.02754)(-0.3628) \approx 0.01$$


end lecture

start lecture. covers D.I. up w/ active load example.

→ using MOSFETs as load.

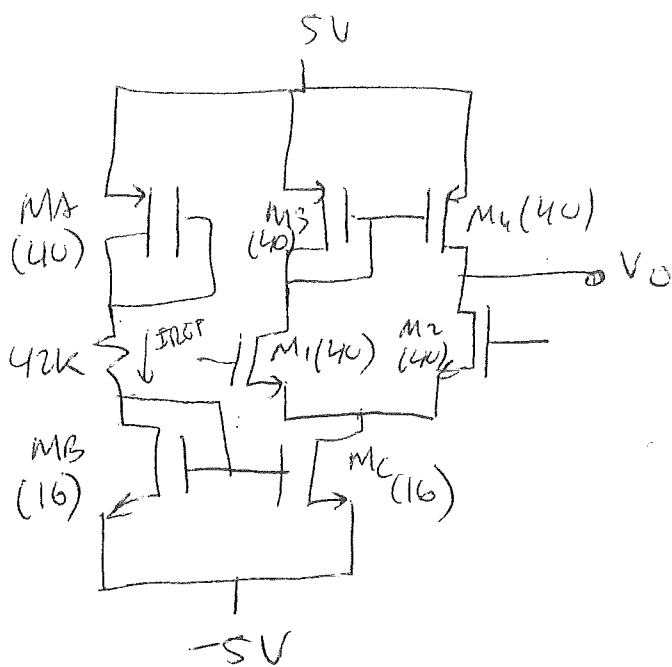

→ current source M_A , $42k$, M_B + M_C

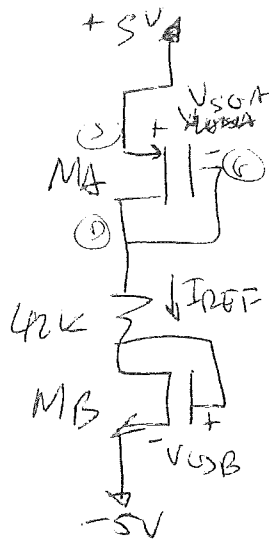

M_A : PMOS 0.02 mA/V^2

$$K_p = \mu_p C_{ox} \frac{W}{L}$$

$$K_p = (0.02)(40)$$

$$K_p = 0.8 \text{ mA/V}^2$$

M_B : NMOS

$$K_n = \mu_n C_{ox} \frac{W}{L}$$

$$K_n = (0.05)(16)$$

$$K_n = 0.8 \text{ mA/V}^2$$

$$5 - V_{SGA} - 42 \cdot I_{REF} - V_{GSB} = -5$$

$$\left. \begin{aligned} M_A \rightarrow I_{REF} &= \frac{1}{2} (0.8) (V_{SGA} - 1.1)^2 \\ M_B \rightarrow I_{REF} &= \frac{1}{2} (0.8) (V_{GSB} - 1.1)^2 \end{aligned} \right\} \therefore V_{SGA} = V_{GSB}$$

$$\text{Then} \rightarrow 5 - V_{GSB} - 42 \left(\frac{1}{2} (0.8) (V_{GSB} - 1.1)^2 \right) - V_{GSB} = -5$$

$$10 - 2V_{GSB} - 16.8V_{GSB}^2 + 36.96V_{GSB} - 20.33 = 0$$

$$V_{GSB} = 1.724 \text{ Volts} = V_{SGA}$$

$$\text{And } I_{REF} = \frac{1}{2} (0.8) (1.724 - 1.1)^2 = 1.558 \text{ mA}$$

Cont's 7

10/24/16
Madhu.

Cont'd
→ Current splits $\frac{1}{2}$ thru diff. pair:

$$I_{D1} = I_{D2} = \frac{I_{RSP}}{2}$$

$$I_{D1} = I_{D2} = 0.07788 \mu A$$


$$\rightarrow \text{and } 0.07788 \mu A = \frac{1}{2} (0.05 \text{ mA/V}^2) (40) (\underbrace{V_{GS1} - V_T}_{V_{OV}})^2$$

$$V_{OV} = V_{GS1} - 1.1 = 0.2791$$

$$V_{GS1} = 1.3791 \text{ V}$$

$$\rightarrow g_{m1} = g_{m2} = k_n (V_{GS1} - V_T) = \frac{0.2232 \text{ mA/V}}{0.05 \times 40} = 0.558 \text{ mS}$$

eq. circuit of diff amp

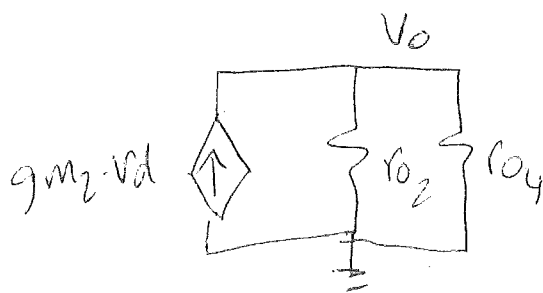

→ need r_{o2} and r_{o4} (right side of diff. amp circuit)

$$v_o = g_{m2} \cdot v_d \cdot (r_{o2} \parallel r_{o4})$$

$$r_o = \frac{1}{\lambda I_D}$$

1.28M

$$r_{o2} = \frac{1}{(0.07788 \mu A)(0.01 \text{ V}^{-1})} = 1284 \text{ k}\Omega$$

$$A_d = \frac{v_o}{v_d} = g_{m2} (r_{o2} \parallel r_{o4})$$

$$r_{o4} = r_{o2} = 1284 \text{ k}\Omega$$

$$\text{then } A_d = 0.558 \text{ mS} \left(\frac{1284 \text{ k}\Omega}{2} \right)$$

$$A_d = 358.2 \text{ V/V}$$

common-mode:

$$A_{CM} = -\frac{1}{2g_{m3}R_o}$$

$$g_{m3} = k_p (V_{GS} - V_T) = 0.352 \text{ mA/V}$$

$$R_o = 6418 \text{ k}\Omega$$

$$A_{CM} = -22 \text{ mV/V} \quad \text{CMRR} = 104.24 \text{ dB}$$

Cont'd in next sheet

CONTINUES FROM COMMON-MODE ANALYSIS

OR

PREVIOUS EXAMPLE

10/24/16

1A

$$\frac{V_0}{V_{SS}} = g_{m1} R_1$$

$$k_p = 40(0.02) (V_{O3} - V_T)$$

$$0.07788 \mu A = \frac{1}{2} 0.8 (V_{O3} - V_T)^2$$

$$\frac{0.07788}{0.4} = V_{OV}^2$$

$$V_{OV} = 0.441 V \rightarrow V_{O3} = 0.441 + 1.1 = 1.54 V$$

$$\rightarrow g_{m3} = 0.8 (0.441) = 352.8 \mu S \quad 0.3528 mS$$

$$\rightarrow R_0 = \frac{1}{\lambda I_D} = \frac{1}{0.01 \cdot 0.1558 \mu A} = 641.8 k\Omega$$

7
10C

$$A_{cm} = - \frac{1}{457.9} = -2.2 mV/V$$


$$CMRR = 20 \log \frac{358.2 V/V}{0.0022 V/V} = 104.24 dB$$

HW#6 - ~~9.1, 9.5, 9.6~~ 9.1, 9.5, 9.6 ← (Problems)


(Chapter Exercises → 9.5 (page 611), 9.17 (page 648), 9.20 (page 657)

Another example.

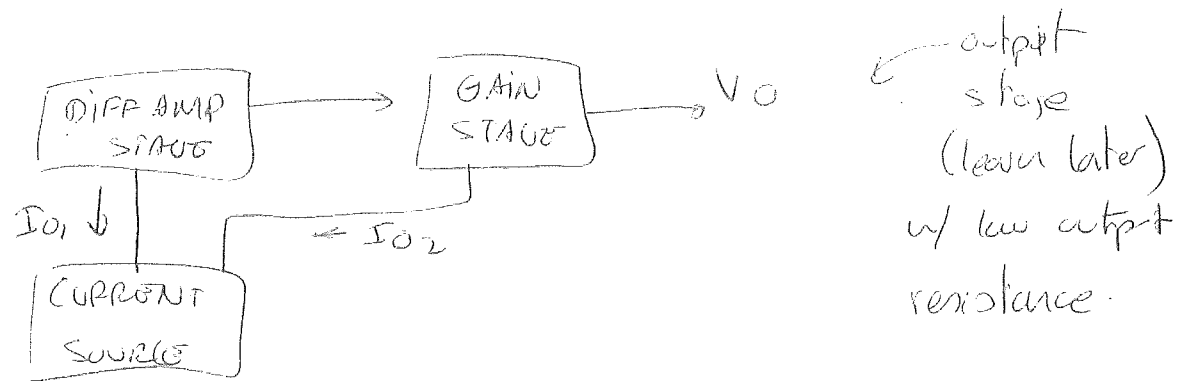→ 2-stage CMOS op-AMP { → with feedback loop }
(DIFF AMP)




Gain stage → output from diff. amp

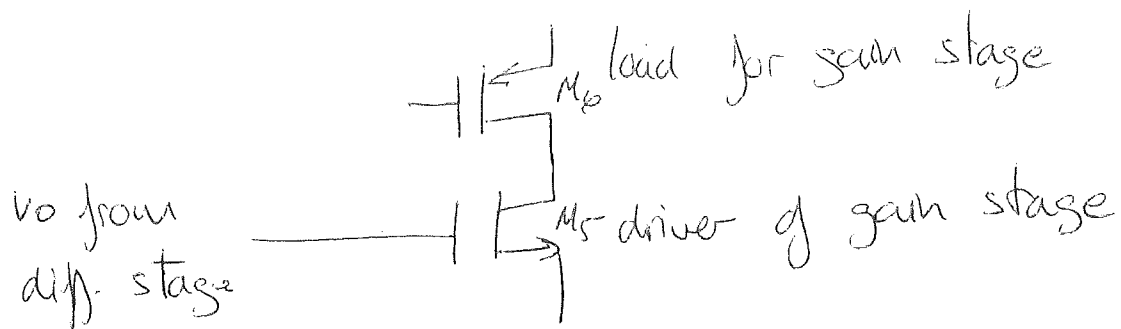

→ load on M_S is r_{o6} of M_P load. (large gains)

→ gain is $\propto (g_{m5} \text{ and } r_{o6})$

→ common source amplifier.

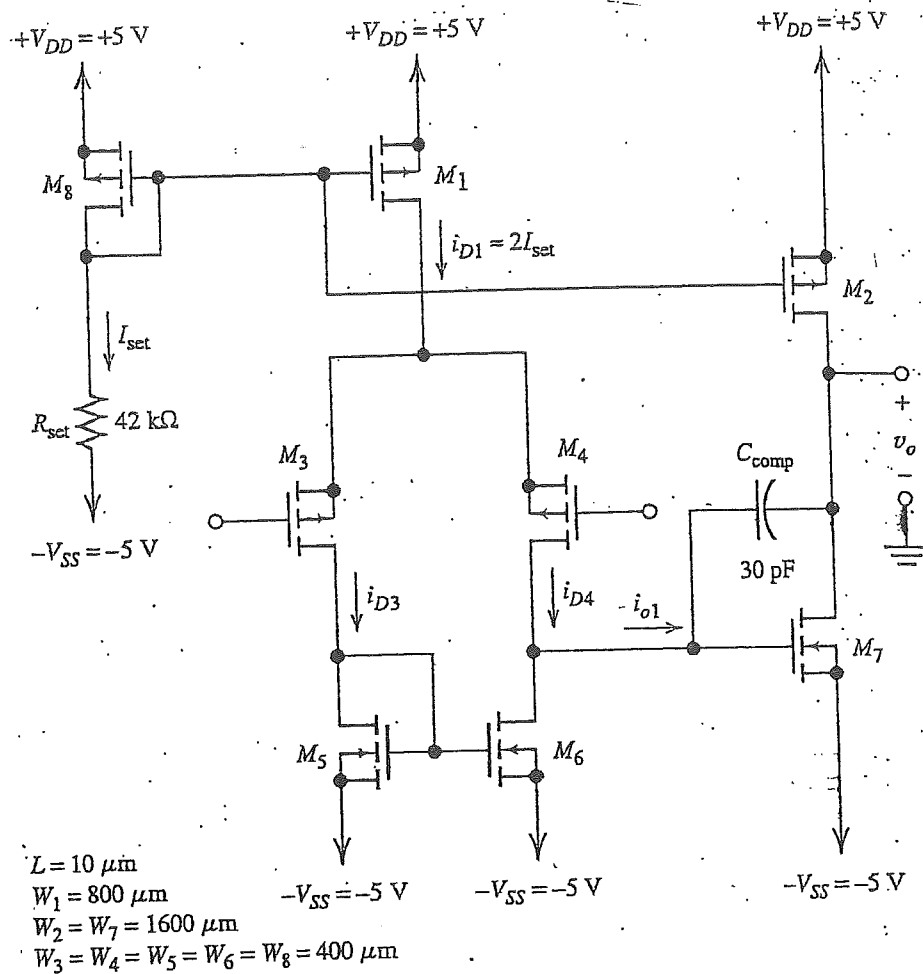

$$\mu_p C_{ox} = 0.025 \text{ mA/V}^2$$



$$\mu_n C_{ox} = 0.05 \text{ mA/V}^2$$

$$|V_T| = 1 \text{ V}$$

$$\lambda = 0.01 \text{ V}^{-1}$$

Basic CMOS Op Amp

10/24/2016
Madhu. (2)

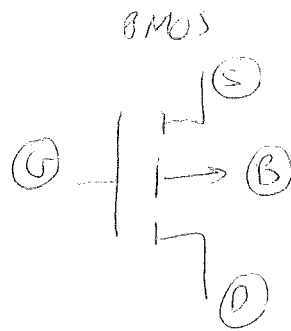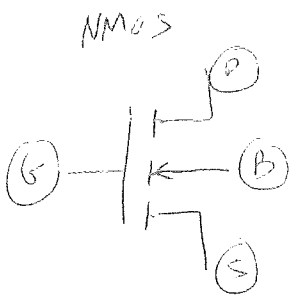


Arrow always goes from P \rightarrow N.

→ Basic CMOS gap example.

NMOS : M5 M6 M7
PMOS : M1 M2 M3 M4 M8

Re-draw w/ basic MOS symbols.

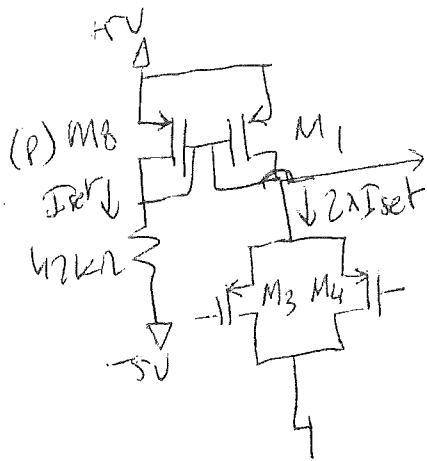

→ M1 : $K = 0.025(40) = 1 \text{ mA/V}^2$
 $V_T = 1 \text{ V}$

KVL: $5 - V_{S08} - I_{set}(42k\Omega) - (-5) =$

$5 - V_{S08} - \frac{1}{2} \text{ mA/V}^2 (V_{S08} - 1)^2 + 5 = 0$


develop
step

$5 - V_{S08} - 21 V_{S08}^2 + 42(V_{S08} - 1) - 21 + 5 = 0$

$V_{S08} = 1.631 \text{ Volts}$

$I_{set} = \frac{1}{2} \text{ mA} (1.631 - 1)^2$
 $= 0.1991 \text{ mA}$

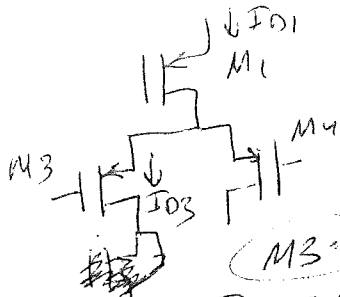→ M1: Current mirror of M3 but with ~~twice~~ the width. (same V_{OS})
 $I_{D1} = 0.3982 \text{ mA}$



→ $I_{03} = 0.1991 \text{ mA}$

$I_{03} = I_{04} = I_{05} = I_{06}$

$$\rightarrow (M2) \quad \frac{W}{L} = 160$$

$$I_{D2} = 4 \times I_{D3} = 4 \times I_{SET} = 4 \times 0.1991 \mu A = 0.7964 \mu A$$

$$I_{D2} = I_{D7}$$

Need: {

Diff pair {

- M_4 (driver of diff pair) $\rightarrow g_{m4} \rightarrow V_{GS4}$
- $r_{o4} \rightarrow I_{D4}$
- M_6 (load of diff pair) $\rightarrow r_{o6} \rightarrow I_{D6}$

Second stage {

- M_7 (driver) $\rightarrow g_{m7} \rightarrow V_{GS7}$
- $r_{o7} \rightarrow I_{D7}$
- M_2 (load) $\rightarrow r_{o2}$

$$\rightarrow (M4)_{PMOS} \quad I_{D4} = 0.1991 \mu A = \frac{1}{2} K_{P4} (V_{GS4} - 1)^2 = \frac{1}{2} (0.025 \mu A/V^2) \cdot \frac{400}{10} (V_{GS4} - 1)^2$$

$$0.1991 \mu A = \frac{1}{2} 1 \mu A/V^2 (V_{OV})^2$$

$$V_{GS4} = 1.631 V$$

$$g_{m4} = 1 \mu A/V^2 (1.631 - 1) = 0.631 \mu A/V$$

$$r_{o4} = \frac{1}{\lambda I_{D4}} = \frac{1}{0.01 V^{-1} \cdot 0.1991 \mu A}$$

$$r_{o4} = 502.3 k\Omega$$

$$\rightarrow (M6)_{NMOS} \quad r_{o6} = \frac{1}{\lambda I_{D6}} = \frac{1}{(0.01 V^{-1})(0.1991 \mu A)} = 502.3 k\Omega = r_{o6}$$

$$\rightarrow (M7)_{NMOS} \quad K_7 = 0.05 \mu A/V^2 \left(\frac{1600}{10} \right) = 8 \mu A/V^2$$

$$I_{D7} = 0.7964 \mu A = \frac{1}{2} 8 \mu A/V^2 (V_{OV7})^2$$

$$V_{OV} = 0.446 V$$

$$V_{GS7} = V_{OV} + 1 = 1.446 V$$

$$r_{o7} = \frac{1}{0.01 V^{-1} (0.7964 \mu A)} = 125.6 k\Omega$$

$$g_{m7} = \frac{8 \mu A}{V} (0.446) \rightarrow \frac{3.568 \mu A}{V}$$

10/26/2016
Madiha

Control


→ M2
PMOS

$$r_{o2} = \frac{1}{I_{D2} \lambda} = \frac{1}{(0.01V^{-1})(0.7964mA)}$$

$$r_{o2} = 125.6k\Omega$$

Diff. mode gain: A_d

→ Diff. op stage

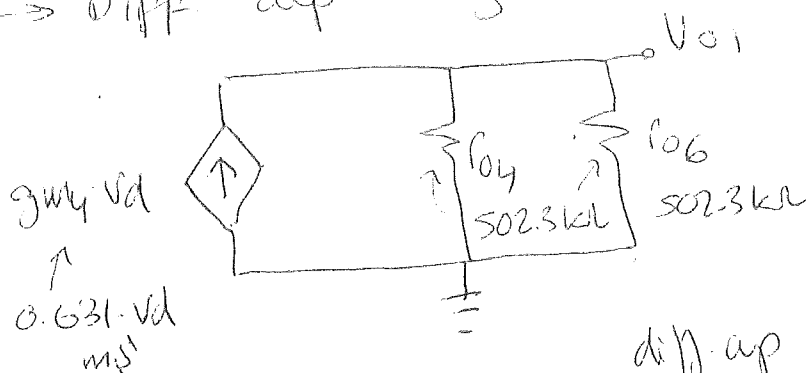

$$v_{o1} = g_{m4} \cdot v_d (r_{o4} \parallel r_{o6})$$

$$\frac{v_{o1}}{v_d} = A_d = (0.631) \left(\frac{502.3k\Omega}{2} \right)$$



diff. op
stage

$$\frac{v_{o1}}{v_d} = A_d = 158.5 \text{ V/V}$$

→ Second stage:

M2 and M7

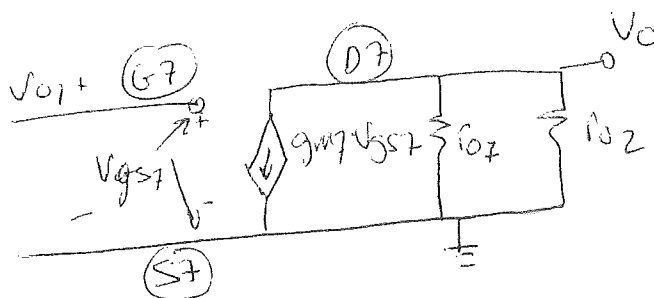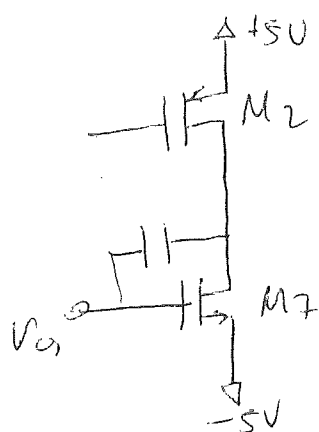→ capacitor acts as open in op-amp frequency.



$$g_{m7} = 3.568 \text{ mA/V}$$

$$r_{o7} = r_{o2} = 125.6k\Omega$$

$$v_{o1} = v_{gs7}$$

$$v_o = -g_{m7} \cdot v_{gs7} (r_{o7} \parallel r_{o2})$$

$$\frac{v_o}{v_{o1}} = -3.568 \text{ mA/V} \left(\frac{125.6k\Omega}{2} \right) = -224.1$$

Second
stage

$$\therefore \text{Overall gain} = A_d = (158.5)(-224.1) = -3.55 \times 10^4$$

$$\text{or } A_d = 91 \text{ dB}$$