

Homework 5 – Solutions

Problems (not review questions): 7.25, 7.30 (use T-model), 7.32, 7.59, 7.64, 7.71

7.25 Consider the FET amplifier of Fig. 7.10 for the case $V_t = 0.4 \text{ V}$, $k_n = 5 \text{ mA/V}^2$, $V_{GS} = 0.6 \text{ V}$, $V_{DD} = 1.8 \text{ V}$, and $R_D = 10 \text{ k}\Omega$.

- Find the dc quantities I_D and V_{DS} .
- Calculate the value of g_m at the bias point.
- Calculate the value of the voltage gain.
- If the MOSFET has $\lambda = 0.1 \text{ V}^{-1}$, find r_o at the bias point and calculate the voltage gain.

$$7.25 \text{ (a) } I_D = \frac{1}{2} k_n (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 5 (0.6 - 0.4)^2 = 0.1 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D R_D = 1.8 - 0.1 \times 10 = 0.8 \text{ V}$$

$$\text{(b) } g_m = k_n V_{OV} = 5 \times 0.2 = 1 \text{ mA/V}$$


$$\text{(c) } A_v = -g_m R_D = -1 \times 10 = -10 \text{ V/V}$$

$$\text{(d) } \lambda = 0.1 \text{ V}^{-1}, \quad V_A = \frac{1}{\lambda} = 10 \text{ V}$$

$$r_o = \frac{V_A}{I_D} = \frac{10}{0.1} = 100 \text{ k}\Omega$$

$$A_v = -g_m (R_D \parallel r_o)$$
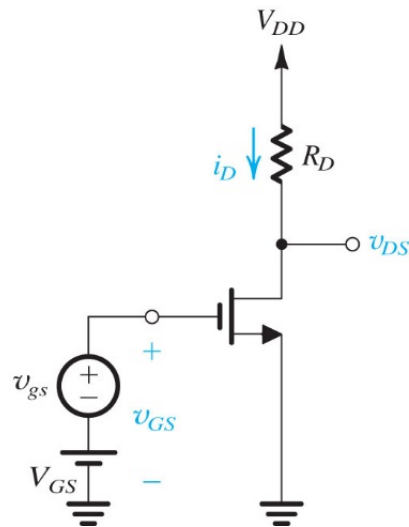
$$= -1(10 \parallel 100) = -9.1 \text{ V/V}$$



7.30 For the NMOS amplifier in Fig. P7.30, replace the transistor with its T equivalent circuit, assuming $\lambda = 0$. Derive expressions for the voltage gains v_s/v_i and v_d/v_i .


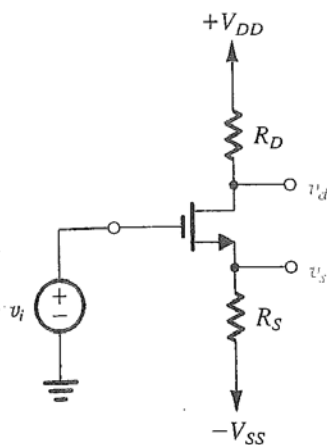


Figure P7.30

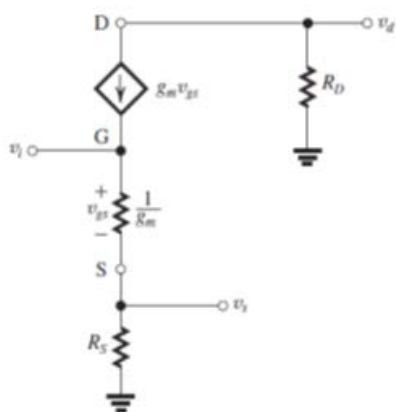

$$v_i = (g_m v_{gs}) \left(\frac{1}{g_m} + R_S \right)$$

$$v_d = -g_m v_{gs} R_D$$

$$v_s = +g_m v_{gs} R_S$$

$$\therefore \frac{v_s}{v_i} = \frac{R_S}{\frac{1}{g_m} + R_S} = \frac{+g_m R_S}{1 + g_m R_S}$$

$$\frac{v_d}{v_i} = \frac{-R_D}{\frac{1}{g_m} + R_S} = \frac{-g_m R_D}{1 + g_m R_S}$$

7.32 For a 0.18- μm CMOS fabrication process: $V_m = 0.5\text{ V}$, $V_p = -0.5\text{ V}$, $\mu_n C_{ox} = 400\text{ }\mu\text{A/V}^2$, $\mu_p C_{ox} = 100\text{ }\mu\text{A/V}^2$, $C_{ox} = 8.6\text{ fF}/\mu\text{m}^2$, V_A (n -channel devices) $= 5L$ (μm), and $|V_A|$ (p -channel devices) $= 6L$ (μm). Find the small-signal model parameters (g_m and r_o) for both an NMOS and a PMOS transistor having $W/L = 10\text{ }\mu\text{m}/0.5\text{ }\mu\text{m}$ and operating at $I_D = 100\text{ }\mu\text{A}$. Also, find the overdrive voltage at which each device must be operating.

7.32 For the NMOS device:

$$\begin{aligned} I_D = 100 &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{OV}^2 \\ &= \frac{1}{2} \times 400 \times \frac{10}{0.5} \times V_{OV}^2 \\ \Rightarrow V_{OV} &= 0.16\text{ V} \\ g_m &= \frac{2I_D}{V_{OV}} = \frac{2 \times 0.1\text{ mA}}{0.16} = 1.25\text{ mA/V} \\ V_A &= 5L = 5 \times 0.5 = 2.5\text{ V} \\ r_o &= \frac{V_A}{I_D} = \frac{2.5}{0.1} = 25\text{ k}\Omega \end{aligned}$$


For the PMOS device:

$$\begin{aligned} I_D = 100 &= \frac{1}{2} \mu_p C_{ox} \frac{W}{L} V_{OV}^2 \\ &= \frac{1}{2} \times 100 \times \frac{10}{0.5} \times V_{OV}^2 \\ \Rightarrow V_{OV} &= 0.316\text{ V} \\ g_m &= \frac{2I_D}{V_{OV}} = \frac{2 \times 0.1}{0.316} = 0.63\text{ mA/V} \\ V_A &= 6L = 6 \times 0.5 = 3\text{ V} \\ r_o &= \frac{V_A}{I_D} = \frac{3}{0.1} = 30\text{ k}\Omega \end{aligned}$$

7.59 An amplifier with an input resistance of $100\text{ k}\Omega$, an open-circuit voltage gain of 100 V/V , and an output resistance of $100\text{ }\Omega$ is connected between a $20\text{-k}\Omega$ signal source and a $2\text{-k}\Omega$ load. Find the overall voltage gain G_v . Also find the current gain, defined as the ratio of the load current to the current drawn from the signal source.

$$\begin{aligned}
 G_v &= \frac{R_{\text{in}}}{R_{\text{in}} + R_{\text{sig}}} A_{vo} \frac{R_L}{R_L + R_o} \\
 &= \frac{100}{100 + 20} \times 100 \times \frac{2}{2 + 0.1} \\
 &= 79.4\text{ V/V} \\
 i_o &= \frac{v_o}{R_L} \\
 i_i &= \frac{v_{\text{sig}}}{R_{\text{sig}} + R_{\text{in}}} \\
 \frac{i_o}{i_i} &= \frac{v_o}{v_{\text{sig}}} \frac{R_{\text{sig}} + R_{\text{in}}}{R_L} \\
 &= G_v \frac{R_{\text{sig}} + R_{\text{in}}}{R_L} \\
 &= 79.4 \times \frac{20 + 100}{2} = 4762\text{ A/A}
 \end{aligned}$$

This figure belongs to Problem 7.59.

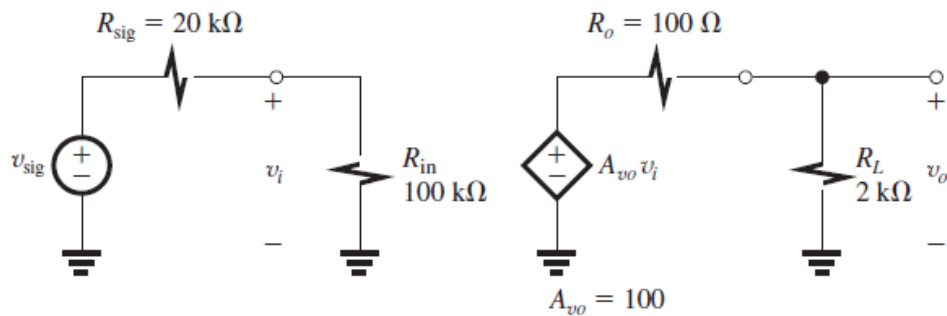

7.64 Calculate the overall voltage gain of a CS amplifier fed with a 1-M Ω source and connected to a 10-k Ω load. The MOSFET has $g_m = 2$ mA/V, and a drain resistance $R_D = 10$ k Ω is utilized.

$$7.64 \quad R_{\text{sig}} = 1 \text{ M}\Omega, R_L = 10 \text{ k}\Omega$$

$$g_m = 2 \text{ mA/V}, R_D = 10 \text{ k}\Omega$$

$$\begin{aligned} G_v &= -g_m(R_D \parallel R_L) \\ &= -2(10 \parallel 10) = -10 \text{ V/V} \end{aligned}$$

7.71 A MOSFET connected in the CS configuration has a transconductance $g_m = 5$ mA/V. When a resistance R_s is connected in the source lead, the effective transconductance is reduced to 2 mA/V. What do you estimate the value of R_s to be?

$$7.71 \quad g_m|_{\text{effective}} = \frac{g_m}{1 + g_m R_s}$$

$$2 = \frac{5}{1 + 5R_s}$$

$$\Rightarrow R_s = 0.3 \text{ k}\Omega = 300 \text{ }\Omega$$