

Homework 8 – Due 11/16/2016

Problems (not review questions): 10.1, 10.3, 10.5, 10.32, 10.34

Solutions for 10.1, 10.3 and 10.5 are in book_solutions.pdf on mycourses

For 10.32, 10.34 use the following equation to find transmission zero frequency $\rightarrow f_z = gm / (2\pi C_{gd})$

Solutions for 10.32: $A_M = -36.4$ V/V, $f_H = 15.2$ kHz, $f_z = 1.6$ GHz

Solutions for 10.34: $A_M = -81$ V/V, $f_H = 554$ kHz, $f_z = 11.2$ GHz

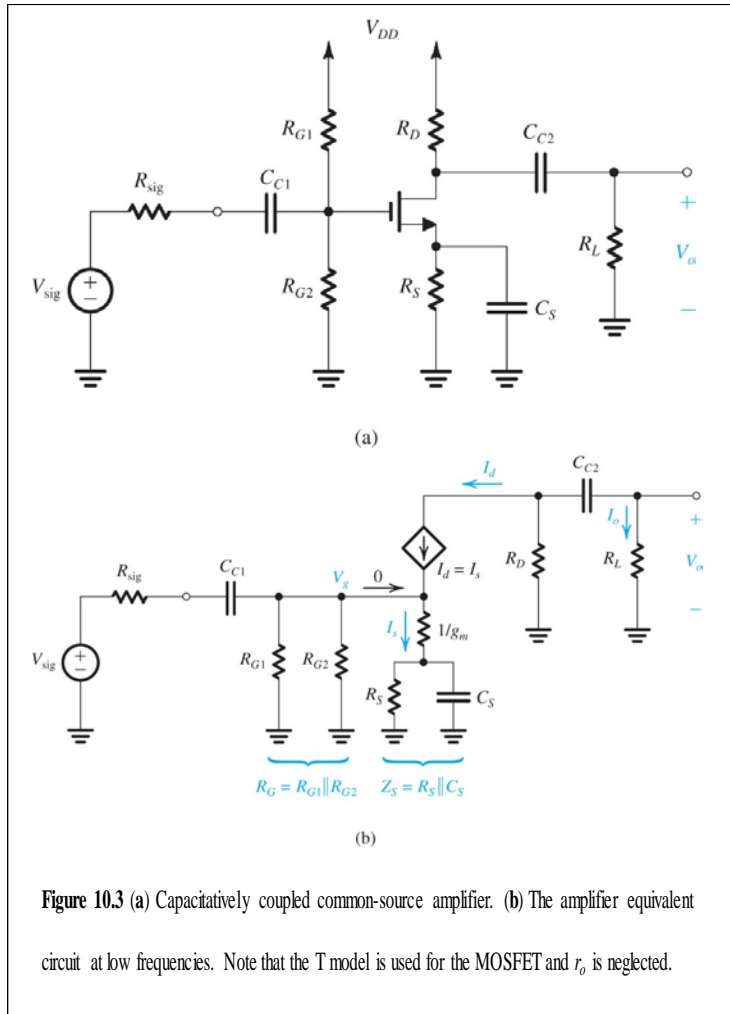


Figure 10.3 (a) Capacitively coupled common-source amplifier. (b) The amplifier equivalent circuit at low frequencies. Note that the T model is used for the MOSFET and r_o is neglected.

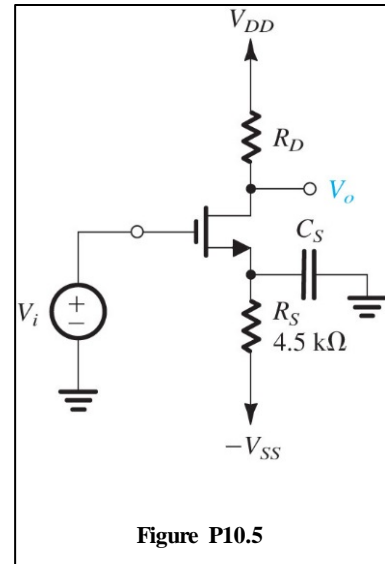


Figure P10.5

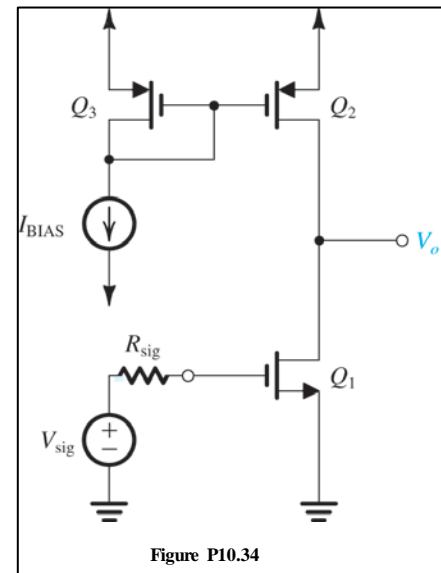


Figure P10.34

EE381 HOMEWORK FORMAT GUIDELINES

Things to remember

- 1) Re-Draw the Circuit on your homework sheet.
- 2) Show all work.
- 3) Final answer should be in decimal form.
- 4) Final answers should be boxed.
- 5) Your name should be on every page.