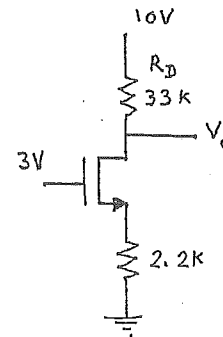


EE 381 ELECTRONICS I (Madhu)
REVIEW PROBLEMS FOR THE FINAL EXAM


Problem 1: $k = 0.2 \text{ mA/V}^2$ and $V_T = 1.5 \text{ V}$.

- (a) Find V_o .
 (b) Find the maximum value that R_D can have before the transistor goes out of saturation. Find V_o for this condition.




Problem 2: $k_1 = 1.25 \text{ mA/V}^2$, $k_2 = 2.5 \text{ mA/V}^2$. $|V_T| = 0.8 \text{ V}$ for both.

- (a) Find V_o .
 (b) Replace the current source by a resistor R_I . What is the value of R_I ?

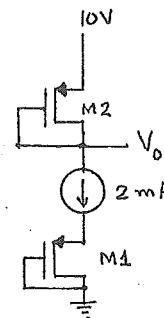


Problem 3: $\mu_n C_{ox} = 0.050 \text{ mA/V}^2$ and $\mu_p C_{ox} = 0.025 \text{ mA/V}^2$.
 $|V_T| = 0.9 \text{ V}$ for both.

- (a) If $(W/L) = 10$ for both transistors, find I_D and V_o .
 (b) Repeat the calculations of Part (a) if (W/L) of the NMOS is changed to 4, keeping (W/L) of the PMOS at 10.

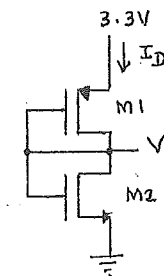

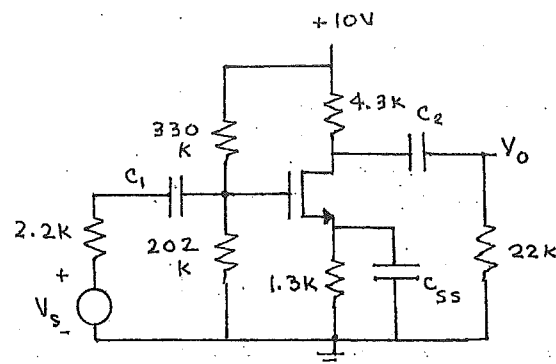
Problem 4: $k = 0.9 \text{ mA/V}^2$ and $V_T = 0.5 \text{ V}$. $C_{gs} = 12 \text{ pF}$. $C_{gd} = 4 \text{ pF}$. $C_{ds} = 6 \text{ pF}$.
 Determine the midband gain and the upper cutoff frequency.



Problem 5: The amplifier of the previous problem is required to have a lower cutoff frequency of 30 Hz. (Note the units!) Select the value of C_{SS} so that it results in a pole at the specified lower cutoff frequency. Select the value of C_I so that the pole due to it cancels the zero caused by C_{SS} and select the value of C_2 so that the pole due to it is at 3 Hz.


Problem 6: $\mu_n C_{ox} = 0.092 \text{ mA/V}^2$. $|V_T| = 0.9 \text{ V}$.
 $(W/L) = 62.5$. $\lambda = 0.025 \text{ V}^{-1}$ for both.

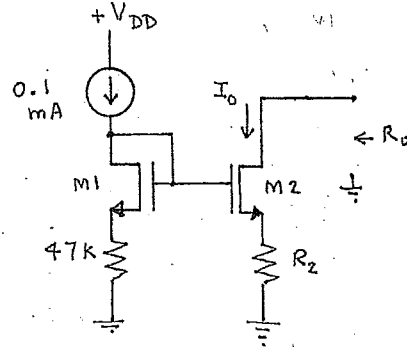- (a) Find the value of R_2 so as to make $I_o = 0.05 \text{ mA}$.
 (b) Find the output resistance R_o .



Problem 7: In the 2-stage CMOS op amp shown below, the sizing ratios of the different transistors are shown in parenthesis. $\mu_n C_{ox} = 0.160 \text{ mA/V}^2$ and $\mu_p C_{ox} = 0.064 \text{ mA/V}^2$.

$|V_T| = 0.7 \text{ V}$ for all transistors. $\lambda = 0.025 \text{ V}^{-1}$ for NMOS and 0.05 V^{-1} for the PMOS devices.

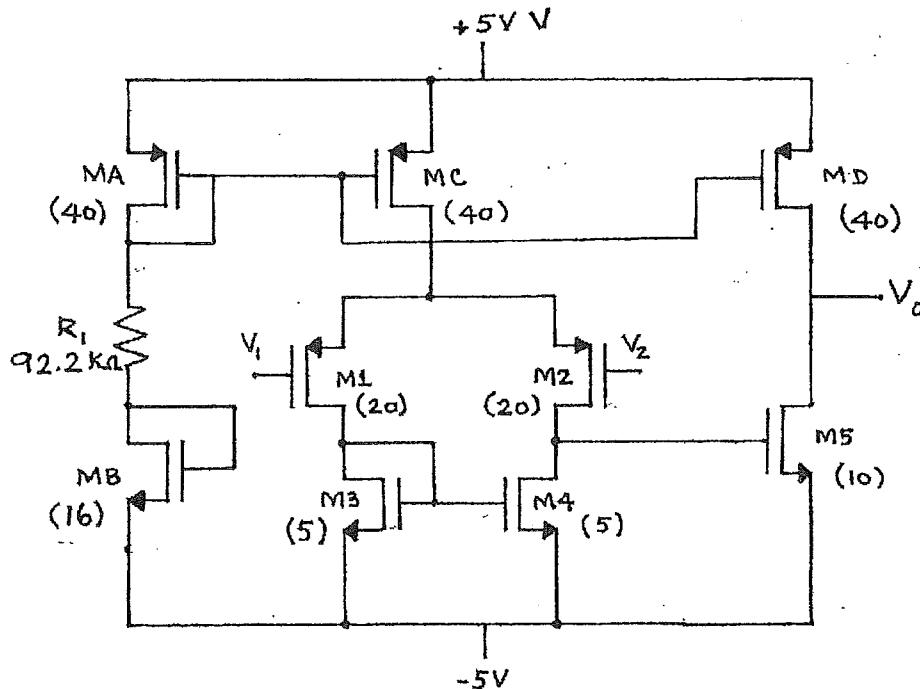


- (a) Determine the Q point values of the drain and gate voltages. Assume that $V_o = 0$ at the Q point.

(b) Determine the diff mode gain.

Problem 8: The asymptotic value of the gain at ω_x is given as 97 dB.

(a) Write the expression of the gain function. Be sure to evaluate the constant K .

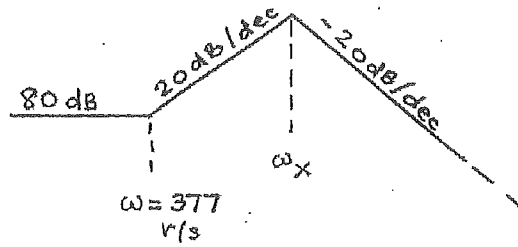(b) Draw the phase plot. Be sure to include all relevant numerical information in the diagram.



Problem 9: A two stage op amp has an equivalent circuit with parameters and element values as follows: $g_{m2} = 1.5$ mS; $R_{o1} = 40$ k Ω ; $C_1 = 13.5$ pF; $g_{m5} = 0.8$ mS; $R_{o2} = 62.5$ k Ω ; $C_2 = 1.2$ pF.


(a) Sketch the Bode magnitude and phase plots.

(b) Determine the value of the Miller compensation capacitor C_C needed to introduce a phase margin of 60°.

PROBLEM 10: Assume ideal diodes. Find the range of values of V_{in} for each of the following two states:

(a) both diodes are ON.


(b) D1 ON and D2 OFF.

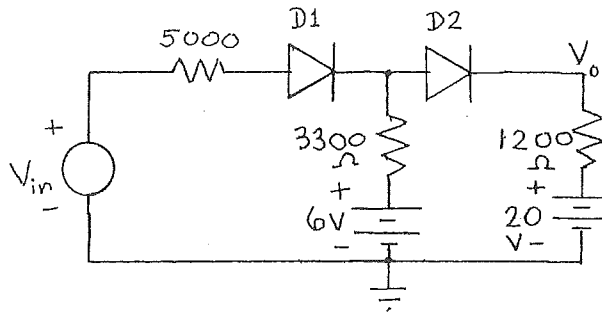

REVIEW PROBLEMS FOR FINAL EXAM

12/5/2018

Madhu

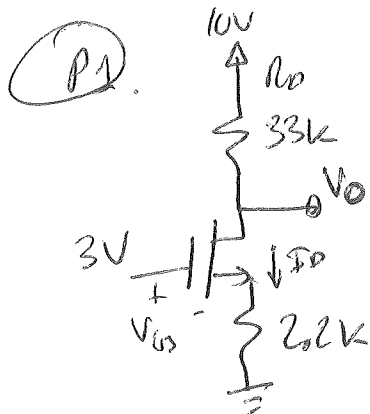

$$k = 0.2 \text{ mA/V}^2$$

$$V_T = 1.5 \text{ V}$$

a) Find V_O .

b) Find max value of R_D for saturation and V_O for this condition.

$$(a) \quad 3 - 2.2 \left(\frac{1}{2} 0.2 (V_{GS} - V_T)^2 \right) = V_{GS}$$

$$3 - 0.22 V_{GS}^2 + 0.66 V_{GS} - 0.495 = V_{GS}$$

$$2.505 - 0.34 V_{GS} - 0.22 V_{GS}^2 = 0$$

$$V_{GS} = -4.23 \text{ V}$$

$$= 2.689 \text{ V}$$

$$V_{GS} = 2.689 \text{ V}$$

$$I_D = 0.1414 \text{ mA}$$

$$\text{And } V_O = 5.335 \text{ V} = 10 - I_D R_D$$

$$(b) \quad V_{GD} = V_T \leq 1.5 \text{ V}$$

$$V_{GD} = 1.5 \text{ V}$$

$$V_D = 1.5 \text{ V (min)}$$

$$R_D = 60.11 \text{ k}\Omega$$

$$V_{DS} = V_{GS} - V_T = 3 - 1.5 = 1.5 \text{ V}$$

$$V_{DS} = \underbrace{I_D R_D}_{V_D} - \underbrace{I_D R_S}_{V_S}$$

$$V_{DS} = 1.5 = (0.1414 \cdot R_D) - 0.31108$$

$$R_D = \frac{1.189 + 0.311}{0.1414} = 3.38 \text{ k}\Omega$$

$$V_{DS} = 1.189 = \underbrace{(10 - I_D R_D)}_{V_D} - \underbrace{I_D R_S}_{V_S}$$


$$1.189 = 10 - 0.1414 \cdot R_D - 0.311$$

$$1.189 - 10 + 0.311 = -0.1414 R_D$$

$$R_D = \frac{8.5}{0.1414} = 60.11 \text{ k}\Omega$$

$$V_O = 10 - 8.5 = 1.5 \text{ V}$$

#2

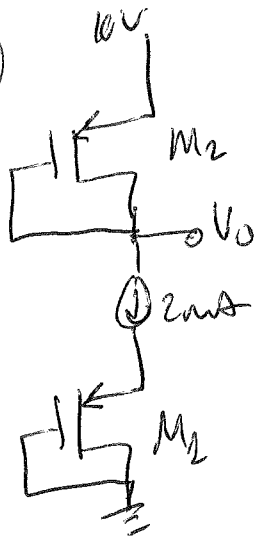

$$k_1 = 1.25 \text{ mA/V}^2$$

$$|V_T| = 0.8 \text{ V}$$

$$k_2 = 2.5 \text{ mA/V}^2$$

(a) V_O .

$$M_2: I_D = 2 \text{ mA}$$

$$2 \text{ mA} = \frac{1}{2} (1.25 \text{ mA/V}^2) (V_{GS2} - 0.8)^2$$

$$V_{GS2} = 2.065 \text{ V}$$

$$V_{OV} = \sqrt{\frac{4}{2.5}} = 1.26 \text{ V}$$

$$V_{GS} = V_{OV} + V_T$$

$$V_O = 7.935 \text{ V} = (10 - 2.065 \text{ V})$$

(b) Replace current source by R_1 . What is R_1 ?

$$V_O = 7.935 \text{ V}$$

$$V_{S1} = 2.589 \text{ V}$$

$$2 \text{ mA} = \frac{1}{2} (1.25 \text{ mA/V}^2) (V_{OV}^2)$$


$$V_{GS1} = V_{S1} = 2.589 \text{ V}$$

$$V_{S1} = 2.589 \text{ V}$$

$$R = \frac{7.935 - 2.589}{2 \text{ mA}} = 2.673 \text{ k}\Omega$$

P3

② 12/5/2016
Madhu

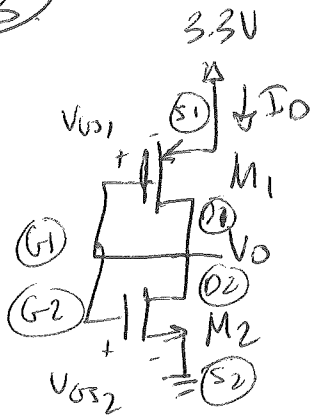

$$\mu_n C_{ox} = 0.05 \text{ mA/V}^2$$

$$\mu_p C_{ox} = 0.025 \text{ mA/V}^2$$

$$|V_{th}| = 0.9 \text{ V}$$

(a) $\frac{W}{L} = 10$ for both. Find I_D + V_O

$$k_n = 10 \cdot 0.05 \text{ mA/V}^2 = 0.5 \text{ mA/V}^2$$

$$k_p = 10 \cdot 0.025 \text{ mA/V}^2 = 0.25 \text{ mA/V}^2$$

$$I_{Dn} = I_{Dp}$$

$$\frac{1}{2} 0.5 \text{ mA/V}^2 (V_{GS1} - V_{th})^2 = \frac{1}{2} 0.25 \text{ mA/V}^2 (V_{GS1} - V_{th})^2$$

$$\frac{V_{GS1} - 0.9}{V_{GS2} - 0.9} = \sqrt{\frac{0.25}{0.125}} = 1.414$$

$$V_{GS1} - 0.9 = 1.414 V_{GS2} - 1.273$$

2 eq, 2 unknowns

$$\begin{cases} V_{GS1} = 1.414 V_{GS2} - 0.3728 \\ V_{GS1} + V_{GS2} = 3.3 \end{cases}$$

$$V_{GS1} = 1.778 \text{ V}$$

$$V_{GS2} = 1.521 \text{ V}$$

(b) $\left(\frac{W}{L}\right)_n = 4$ $\left(\frac{W}{L}\right)_p = 10$

$$k_n = 0.2 \text{ mA/V}^2$$

$$k_p = 0.25 \text{ mA/V}^2$$

$$0.1 (V_{GS2} - 0.9)^2 = 0.125 (V_{GS1} - 0.9)^2$$

$$\frac{V_{GS2} - 0.9}{V_{GS1} - 0.9} = \sqrt{\frac{0.125}{0.1}} = 1.118$$

$$V_{GS2} - 0.9 = 1.118 V_{GS1} - 1.006$$


$$\begin{cases} 1.118 V_{GS1} - V_{GS2} = 0.1062 \\ V_{GS1} + V_{GS2} = 3.3 \end{cases} \quad \begin{matrix} \text{2 eq} \\ \text{2 unknowns} \end{matrix}$$

$$V_{GS1} = 1.608 \text{ V}$$

$$V_{GS2} = 1.692 \text{ V}$$



PU.

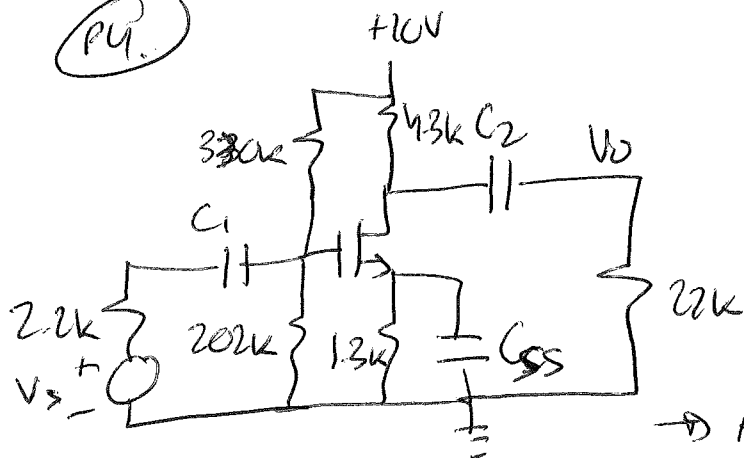

$$k = 0.9 \text{ mA/V}^2$$

$$V_T = 0.5$$

$$C_{SS} = 12 \text{ pF}$$


$$C_{sd} = 4 \text{ pF}$$

$$C_{ds} = 16 \text{ pF}$$

Find midband gain and upper cutoff frequency.

DC Analysis

Caps \rightarrow open

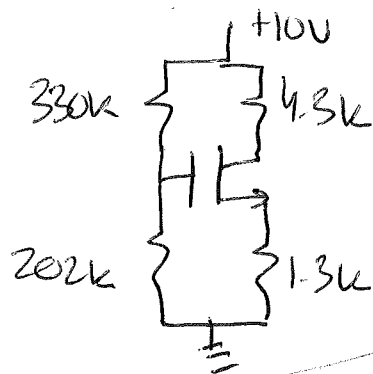

$$V_G = 10V \cdot \frac{202k}{202k + 330k} = 3.797V$$

$$V_{GS} = 3.797 - \left(\frac{1}{2} \cdot 0.9 (V_{GS} - 0.5)^2 \right) (1.3k)$$

$$V_{GS} = 3.797 - 0.585 (V_{GS} - 0.5)^2$$


$$3.797 - 0.585 V_{GS}^2 + 0.585 V_{GS} - 0.14625 = V_{GS}$$

$$V_{GS} = 2.168V$$

$$I_{DS} = 1.501 \text{ mA}$$

$$I_{DS} = k (V_{GS} - V_T)$$

Small signal midband:

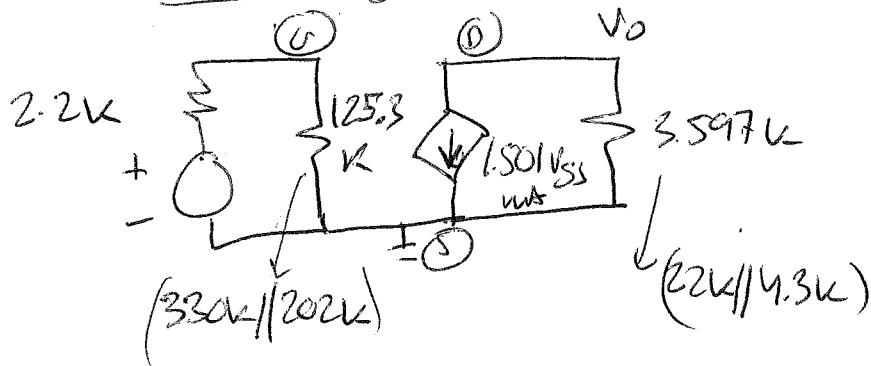

$$\frac{V_O}{V_{GS}} = -5.399$$


$$\frac{V_{GS}}{V_{sig}} = \frac{125.3}{125.3 + 2.2} = 0.9827$$

$$A_{mid} = -5.306$$

③ 12/5/2016
Madhu

→ Upper cut-off frequency

W_{hi} Input side:

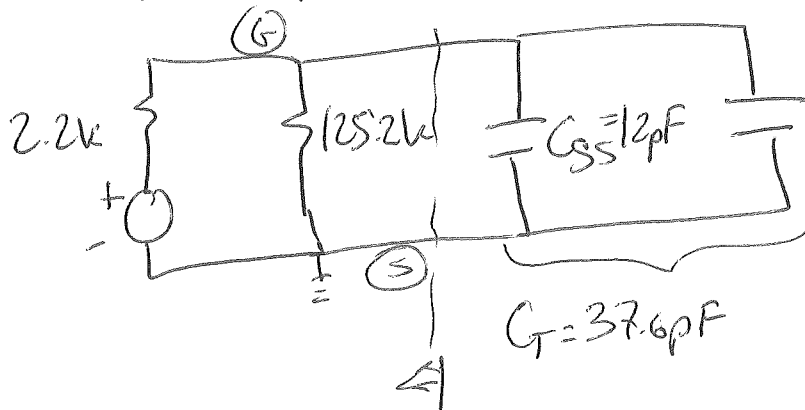

$$C_M = C_{gd}(1 + g_m R_{eq})$$


$$= 4pF(1 + 1.501ms \cdot 3.597k)$$

$$C_M = 4(1 + 5.399) = 25.6pF$$

$$R_{TH} = 125.2k // 2.2k = 2.162k$$

$$\therefore W_{hi}(w) = \frac{1}{(2.162k)(37.6pF)} = 1.230 \times 10^7 \text{ 1/s}$$

W_{hi} output side:

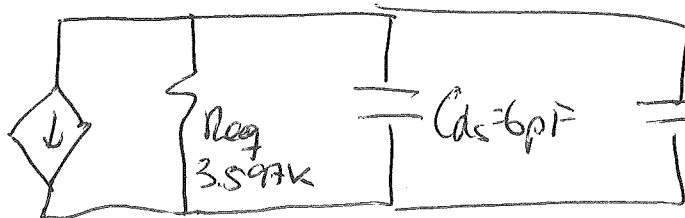

$$C'_M = C_{ds}(1 + \frac{1}{g_m R_{eq}})$$

$$C'_M = 4pF(1 + \frac{1}{5.399}) = 4.741pF$$

$$W_{hi}(out) = \frac{1}{(3.597 \times 10^3)(4.741 \times 10^{-12})} = 2.588 \times 10^7 \text{ 1/s}$$

No dominant pole


$$\left| \frac{(1.23 \times 10^7)(2.588 \times 10^7)}{(1.23 \times 10^7)(10 + 2.588 \times 10^7)} \right| = 0.707$$

→ to find 3dB pole.

$$\therefore W_{hi} = 1.044 \times 10^7 \text{ 1/s}$$

(P5) $\rightarrow f_{L0} = 30 \text{ Hz} \rightarrow \omega_{L0} = 188.5 \text{ rad/s}$

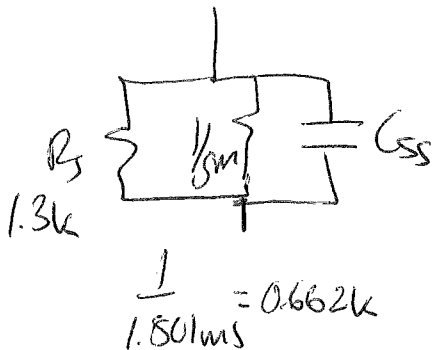Bypass capacitor $C_{SS} \rightarrow \omega_p = 188.5 \text{ rad/s}$




$$\omega_p = 188.5 \text{ rad/s} = \frac{1}{(1.3 \text{ k} \parallel 0.662 \text{ k}) \cdot C_{SS}}$$

$$C_{SS} = \frac{1}{(188.5 \text{ rad/s})(0.4405 \times 10^3)} = 12.04 \mu\text{F}$$

$$\omega_z \text{ due to } C_{SS} = \frac{1}{R_S C_{SS}} = \frac{1}{(1.3 \times 10^3)(12.04 \times 10^{-6})} = 63.89 \text{ rad/s}$$

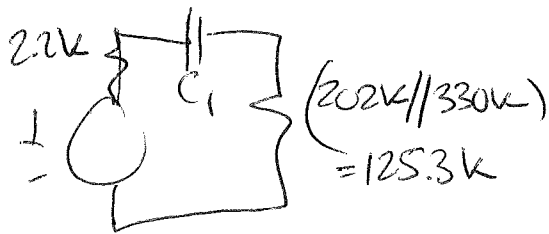\rightarrow Want C_1 to cancel that zero (ω_z of C_{SS})




$$\omega_{pC1} = \frac{1}{C_1 \cdot (127.5 \times 10^3 \Omega)} = 63.89 \text{ rad/s}$$

$$\therefore C_1 = \frac{1}{(63.89 \text{ rad/s})(127.5 \times 10^3 \Omega)}$$

$$C_1 = 122.8 \mu\text{F}$$

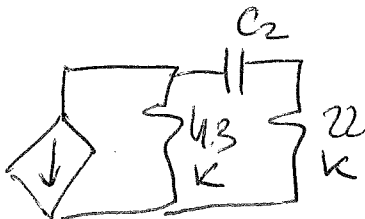
\rightarrow Make C_2 's pole at 0.1 rad/sec. $= 3 \text{ Hz}$ $\omega_{pC2} = 6 \text{ rad/s}$



$$\omega_{pC2} = \frac{1}{C_2 \cdot (26.3 \text{ k})} = 6 \text{ rad/s}$$

$$C_2 = \frac{1}{(26.3 \text{ k})(6 \text{ rad/s})} = 2.07 \mu\text{F}$$

12/7/2016 (2)

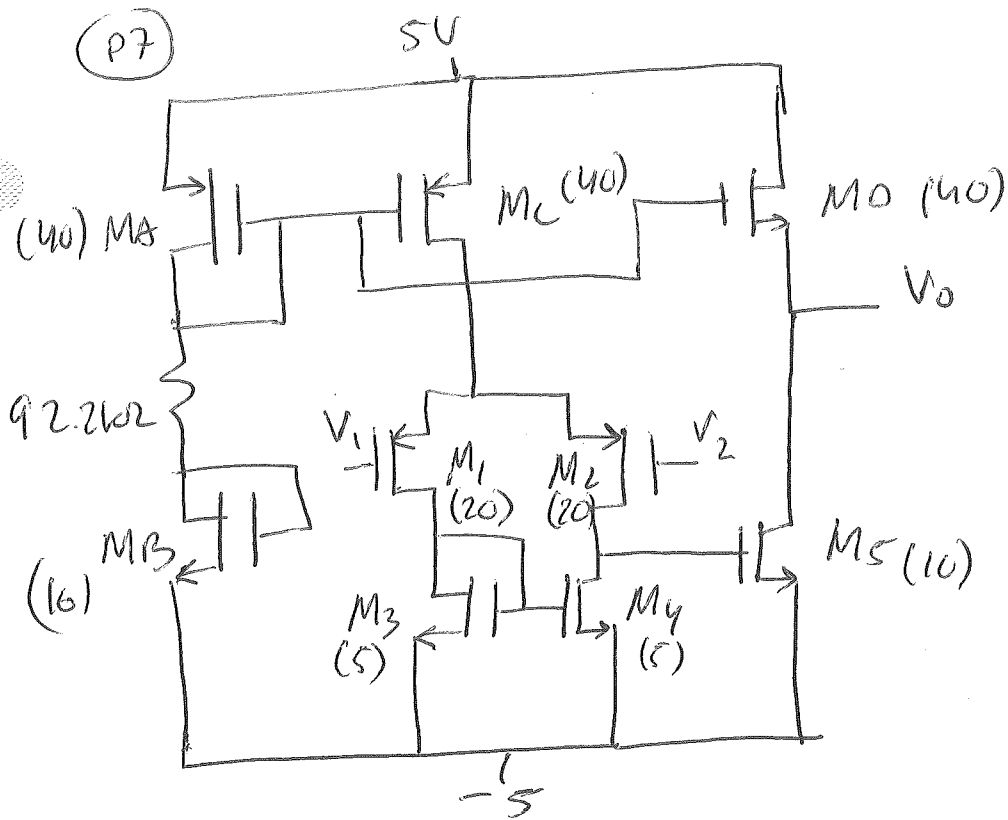

$$\mu n \mu_{ox} = 0.16 \text{ mA/V}^2$$

$$\mu p \mu_{ox} = 0.064 \text{ mA/V}^2$$

$$K_A = 0.064 \times 40 = 2.56 \text{ mA/V}^2$$

$$K_B = 0.16 \times 16 = 2.56 \text{ mA/V}^2$$

$$\therefore V_{SGA} = V_{SGB}$$

$$5 - V_{SGA} - 92.2 \text{ k}\Omega \left(\frac{1}{2} \right) (2.56) (V_{SGA} - 0.7)^2 - V_{SGA} = -5$$

$$5 - V_{SGA} - 118 V_{SGA}^2 + 165.2 V_{SGA} - 57.82 - V_{SGA} = -5$$

$$V_{SGA} = 0.9616 \text{ V} \left[-118 V_{SGA}^2 + 165.2 V_{SGA} - 47.82 = 0 \right]$$

$$I_{REF} = 0.0876 \text{ mA}$$

$$-118 V_{SGA}^2 + 165.2 V_{SGA} - 47.82 = 0$$

$$M_A: V_G = V_D = 4.038 \text{ V}$$

$$M_B: V_G = V_D = -4.038 \text{ V}$$

$$\rightarrow M_1: I_D = 0.0438 \text{ mA}$$

$$\left. \begin{array}{l} \text{PMOS} \\ K_1 = 0.064 \times 20 = 1.28 \text{ mA/V}^2 \end{array} \right\}$$

$$0.0438 \text{ mA} = \frac{1}{2} \cdot 1.28 \text{ mA/V}^2 (V_{SG1} - V_t)^2$$

$$V_{OV} = \sqrt{\frac{2 \cdot 0.0438}{1.28}} = 0.2616$$

$$V_{SG1} = 0.9616 \text{ V} = 0.2616 + 0.7$$

M3: $k_3 = 0.8 \text{ mA/V}^2$

NMOS $I_{D3} = 0.0438 \text{ mA}$

$$0.0438 \text{ mA} = \frac{1}{2} \cdot 0.8 \text{ mA/V}^2 (V_{OV})^2$$

$$V_{OV} = 0.331 \text{ V}$$

$$V_{GS3} = 1.031 \text{ V}$$

$$M3: V_{G3} = V_{D3} = -3.969 \text{ V}$$

→ M2 same as M1

→ M4 same as M3 → what is V_{O4} ?

Mc: $k_c = 2.5 \text{ mA/V}^2$

$$V_G \text{ of } M_c = V_G \text{ of } M_A = 4.038 \text{ V}$$

M_D: same as M_c.

M₅: $I_{D5} = 0.0876 \text{ mA}$

$$k_5 = 1.6 \text{ mA/V}^2 = 10 \times 0.16 \text{ mA/V}^2$$

$$0.0876 \text{ mA} = \frac{1}{2} \cdot 1.6 \text{ mA/V}^2 (V_{OV})^2$$


$$V_{OV} = \cancel{0.462 \text{ V}} + \cancel{0.464 \text{ V}} = 0.331 \text{ V}$$

$$V_{GS5} = \cancel{7.16 \text{ V}} = 1.031 \text{ V}$$

$$V_{DS} = \cancel{-3.84 \text{ V}} = V_{D5} = -3.969 \text{ V}$$

12/7/2016

Madhu

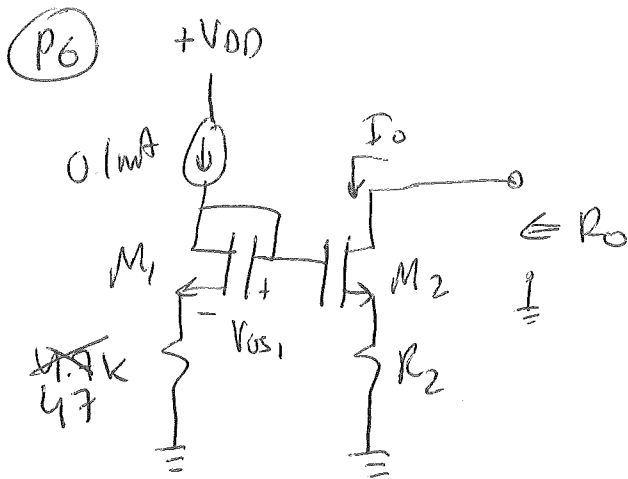

$$\mu_n C_{ox} = 0.092 \text{ mA/V}^2$$

$$|V_T| = 0.9 \text{ V}$$

$$\frac{W}{L} = 62.5, \lambda = 0.025 \text{ V}^{-1} \text{ (for both)}$$

- (a) Find R_2 to make $I_O = 0.05 \text{ mA}$
 (b) Find output resistance R_o .

$$(a) I_{D1} = 1 \text{ mA} = \frac{1}{2} (0.092 \text{ mA/V}^2) (62.5) \cdot \underbrace{(V_{GS1} - V_T)^2}_{V_{OV}^2}$$

$$V_{OV1} = 0.186$$

$$V_{GS1} = 1.086 \text{ V}$$

$$V_{G1} = (47 \text{ k}\Omega)(0.1 \text{ mA}) + 1.086 \text{ V} = 5.786 \text{ V}$$

$$\text{Also } V_{G2} = 5.786 \text{ V}$$

$$\text{For } I_{D2} = 0.05 \text{ mA} = \frac{1}{2} (0.092 \text{ mA/V}^2) (62.5) (V_{OV})^2$$

$$V_{OV2} = \cancel{0.186} 0.132$$

$$V_{GS2} = 1.032 \text{ V}$$

$$\therefore V_{GS2} = V_{G2} - V_{S2}$$

$$1.032 \text{ V} = 5.786 - V_{S2}$$

$$V_{S2} = 4.754 = R_2 \cdot (0.05)$$

$$R_2 = 95.08 \text{ k}\Omega$$

$$\text{OR: } 1.032 = 5.786 - R_2 \cdot (0.05)$$

$$R_2 = 95.08 \text{ k}\Omega$$

b) Find output resistance R_o :

$$\frac{1.086 - 0.9}{r = 0.186}$$

Draw small signal circuit, need $g_{m1} = 0.092 \times 62.5 (V_{ov1})$


$$g_{m1} = 1.07 \text{ mS}$$

$$\text{and } g_{m2} = 0.092 \times 62.5 (V_{ov2})^{0.132}$$

$$g_{m2} = 0.759 \text{ mS}$$

$$\text{and } r_{o2} = \frac{1}{\lambda \cdot I_{D2}} = \frac{1}{0.025 \times 0.05}$$

$$r_{o2} = 800 \text{ k}\Omega$$

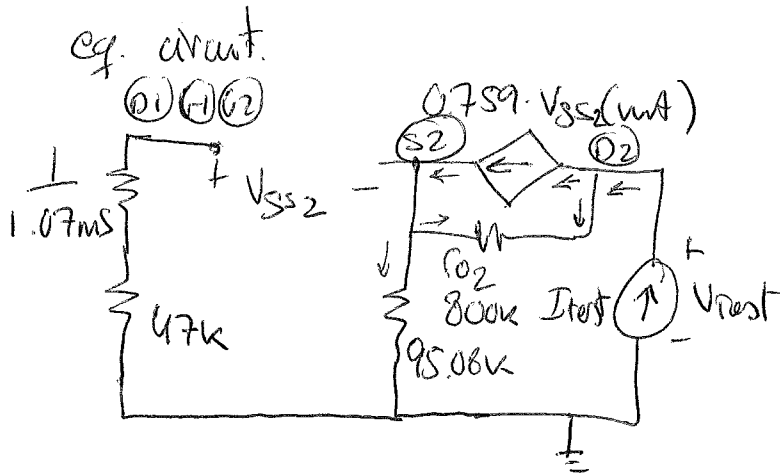

$$V_{GS2} = -V_{S2} \text{ since } V_{S2} = 0 \text{V (no current flowing)}$$

$$\text{Node } S2: \frac{V_{S2}}{95.08 \text{ k}} + \frac{V_{S2} - V_{test}}{800 \text{ k}} = 0.759 (-V_{S2})$$

$$0.77076 V_{S2} - 1.25 \times 10^{-3} V_{test} = 0 \rightarrow (1)$$

$$\text{Node } D2: \frac{V_{test} - V_{S2}}{800} = I_{test} - 0.759 (-V_{S2})$$

$$-0.76025 V_{S2} + 1.25 \times 10^{-3} V_{test} = I_T$$

$$\text{set } I_T = 1 \text{ mA}$$

$$-0.76025 V_{S2} + 1.25 \times 10^{-3} V_{test} = 1 \text{ mA} \rightarrow (2)$$

$$V_{S2} = 95.15 \text{ V}$$

$$V_{test} = 5.867 \times 10^4$$

$$\therefore R_o = \frac{5.867 \times 10^4}{1 \times 10^{-3}} = 58.67 \text{ M}\Omega$$

12/9/2016

Diff. mode gain

→ Need g_{m2}, r_{o2}, r_{o4}
 g_{m5}, r_{o5}, r_{oD}

$$\rightarrow g_{m2} = 20 \times 0.064 \text{ mA/V}^2 (0.261)^{0.3341 \text{ mS}} = \cancel{0.072 \text{ mS}}$$


$$r_{o2} = \frac{1}{0.05 \times 0.0438} = 456.6 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{0.025 \times 0.0438} = 913.2 \text{ k}\Omega$$


$$\rightarrow g_{m5} = 10 \times 0.16 \text{ mA/V}^2 (0.331)^{0.331} = 0.528 \text{ mS}$$

$$r_{o5} = \frac{1}{0.025 \times 0.0876} = 456.6 \text{ k}\Omega$$
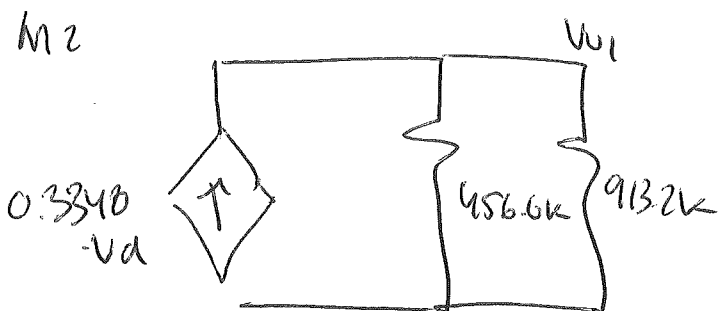
$$r_{oD} = \frac{1}{0.05 \times 0.0876} = 228.3 \text{ k}\Omega$$



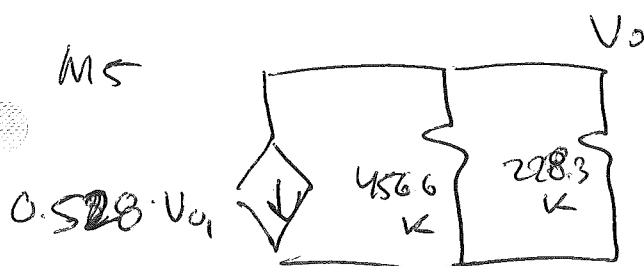
$$\frac{V_{d1}}{V_d} = 101.9 = (0.3348 \text{ mS}) (304.4 \text{ k}\Omega)$$



$$\frac{V_o}{V_{d1}} = -80.36 = -(0.528 \text{ mS}) (152.2 \text{ k}\Omega)$$

$$A_d = -8189 \text{ V/V}$$

P8

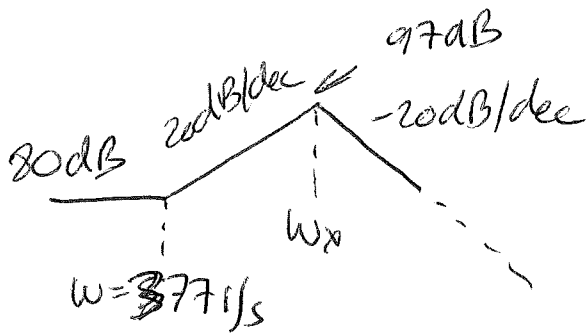

a) Write expression for gain function.

$$\omega_x? \rightarrow 80 + 20 \text{ dB/dec} \log\left(\frac{\omega_x}{377}\right) = 97$$

$$\omega_x = 2669 \text{ 1/s}$$

$$\therefore H(s) = K \frac{(s + 377)}{(s + 2669)^2}$$

$$\rightarrow \text{Find } K \text{ if } H(0) = 10^4 \leftarrow \begin{matrix} 20 \cdot \log H(\omega) = 80 \\ 80/20 \end{matrix} \quad H(0) = 10$$

$$10^4 = K \frac{377}{(2669)^2}$$

$$K = \frac{10^4 \cdot (2669)^2}{377} = 1.889 \times 10^8$$

$$\rightarrow H(s) = 1.889 \times 10^8 \frac{(s + 377)}{(s + 2669)^2}$$

7 cart.s

Control

② 12/9/2006

→ Phase plot.

$\omega = 377$ (zero)

$(0, 377)$ level 0°

$(37.7, 3770)$ $+45^\circ/\text{dec}$ slope

$(3770, \infty)$ level $+90^\circ$ level

$\omega = 2669$ (pole)

$(0, 266.9)$ level 0° level

$(266.9, 26690)$ ~~$-45^\circ/\text{dec}$~~ $-90^\circ/\text{dec}$ (double pole) slope

$(26690, \infty)$ level -180° level

Combined.

$(0, 377)$ level 0°

$(37.7, 266.9)$ $+45^\circ/\text{dec}$ slope

$(266.9, 3770)$ $-45^\circ/\text{dec}$ slope

$(3770, 26690)$ $-90^\circ/\text{dec}$ slope

$(26690, \infty)$ level -90°

