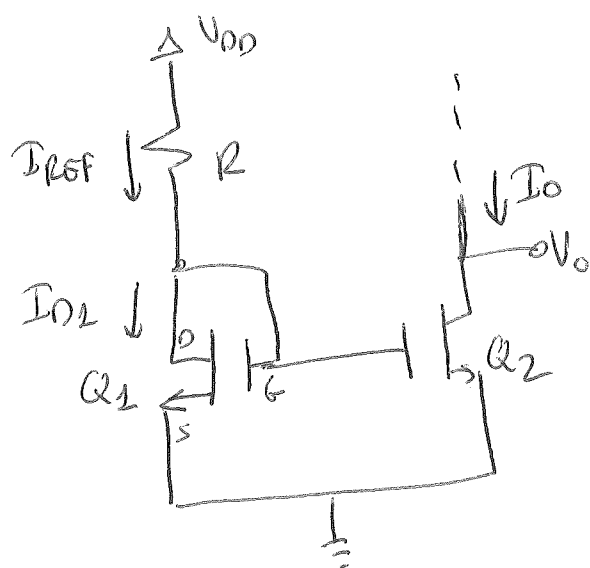


## 8.2.1 - Current Sources, current Mirrors,

9/29/2016

### Basic MOSFET current source.



$Q_2 \rightarrow$  "Heart" of circuit.

Diode connected  $\rightarrow$  always sat.

$$I_{D2} = \frac{1}{2} k_n' \left( \frac{W}{L} \right)_2 (V_{GS} - V_{th})^2 \quad (1)$$

(assume  $\lambda_0 \rightarrow 0$ )

Drain current supplied thru  $V_{DD}$  and resistor  $R$  (external to circuit)

Gate current  $\rightarrow 0$

$$\therefore I_{D2} = I_{REF} = \frac{V_{DD} - V_{GS}}{R} \quad (2)$$

$\rightarrow$  Equations (1) + (2) used to determine ~~REF~~  $R$  for a set  $I_{REF}$ .

$\rightarrow Q_2 \rightarrow$  has same  $V_{GS}$  as  $Q_1$  (also in saturation)

$$\therefore I_O = I_{D2} = \frac{1}{2} k_n' \left( \frac{W}{L} \right)_2 (V_{GS} - V_{th})^2 \quad (3)$$

From (1) and (3)

$$\frac{I_O}{I_{REF}} = \frac{\frac{1}{2} k_n' \left( \frac{W}{L} \right)_2 (V_{GS} - V_{th})^2}{\frac{1}{2} k_n' \left( \frac{W}{L} \right)_1 (V_{GS} - V_{th})^2} = \frac{\left( \frac{W}{L} \right)_2}{\left( \frac{W}{L} \right)_1}$$

$\rightarrow$  If  $\left( \frac{W}{L} \right)_1 = \left( \frac{W}{L} \right)_2$  then  $I_{REF} = I_O \rightarrow$  "current mirror"

$\rightarrow$  Scaling  $\left( \frac{W}{L} \right)_1$  to  $\left( \frac{W}{L} \right)_2$  scales  $I_O$  to  $I_{REF} \rightarrow$  current gain or current transfer ratio.

## Effect of $V_o$ and $I_o$


→  $Q_2$  must remain in saturation.

$$\therefore V_o = V_{DS_2} \geq V_{GS_2} - V_{tn} \quad \text{or} \quad V_o \geq V_{ov}$$

$V_{ov}$  generally a few  
tenths of  $V_{DD}$ .

→ Also channel-length modulation  $\lambda$  can have significant effect on the operation of the current source.

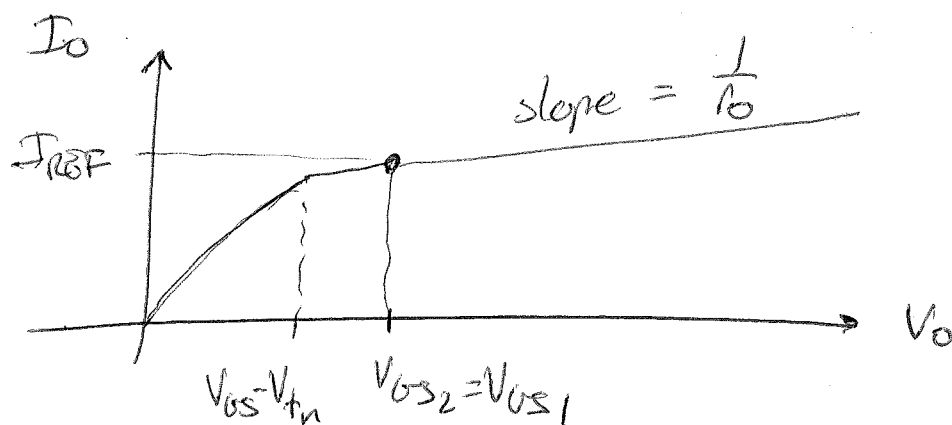As  $V_o$  increases beyond initial value of  $V_{DS_1}$ ,  $I_o$  increases according to  $r_{o2}$  of  $Q_2$ .



$\therefore$  Output resistance of current source

$$R_o = \frac{\Delta V_o}{\Delta I_o} = r_{o2} = \frac{V_{A2}}{I_o} = \frac{1}{\lambda_2 I_o}$$


→ use long  
channel trans.  
to get high  $R$

---

Also  $I_o = \frac{(W/L)_2}{(W/L)_1} I_{REF} \left( 1 + \frac{V_o - V_{DS}}{V_{A2}} \right)$  take into account  
channel length mod.

# Ex. 8.1 - Current mirror example:

9/29/2016 (2)

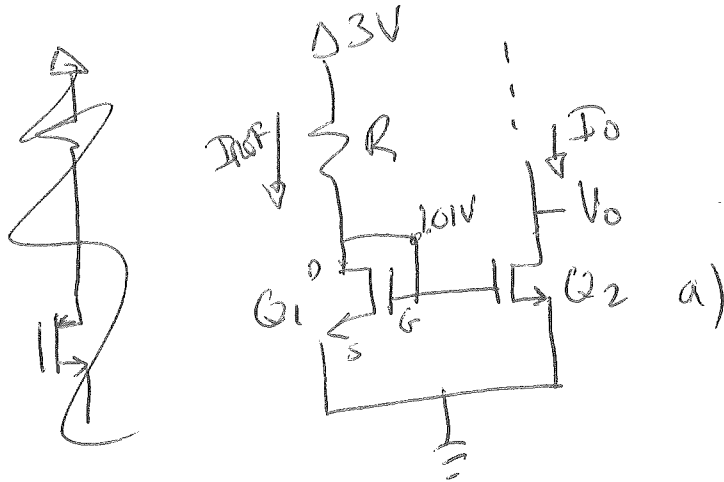

$$V_{DD} = 3V$$

$$I_{REF} = 100 \mu A$$

$$\frac{I_{REF}}{I_{REF}} = \frac{15 \mu A}{16 \mu A}$$

Design circuit for  $I_O = 100 \mu A$

Find R for  $Q_1 = Q_2$  and

$$L = 1 \mu m, W = 10 \mu m, V_T = 0.7V$$

$$K_n = 200 \mu A/V^2$$

a)  $Q_1 = Q_2$  in saturation  $V_O = V_G$

$$I_{O1} = I_{REF} = \frac{1}{2} K_n \left( \frac{W}{L} \right)_1 \underbrace{(V_{GS} - V_T)^2}_{(V_{OV})^2}$$

$$100 \times 10^{-6} A = \frac{1}{2} 200 \times 10^{-6} A/V^2 \left( \frac{10}{1} \right) V_{OV}^2$$

$$V_{OV}^2 = 0.316 V \rightarrow V_{OV} = \frac{2 \cdot 100 \times 10^{-6}}{200 \times 10^{-6}} \cdot \frac{1}{10}$$

$$\sqrt{V_{OV}^2} = \sqrt{0.2}$$

$$V_{OV} = V_{GS} - V_T = 0.316 V$$

$$V_{GS} = 0.316 V + 0.7 V = 1.01 V$$

$$R = \frac{3V - 1.01V}{100 \times 10^{-6} A} = 19.83 k\Omega$$

b) Find lowest possible value of  $V_O$ ?

$$V_{Omin} = V_{GS} - V_T = V_{OV} = 0.316 V$$

c) Assuming  $V_A' = 20\text{V}/\mu\text{m}$  (length dependent early voltage)  
 find output resistance of the current source.

$$R_o = r_{o2} = \frac{V_{A2}}{I_{O2}}$$

$$V_{A2} = V_A' \times (\text{length})$$

$$V_{A2} = 20\text{V}/\mu\text{m} \times 1\mu\text{m} = 20\text{V}$$

$$\boxed{R_o = \frac{20\text{V}}{100\mu\text{A}} = 200\text{k}\Omega}$$

d) Find change in output current resulting from a  
 +1-V change in  $V_o$ .

$$\Delta V_o = \Delta I_{O2} \cdot R_o \rightarrow \Delta V_o = 1\text{V}, R_o = 200\text{k}\Omega.$$

$$\boxed{\Delta I_{O2} = \frac{1\text{V}}{200\text{k}\Omega} = 5\mu\text{A}}$$

HW #4:

5.46, 5.50, 5.61

↳ sol: (a)  $R = 21\text{k}\Omega$  (b)  $W_2 = 14.4\mu\text{m}$   $R_2 = 3.1\text{k}\Omega$

$$V_{DS} = V_{DS} - V_T = 0.25\text{V}$$

## Chapter 7 - MOSFET as transistor amplifiers

10/3/2016  
Electronics 1

- Study models used to represent MOSFETs in the analysis and design of small-signal linear amplifiers.
- Three basic configurations of <sup>single-</sup>MOSFET amplifiers.

### 7.1 - Basic principles

MOSFETs operated in saturation (also called active region).


$$\therefore i_D = \frac{1}{2} k_n (V_{GS} - V_{th})^2 \quad \left\{ \begin{array}{l} \text{implies} \\ V_{DS} \leq V_{th} \\ V_{DS} \geq V_{GS} - V_{th} \end{array} \right.$$

→ ~~Voltage~~ amplifier:

→ Equation above describes a transconductance amplifier: Amplifier with a voltage input and current output.

→ we want voltage amplifier.

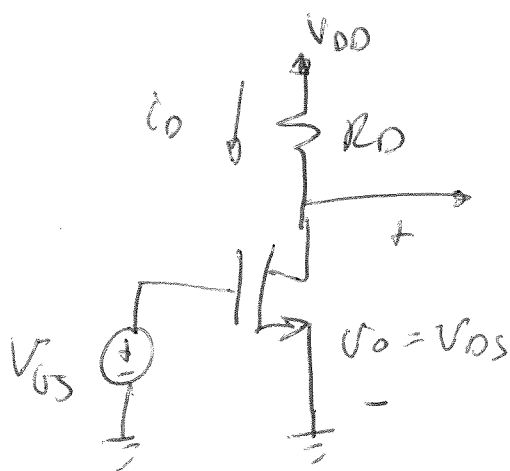→ pass the output current through a resistor and take voltage across it is the output.



→ Voltage amplifier.

→  $R_D \rightarrow$  load resistance.


→  $V_O = V_{DS}$  in order to have a common ground.

→  $R_D, V_{DD}$  bias NMOS in saturation.

$$V_O = V_{DS} = V_{DD} - i_D R_D$$

→ which is inverted value of  $i_D R_D$  shifted by a constant value  $V_{DD}$ .

→ Keep MOSFET in sat./active region.

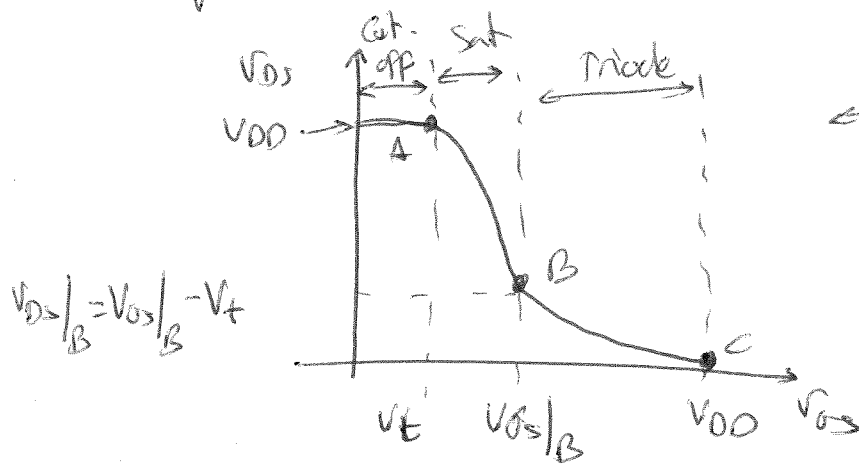

→ Voltage transfer characteristics

→ VTC

For  $V_{GS} < V_T \rightarrow$  NMOS cut-off.  $i_D = 0A$  and  $V_{DS} = V_{DD}$

→ As  $V_{GS}$  increases, NMOS turns on and  $i_D \neq 0$

and  $V_{DS}$  decreases.

→ When  $V_{DS} = V_{GS} - V_T$ , NMOS in triode region.

→ For segment AB:

$$V_{DS} = V_{DD} - i_D R_D$$

$$V_{DS} = V_{DD} - \frac{1}{2} k_n R_D (V_{GS} - V_T)^2$$

$$V_{GS} = V_{GS/B}$$

$$V_{DS} = V_{GS/B} - V_T$$


and

$$V_{GS/B} = V_T + \frac{\sqrt{2 k_n R_D V_{DD} + 1} - 1}{k_n R_D}$$

6/3/2016  
②


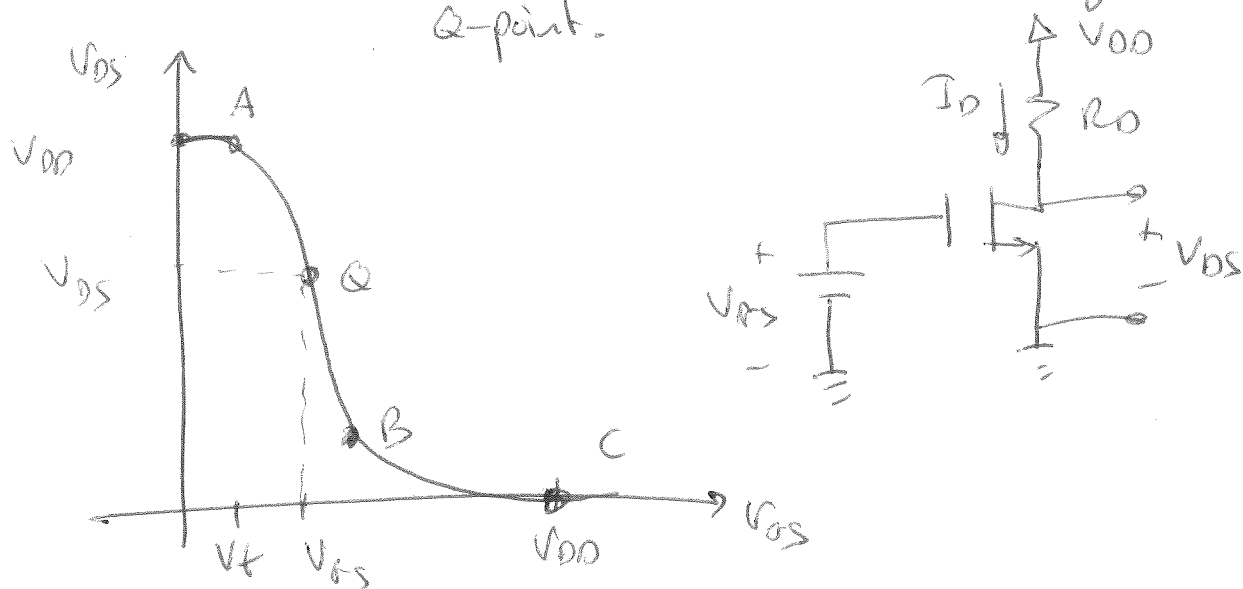
## 7.1.4. Biasing transistor for linear amplification. (or ~~small signal~~ linear)

→ Want to bias transistor in linear region of VTC.  
Q-point.



→ Point Q is known as bias point or dc operating point or quiescent point.  $\equiv$  Q-point (how to bias at this point next class.)

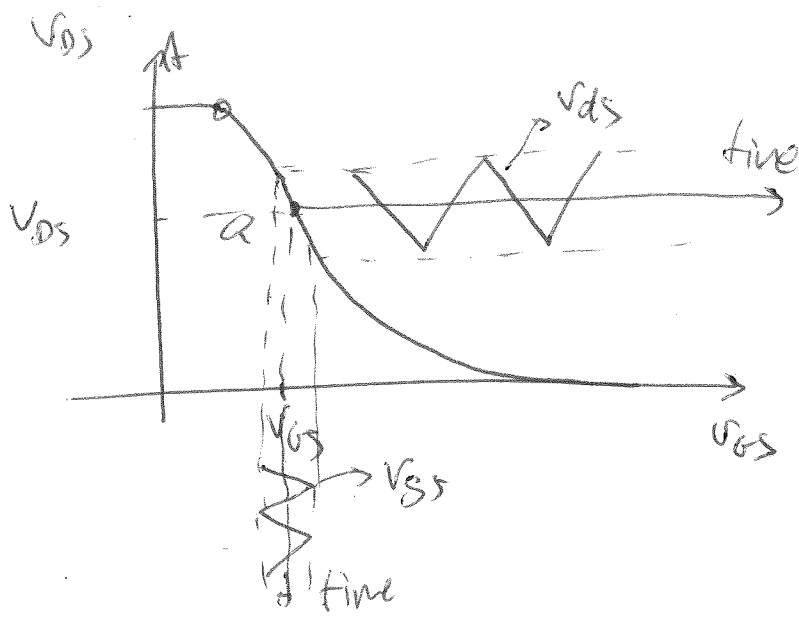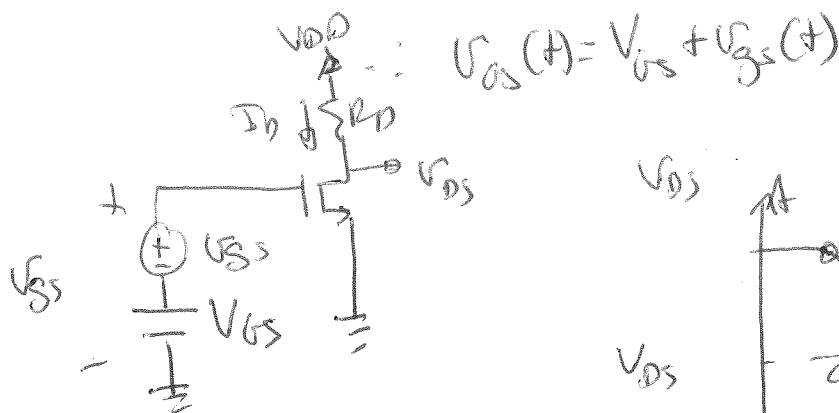→ Next superimpose signal to be amplified  $V_{GS}(t)$ .



shorter -  
The ~~lower~~ the ~~signal~~ the ~~greater~~ the ~~linearity~~ ~~advised~~.  
The ~~larger~~ the ~~greater~~ the ~~linearity~~ ~~advised~~.

→ large  $v_{gs}$  swing lead to non-linear amplification → distortion  
and turning off of MOSFET → "clipped off" clipping.

→ "Allowable signal swing at a pt."

$\frac{I_{DQ}}{I_{DQ}} \frac{16}{17} \uparrow$   
 $\frac{I_{DQ}}{I_{DQ}} \frac{17}{16} \downarrow$

## 7.15. Small-signal voltage gain.

$$A_v = \left. \frac{dV_{DS}}{dV_{GS}} \right|_{V_{GS}=V_{GS}} \leftarrow \text{at a-point}$$

$$V_{DS} = V_{DD} - \frac{1}{2} k_n R_D (V_{GS} - V_t)^2$$

$$\left. \frac{dV_{DS}}{dV_{GS}} \right|_{V_{GS}=V_{GS}} = -k_n R_D (V_{GS} - V_t) = -k_n R_D V_{OV} = A_v$$

→ gain is negative (inverting)

→ proportional to  $R_D$  and  $k_n$  and  $V_{OV}$

Also  $A_v = - \frac{I_{DQ} R_D}{V_{OV}/2}$

← for  $I_{DQ} = \frac{1}{2} k_n V_{OV}^2$

$$V_{OV}^2 = \frac{2 I_{DQ}}{k_n}$$

$$k_n = \frac{2 I_{DQ}}{V_{OV}^2}$$

$$A_v = - \frac{V_{DD} - V_{DS}}{V_{OV}/2}$$

at point B

$$\frac{V_{DD} - V_{DS}|_B}{V_{OV}|_B/2} = \frac{V_{DD} - V_{OV}|_B}{V_{OV}|_B/2}$$


$$V_{DS}|_B = V_{OV}|_B$$

more to go  
After small signal gain analysis



# 7.2. SMALL-SIGNAL OPERATION and MODELS

14/5/2016  
Electronics 1.

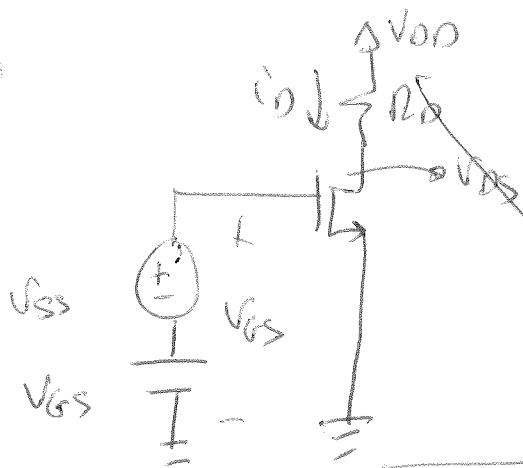

→ DC voltage  $V_{GS}$

→ Input signal to be applied →  $v_{gs}$

→ Output at voltage at drain.

→ Separate DC analysis and signal analysis

→ DC Bias Point:

$$I_D = \frac{1}{2} k_n (V_{GS} - V_t)^2 = \frac{1}{2} k_n V_{OV}^2 \quad (\lambda \approx 0)$$

→ at drain voltage  $V_{DS} = V_{DD} - I_D R_D$


$V_{DS} > V_{OV}$  (sat.)

↳ large enough to allow for voltage swing.

move to  
circuit model  
introduction

→ Signal current in Drain terminal. (signal analysis)

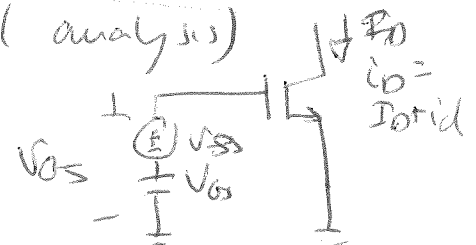total →  $V_{GS} = V_{GS} + v_{gs}$  → DC → small signal



$$I_D = \frac{1}{2} k_n (V_{GS} + v_{gs} - V_t)^2$$

$$I_D = \frac{1}{2} k_n (V_{GS} - V_t)^2 + k_n (V_{GS} - V_t) v_{gs} + \frac{1}{2} k_n v_{gs}^2$$

DC  $I_D$

proportional  
small-signal  $v_{gs}$


small (ignore)  
 $v_{gs}$  neglect

$$I_D \approx I_D + i_d$$

where  $i_d = k_n (V_{GS} - V_t) v_{gs}$

and  $\frac{i_d}{v_{gs}} = k_n (V_{GS} - V_t) \equiv g_m \rightarrow$  MOSFET transconductance

$$i_d = g_m \cdot v_{gs}$$

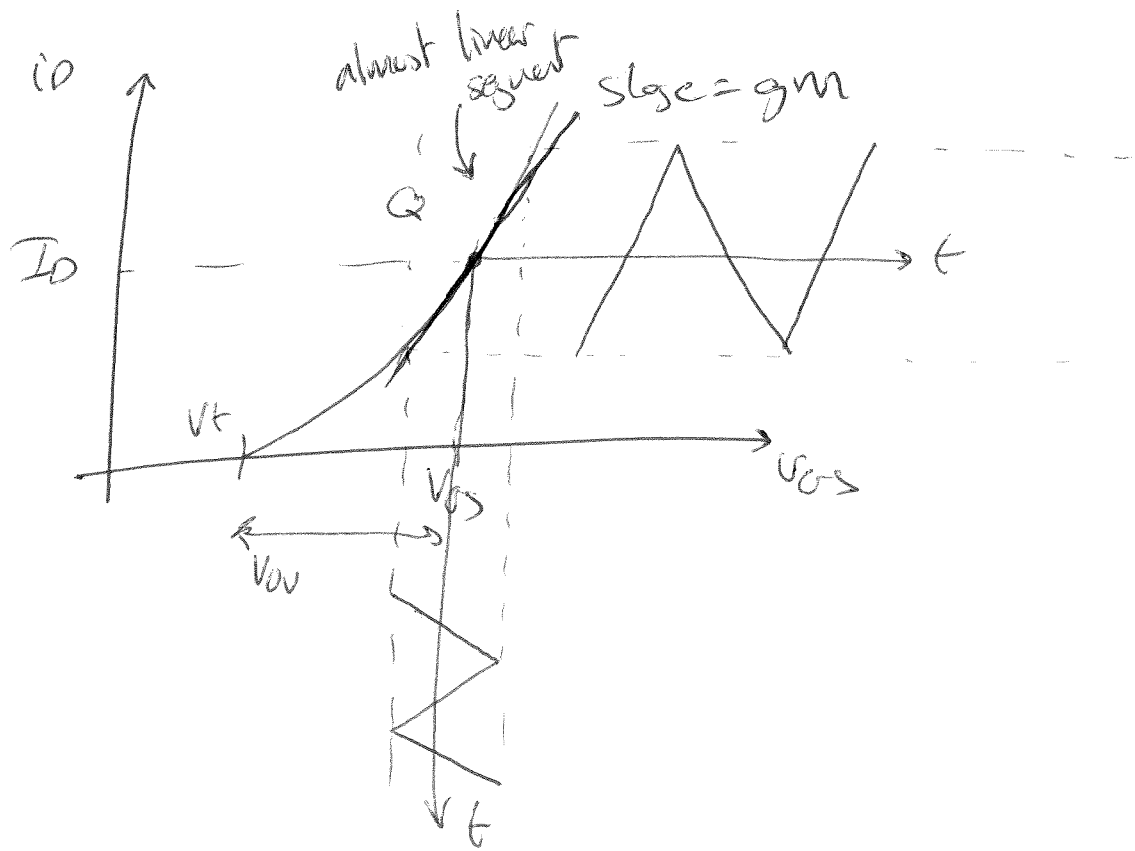

$$\rightarrow g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS} = V_{GS}} = k_n (V_{GS} - V_T) = k_n' \left( \frac{W}{L} \right) (V_{GS} - V_T) = k_n' \left( \frac{W}{L} \right) V_{OV}$$



$$\rightarrow \text{Also } g_m = \sqrt{2k_n} \sqrt{W/L} \sqrt{I_D}$$

$$\text{if } V_{OV} = \sqrt{\frac{2I_D}{k_n}} = \sqrt{\frac{2I_D}{k_n' (W/L)}}$$

$$\text{then } I_D = \frac{1}{2} k_n V_{OV}^2$$
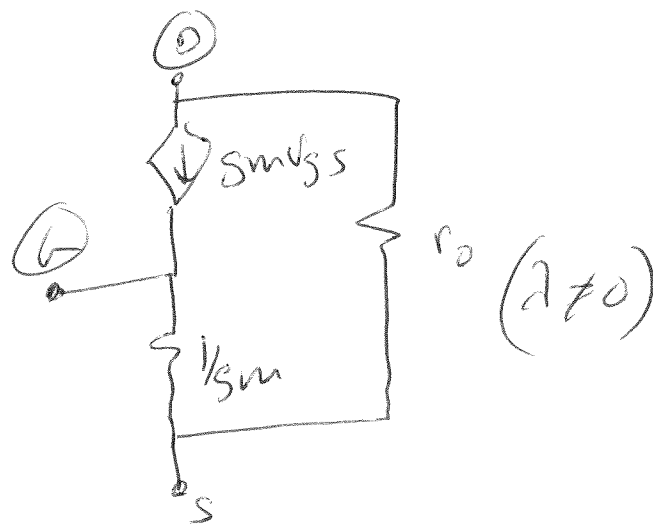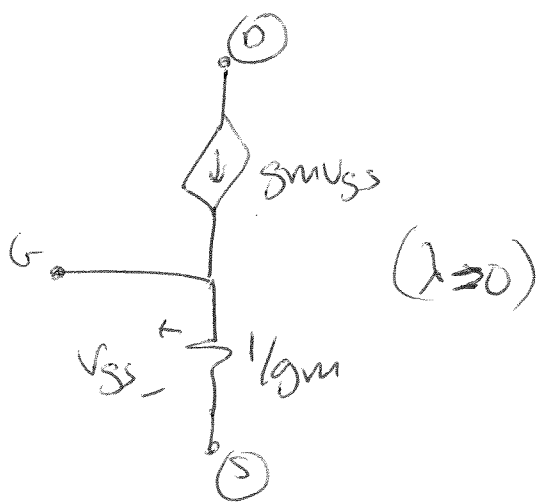
$$\rightarrow \text{And } g_m = \frac{2I_D}{V_{GS} - V_T} = \frac{2I_D}{V_{OV}}$$







T-model

Modeling the body effect:

$$g_{mb} \equiv \left. \frac{\partial i_D}{\partial V_{BS}} \right|_{V_{GS} = \text{constant}, V_{DS} = \text{constant}}$$

$$g_{mb} = \chi g_m$$

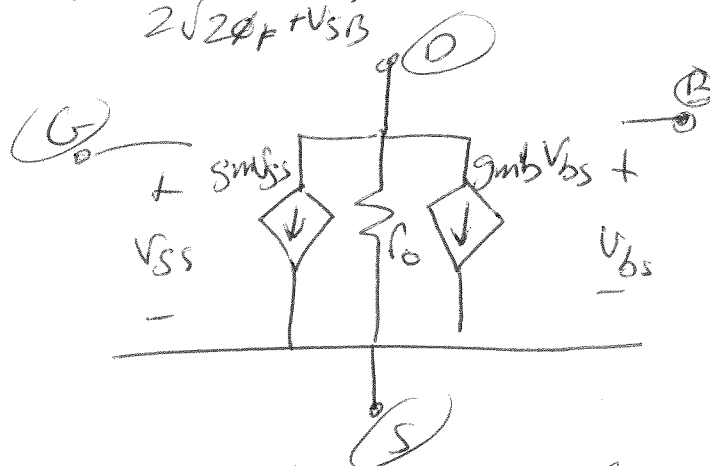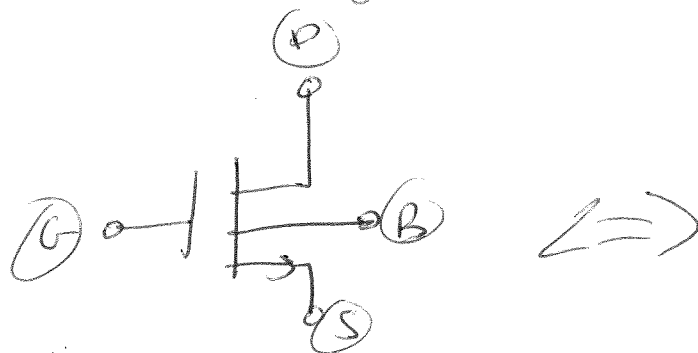
$$\chi = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}}$$



→ Systematic Procedure for analysis of transistor amplifier circuit.

1. Eliminate signal source + determine DC operating point.
2. Calculate
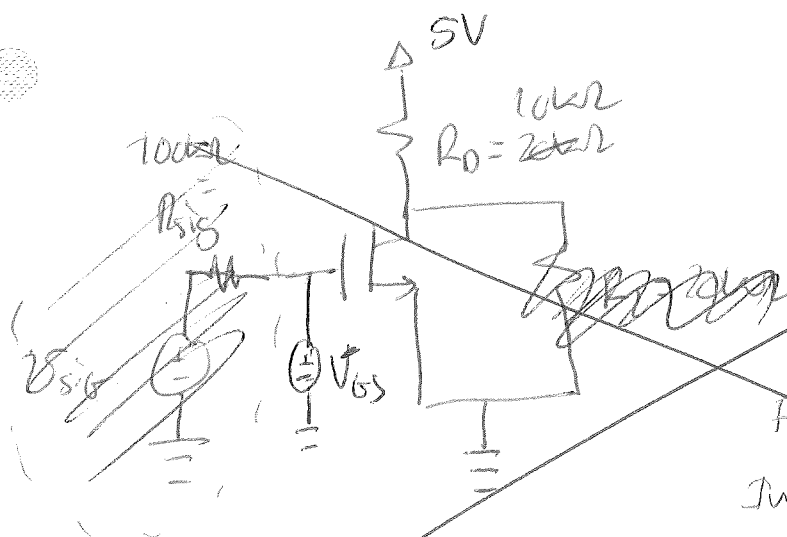
### 7.33 - Common-source (CS) amplifier - example.




$$I_D = 0.25 \text{ mA}$$

$$V_{ov} = 0.25 \text{ V}$$

Find  $R_{in}$ ,  $A_{vo}$ ,  $R_o$ ,  $A_v$ , and  $G_v$ .

Input sine wave limited to 10% of  $2V_{ov}$ , what is peak of sine-wave voltage at output?

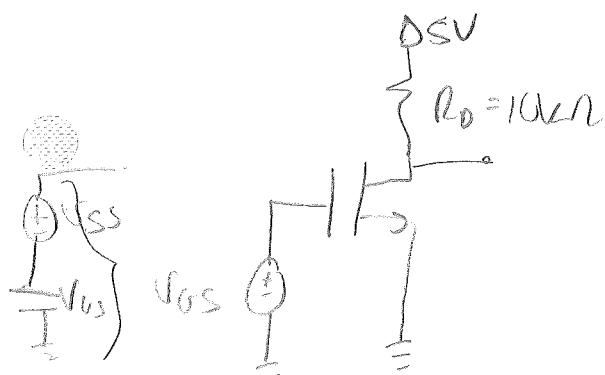DC Analysis  $I_D = \frac{1}{2} k_n (V_{GS} - V_T)^2$



$$V_T = 1 \text{ V}, k_n = 20 \mu\text{A/V}^2, \frac{W}{L} = 20, V_{GS} = 2 \text{ V}$$

$$V_{GS} = 0.2 \sin \omega t \text{ volts.}$$

$$\lambda = 0$$

(a) Find  $V_{DS}$  (DC) and  $I_D$  (DC)

(b) Find voltage gain.  $\frac{v_{ds}}{v_{gs}}$

1st - DC analysis's.

$$(a) \quad I_D = \frac{1}{2} k_n \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 = \frac{1}{2} 20 \times 10^{-6} \text{ A/V}^2 (20) (2 - 1)^2 = 200 \mu\text{A}$$

$$V_{DS} = V_{DD} - I_D R_D = 5 \text{ V} - (200 \mu\text{A})(10 \text{ k}\Omega) = 3 \text{ V}$$

(b) small-signal analysis  
(w/o) model:

$$V_{DS} = V_{DD} - i_D R_D$$


$$v_{ds} = -i_D R_D = -g_m v_{gs} R_D$$

$$\rightarrow \frac{v_{ds}}{v_{gs}} = -g_m R_D$$


$$g_m = \frac{i_D}{v_{gs}} = k_n' \frac{W}{L} (V_{GS} - V_T) = 20 \times 10^{-6} (20) (2 - 1) = 400 \times 10^{-6} \text{ A/V}$$

$$\left\{ \frac{v_{ds}}{v_{gs}} = -400 \times 10^{-6} \text{ A/V} \cdot 10 \text{ k}\Omega = -4 \text{ V/V} \right\}$$
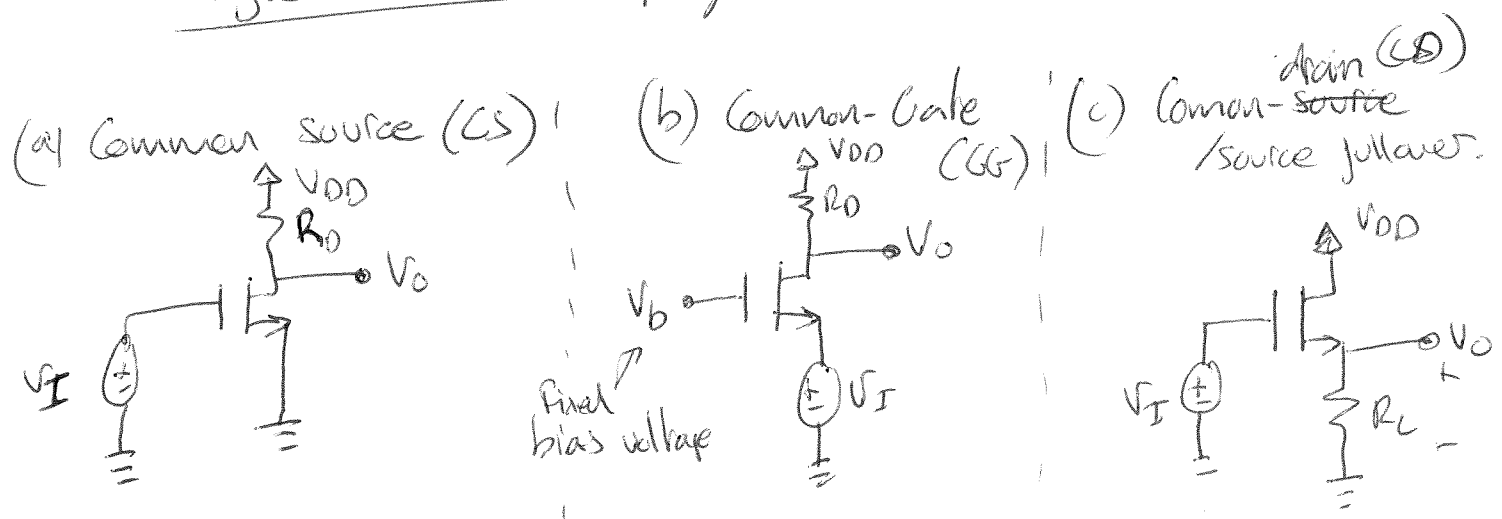
# 7.3.1. - Three basic configurations of single MOSFET amplifiers:



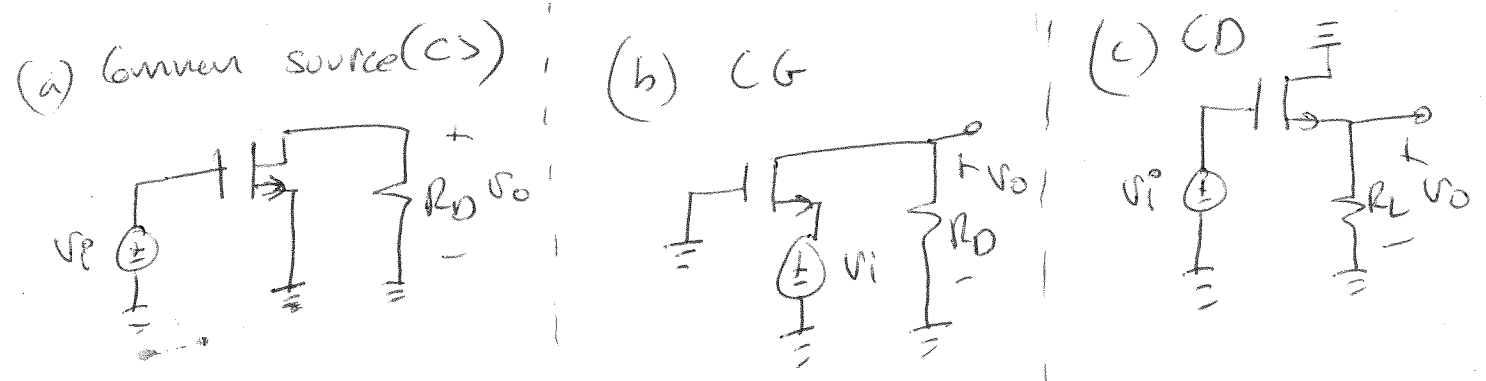signal-analysis circuits:  $V_{source} \rightarrow 0V$   
 $I_{source} \rightarrow 0A$       leave small signal sources on.



(a) Most common amplifier. Cascoded to obtain large amplification values


(b) CG - Gate voltage is fixed. Grounded for small signal analysis. Signal applied to source

(c) CD - Drain is grounded for small signal analysis. Signal applied to gate. Also known as source follower.

w/ model

10/6/2016 (3)

FRONT

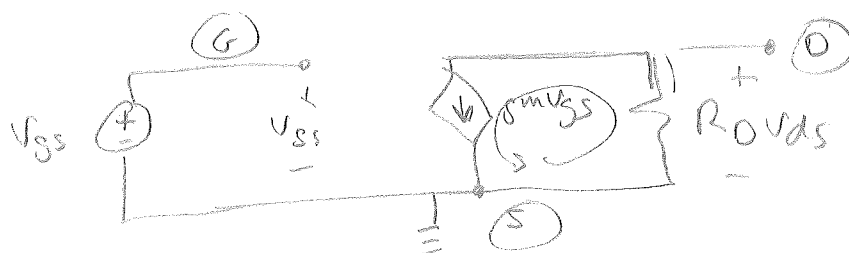

$$v_{ds} = -g_m \cdot v_{gs} \cdot R_O$$

$$\frac{v_{ds}}{v_{gs}} = -4V/V \quad (\text{same as before})$$


(C) If  $v_{gs} = 0.2 \sin \omega t$  volts, what are minimum and maximum values of  $v_{ds}$ .

$$v_{ds} = 0.8 \sin \omega t$$

$$v_{DS} = V_{DS} + v_{ds}$$

$$V_{DS_{max}} = 3V + 0.8V = 3.8V$$

$$V_{DS_{min}} = 3V - 0.8V = 2.2V$$

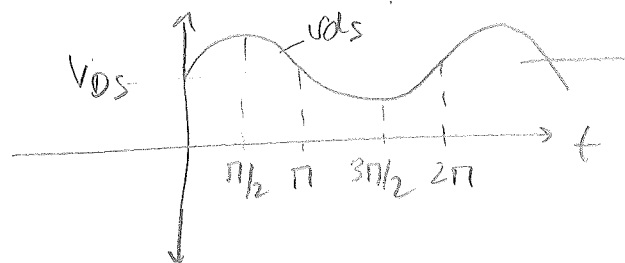


★ Systematic procedure for analysis of transfer amplifier circuits

1. Eliminate signal source + determine DC operating point.
2. Calculate values of small-signal model parameters
3. Eliminate DC sources.  $V_S \rightarrow 0V$ ,  $I_S \rightarrow 0A$   
short-circuit open-circuit
4. Replace transistors w/ small-signal model. Choose more appropriate one.
5. Analyze resulting circuit for required quantities  
(voltage gain, input resistance, etc.)

721 A CS w/ MOPET  $I_D = 0.25 \text{ mA}$  with  $V_{ov} = 0.25 \text{ V}$   
 $R_D = 20 \text{ k}\Omega$ . Amplifier signal  $R_{is} = 100 \text{ k}\Omega$   
 and output load  $= 20 \text{ k}\Omega$ .

~~BACK~~

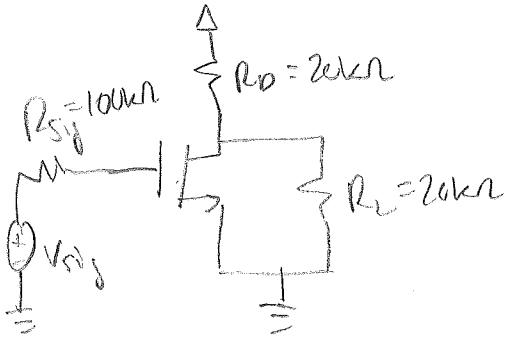
$V_{DD} \rightarrow F_{nd} \quad R_{in}, A_{vo}, R_o, A_v, G_v.$



$\rightarrow$  DC given.  
 $\rightarrow$  DO ac analysis.



$$V_i = V_{gs}$$

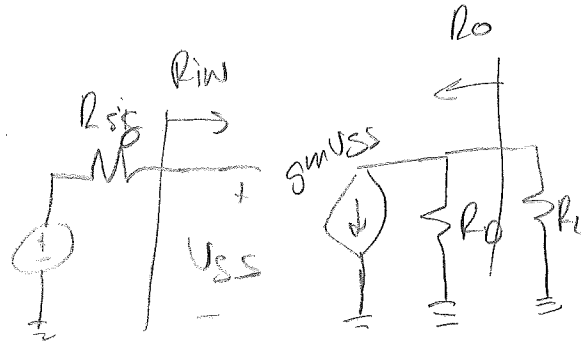


~~★~~

$$R_{in} = \frac{v_x}{i_x} = \frac{1}{0} = \infty$$



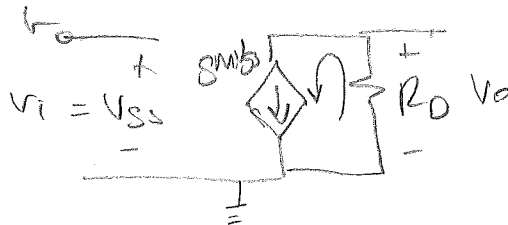~~★~~  $A_{vo} \rightarrow$  open circuit voltage gain



$$v_o = -g_m v_{gs} \cdot R_D$$

$$v_i = v_{gs}$$


$$v_o = -g_m v_i \cdot R_D$$

$$A_{vo} = \frac{v_o}{v_i} = -g_m R_D$$

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 0.25 \times 10^{-3} \text{ A}}{0.25 \text{ V}}$$

$$g_m = 2 \text{ mA/V}$$

$$|A_{vo}| = (2 \text{ mA/V}) (20 \text{ k}\Omega) = -40 \text{ V/V}$$

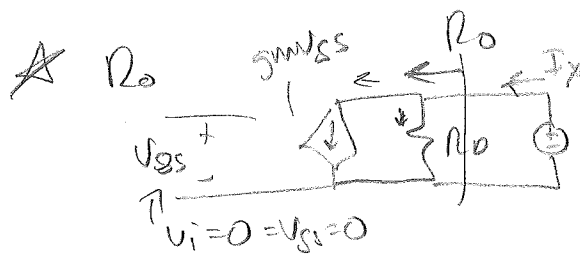

$$I_x = \frac{v_x}{R_D}$$

$$R_o = \frac{v_x}{I_x}$$


$$\therefore R_o = \frac{v_x}{v_x/R_D} = R_D = 20 \text{ k}\Omega$$

2 Conts



Cont'd  
Av

10/6/2016  
(4)

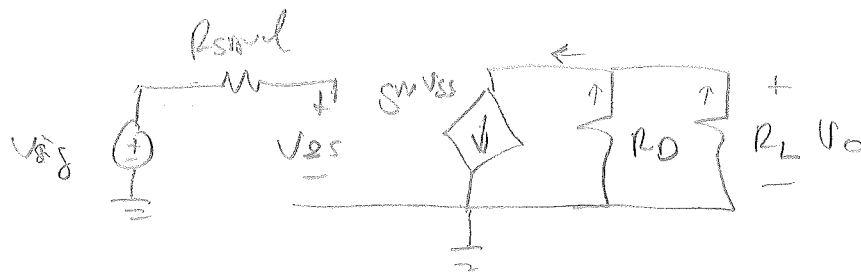

$$v_{gs} = v_i$$


$$R_o = 20k\Omega$$

$$v_o = -g_m v_{gs} (R_D // R_L)$$

$$A_v = \frac{v_o}{v_i} = -g_m (R_D // R_L) = -g_m \left( \frac{R_D R_L}{R_D + R_L} \right)$$

$$= -2mA/V (10k\Omega) \parallel 20k\Omega = -20V/V$$

Also:

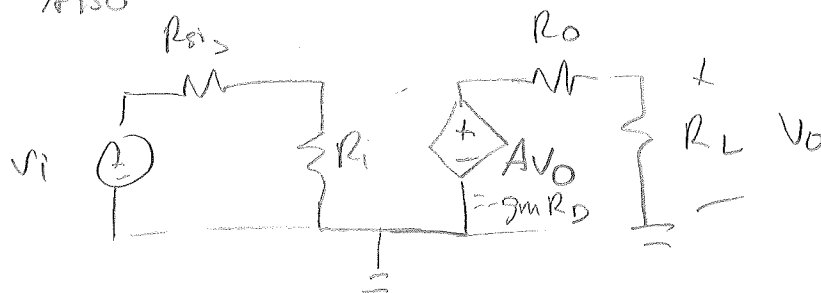

same.

$$R_{sig} = 100k\Omega$$

$$R_i = \infty$$

$$R_o = 20k\Omega$$

$$R_L = 20k\Omega$$

$$A_{vo} = -g_m R_D$$

$$g_m = 2mA/V$$

$$v_o = -g_m R_D \left( \frac{R_L}{R_o + R_L} \right) = -40 \left( \frac{20}{20 + 20} \right) = -20V/V$$

\* Also known as:

$$\text{Overall voltage gain} = \frac{v_o}{v_{sig}} = -20V/V$$

\* To maintain linearity peak of input is limited to 10% of 2Vov. What is peak of sine-wave voltage at input.



peak of  $v_i$  →  $\hat{v}_i = 0.1 \cdot 2(0.25V) = 0.05V$

$$\hat{v}_o = 0.05 \cdot (-20) = -1V \checkmark$$



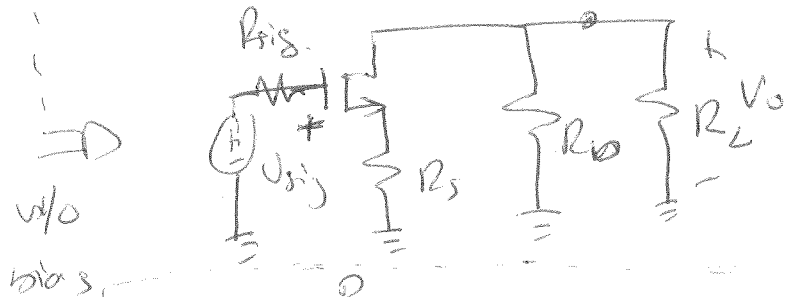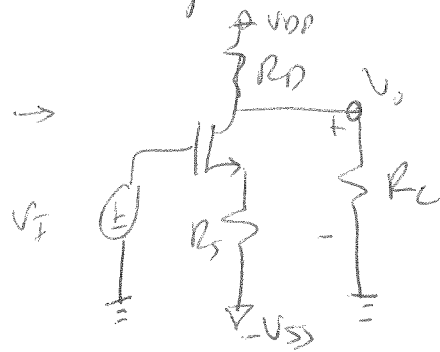
### 7.3.4. Common-source (CS) amplifier w/ a source resistance.

→ Beneficial to insert a resistance  $R_S$  in source lead.



⇒ Small signal:

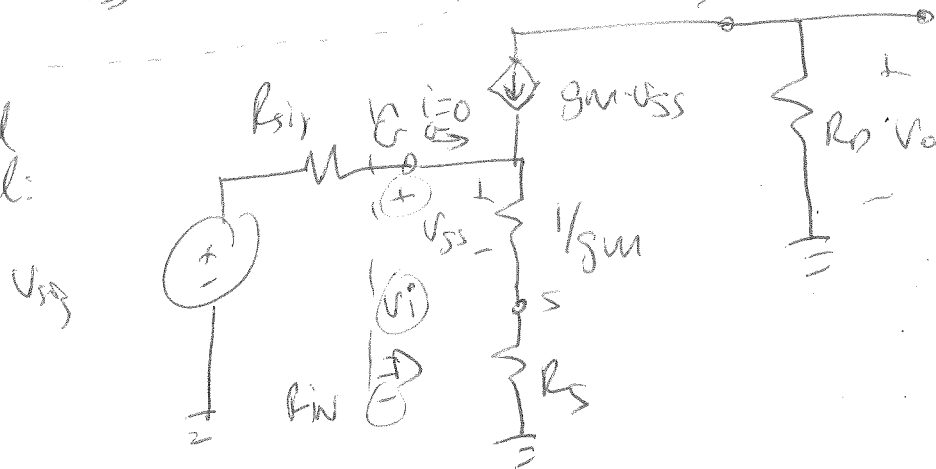

\* T-model used: whenever a resistance is connected in the source lead, the T-model is preferred.

$$R_{in} = \infty \text{ since } i_G = 0 \therefore (V_i = V_{sig})$$

→ but  $V_i \neq V_{GS}$

$$V_{GS} = V_i \frac{1/g_m}{1/g_m + R_S} = V_i \frac{1/g_m}{1/g_m} \frac{1}{1 + R_S g_m}$$

$$V_{GS} = V_i \frac{1}{1 + R_S g_m}$$

→ Magnitude of

$V_{GS}$  can be controlled by value of  $R_S$  and make sure it is not too large → output distortion.

→ Also: Extended Bandwidth of amplifier + negative feedback.

→ Negative feedback →

If  $V_{SS}$  and  $V_i$  constant and drain current increases, source current also increases and voltage drop across  $R_s$  also increases. Then  $V_{GS}$  decreases and drain current decreases, which counteracts initial change.

→ Output voltage  $v_o = -i R_D = -g_m v_{GS} R_D$

$$\text{and } g_m v_{GS} = \frac{V_i}{1/g_m + R_s} = V_i \frac{g_m}{g_m} \left( \frac{1}{1/g_m + R_s} \right)$$

$$g_m v_{GS} = V_i \left( \frac{g_m}{1 + g_m R_s} \right)$$

$$V_i = g_m v_{GS} \left( \frac{1 + g_m R_s}{g_m} \right)$$

$$\frac{v_o}{V_i} = \frac{-g_m v_{GS} R_D}{g_m v_{GS} \left( \frac{1 + g_m R_s}{g_m} \right)} = \frac{-R_D}{1 + g_m R_s} = \frac{-g_m R_D}{1 + g_m R_s}$$

$$A_{v_o} = \frac{-g_m R_D}{1 + g_m R_s} = - \frac{g_m}{g_m} \left( \frac{R_D}{1/g_m + R_s} \right) = \left[ - \frac{R_D}{1/g_m + R_s} \right]$$

Compared to ↙

CS  $A_{v_o} = -g_m R_D$

∴ Reduces gain.

Known as source-degeneration resistance

Also w/ load.  $\Rightarrow A_v = \frac{-g_m (R_D \parallel R_L)}{1 + g_m R_s} = \frac{-R_D \parallel R_L}{1/g_m + R_s}$

Ex.  
7.23

10/11/2016


Same as previous example but

②

$V_{sig} = 0.2V$  peak ~~and want~~ instead of  $50mV$  peak.  
and want to modify circuit (by adding  $R_s$ ) to  
keep  $V_{GS}$  unchanged and prevent ~~linear~~ nonlinear  
distortion.

Value of  $R_s$ ? What is voltage gain? Peak  
output voltage?

Prev.  $R_D = 20k\Omega$

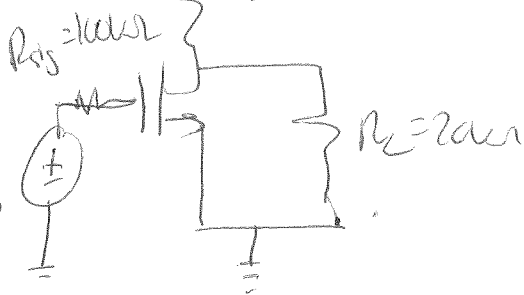


$I_D = 0.25mA$ ,  $V_{ov} = 0.25V$

$R_i = \infty$   
 $R_o = R_D$   
 $\hat{V}_{sig} = V_{GS} = 50mV$


$$A_v = -g_m R_D$$

$$A_v = -g_m (R_D || R_L)$$

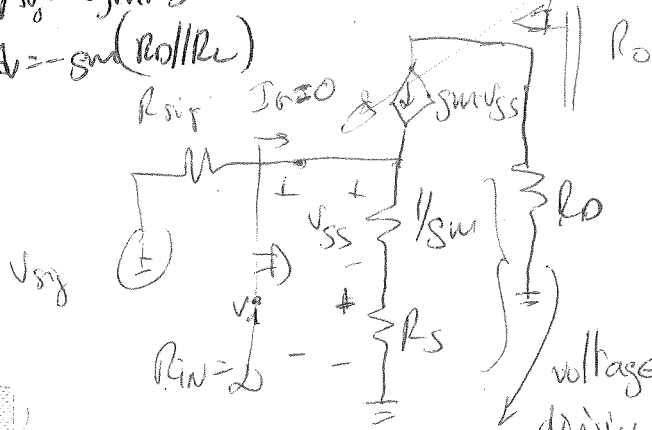

$$V_{GS} = V_i \frac{1/g_m}{1/g_m + R_s}$$

New

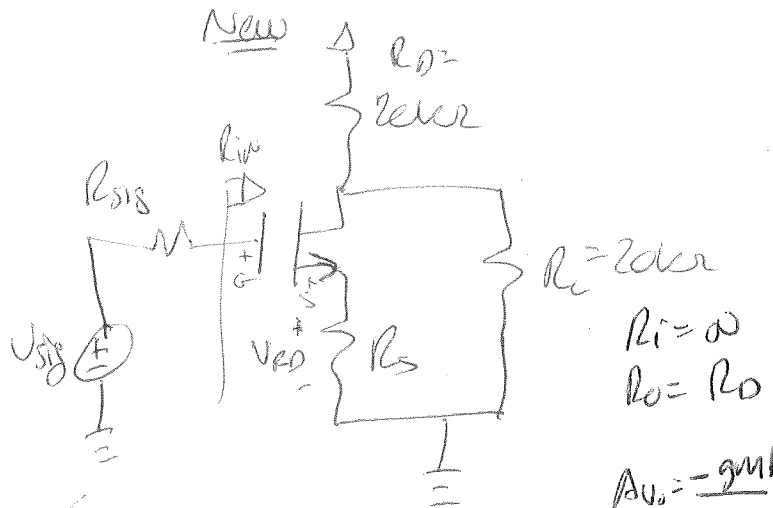

$$R_i = \infty$$

$$R_o = R_D$$

$$A_{v0} = \frac{-g_m R_D}{1 + g_m R_s}$$

$$A_v = \frac{-g_m R_D || R_L}{1 + g_m R_s}$$

$\hat{V}_{sig} = 0.2V \neq V_{GS}$

$\rightarrow$  want  $\hat{V}_{GS} = 50mV$

$R_i$  is still  $\infty$  since  $I_D = 0$

$$\therefore V_{GS} = V_i = V_{GS} + I_D R_s \quad g_m V_{GS} R_s$$

$$V_i = V_{GS} (1 + g_m R_s)$$

$$V_{GS} = V_i \left( \frac{1}{1 + g_m R_s} \right) \quad \checkmark$$

$$V_{GS} = V_i \frac{1/g_m}{1/g_m + R_s} \left( \frac{1}{1 + g_m R_s} \right)$$

$$V_{GS} = V_i \left( \frac{1/g_m}{1/g_m + R_s} \right) \quad \text{LD Conf}$$

Cont'd

~~want  $V_{GS} = \frac{V_{DD}}{2}$~~

$$V_{GS} = \frac{V_i}{1 + g_m R_s} \rightarrow \text{want}$$

$$V_{GS} = 50 \text{ mV}$$

$$\text{want } V_i = 0.2 \text{ V}$$

$$\text{then } V_{GS} = 50 \text{ mV} = \frac{0.2 \text{ V}}{1 + g_m R_s}$$

$$\therefore g_m R_s = 3$$

$$\rightarrow \left| \cancel{R_s = \frac{g_m}{3}} \right| R_s = \frac{3}{g_m}$$

---

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.25 \times 10^{-3} \text{ A}}{0.25 \text{ V}} = 2 \text{ mA/V}$$

$$\rightarrow R_s = \frac{2 \times 10^{-3} \text{ A/V}}{2} = \frac{3}{2 \times 10^{-3} \text{ A/V}} = 1.5 \text{ k}\Omega$$

$$G_v = A_v = \frac{-R_D \parallel R_L}{1/g_m + R_s} = - \frac{(20 \parallel 20) \times 10^3}{0.5 \times 10^3 + 1.5 \times 10^3} = -5 \text{ V/V}$$

$$\hat{V}_o = G_v \cdot \hat{V}_{GS} = 5 \times 0.2 = 1 \text{ V (unchanged)}$$

---

HW#5 7.25, 7.30, 7.32, 7.59, 7.64, 7.71